




**ON Semiconductor®**

# The Dark Side of Loop Control Theory

Christophe Basso

IEEE Senior Member

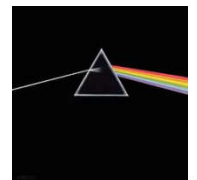

# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough



# What is the Purpose of this Seminar?

- ❑ There have been numerous seminars on control loop theory
- ❑ Seminars are usually highly theoretical – link to the market?
- ❑ Control theory is a vast territory: you don't need to know everything!
- ❑ This 3-hour seminar will shed light on some of the less covered topics:
  - ❖ PID compensators and classical poles/zeros compensation
  - ❖ Output impedance considerations in a switching regulator
  - ❖ Understanding delay and modulus margins
- In a 3-hour course, we are just scratching the surface...!



---

# Course Agenda

## Introduction to Control Systems

Shaping the Error Signal

How to Implement the PID Block?

The PID at Work with a Buck Converter

Considering the Output Impedance

Classical Poles/Zeros Placement

Shaping the Output Impedance

Quality Factor and Phase Margin


What is Delay Margin?

Gain Margin is not Enough



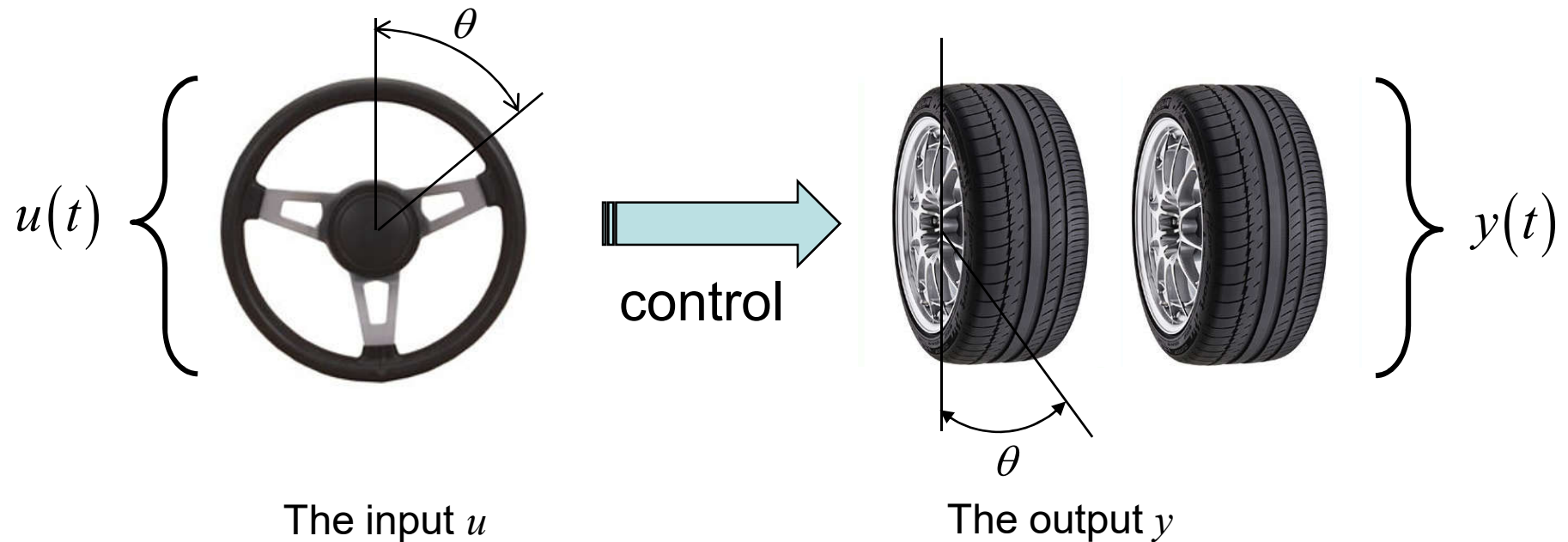
# What is a Closed-Loop System?

- ❑ A closed-loop system forces a variable to follow a setpoint
- ❑ The setpoint is the input, the controlled variable is the output
- ❑ French term is "enslavement": the output is slave to the input
- ❑ A car steering wheel is a possible example:


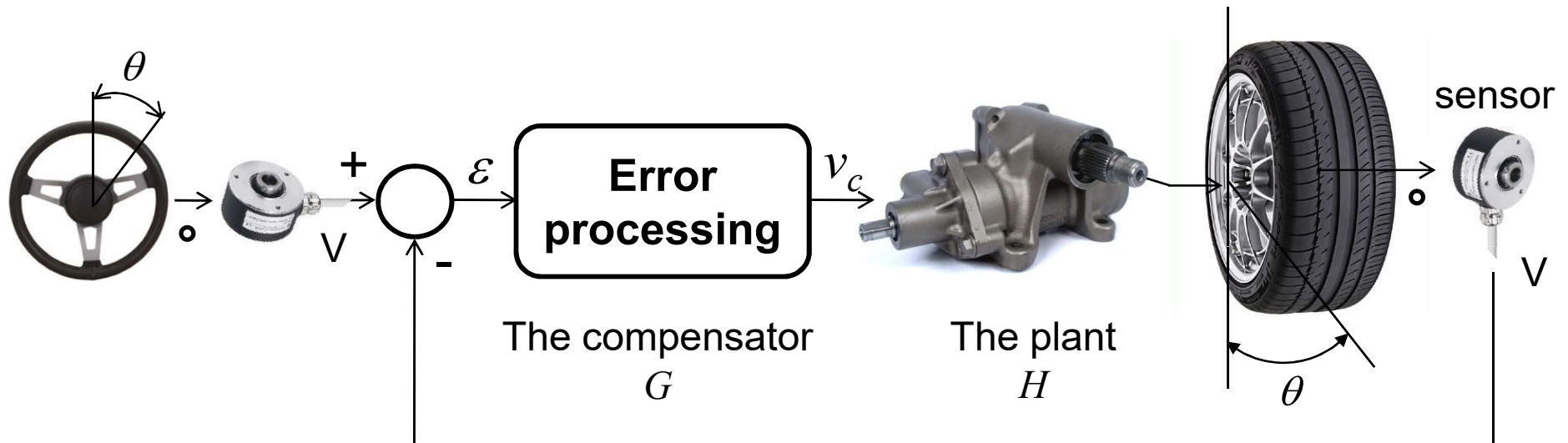
# Representing a Closed-Loop System

- ❑ A closed-loop system can be represented by blocks
- ❑ The output is monitored and compared to the input




- ❑ Any deviation between the two gives birth to an error  $\varepsilon$
- ❑ This error is amplified and drives a corrective action
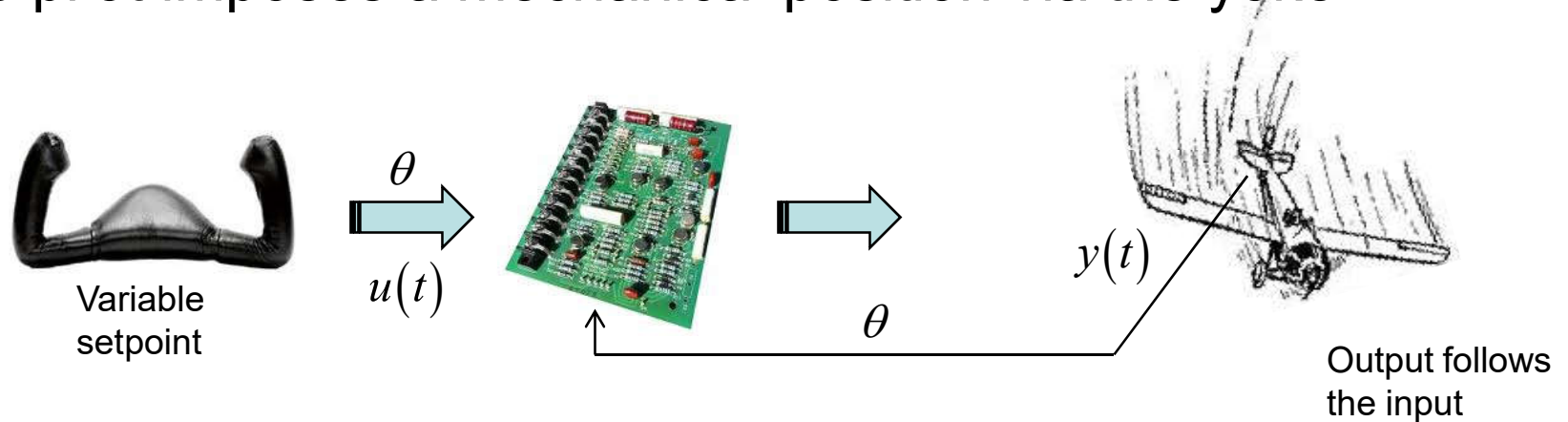
# A Servomechanism or a Regulator?


□ Airplane elevator control is a servo-mechanism:

- The pilot imposes a mechanical position via the yoke





□ Car cruise control is a regulator:

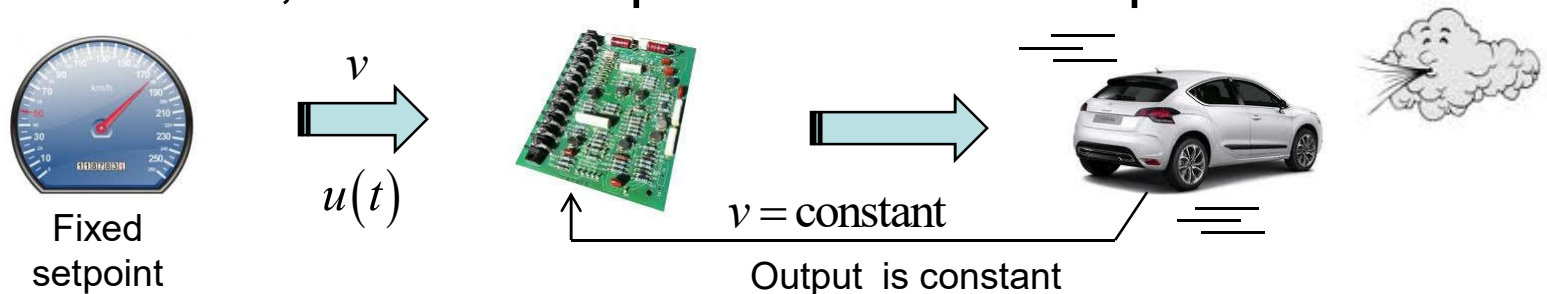- The speed is set, the car keeps it constant despite wind, etc.


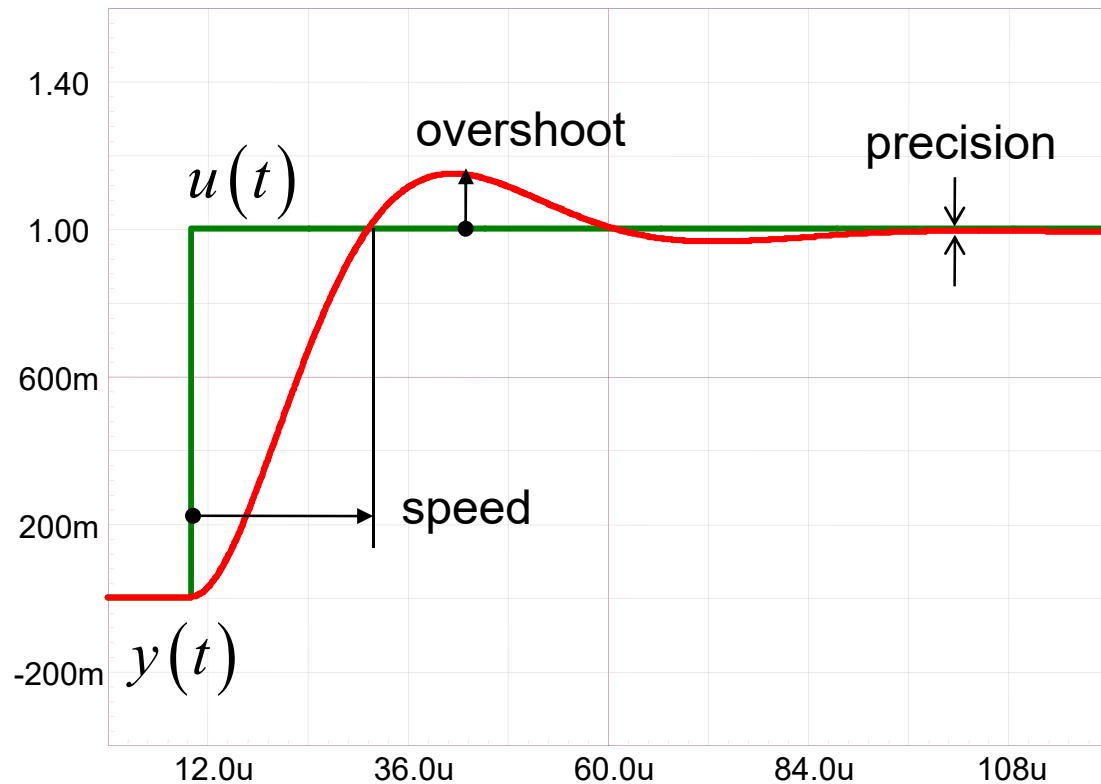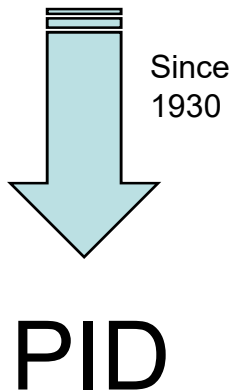
# Processing the Error Signal

- ❑ The error signal is processed through the compensator  $G$
- ❑ We want the following operating characteristics:
  - ✓ Speed
  - ✓ Precision
  - ✓ Robustness





---

# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal**
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough






# Where do You Shape the Signal?

- The compensator is the place where you apply corrections





The compensator:  $G$

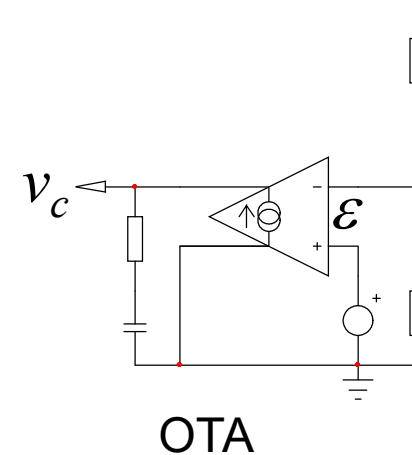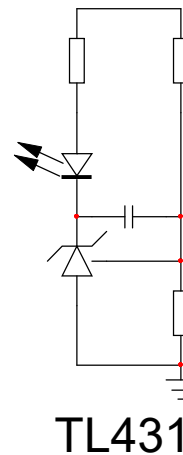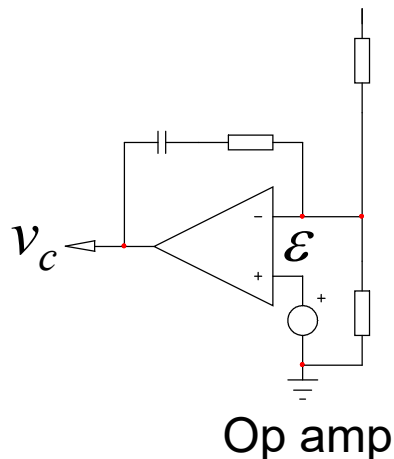- The compensator is built with an error amplifier:



# The PID Compensator

□ A PID welcomes a Proportional block

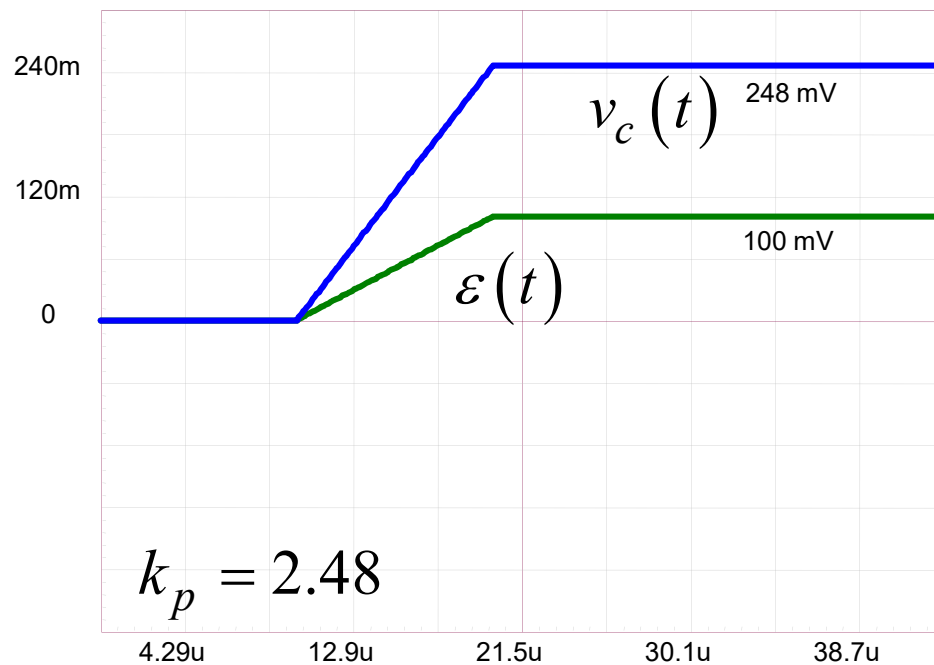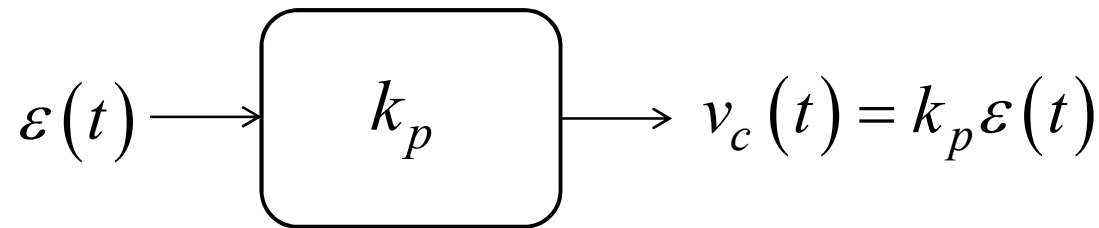

$k_p$  is high:

- ✓ reaction speed
- ❖ risks of overshoot


$k_p$  is low:

- ❖ sluggish response
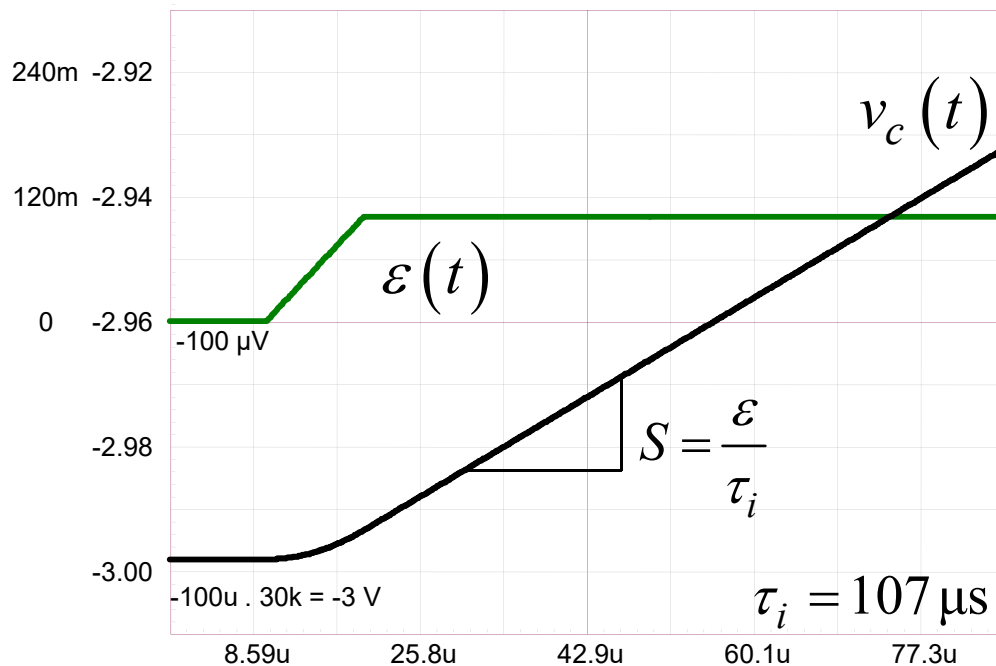
# The PID Compensator

□ A PID includes an Integrating block

$$\varepsilon(t) \rightarrow \left[ \frac{k_p}{\tau_i} \int \right] \rightarrow v_c(t) = \frac{k_p}{\tau_i} \int_0^t \varepsilon(\tau) d\tau$$




Integral action:

- ✓ no static error
- ❖ slow response
- ❖ decreases stability
- ❖ large overshoots
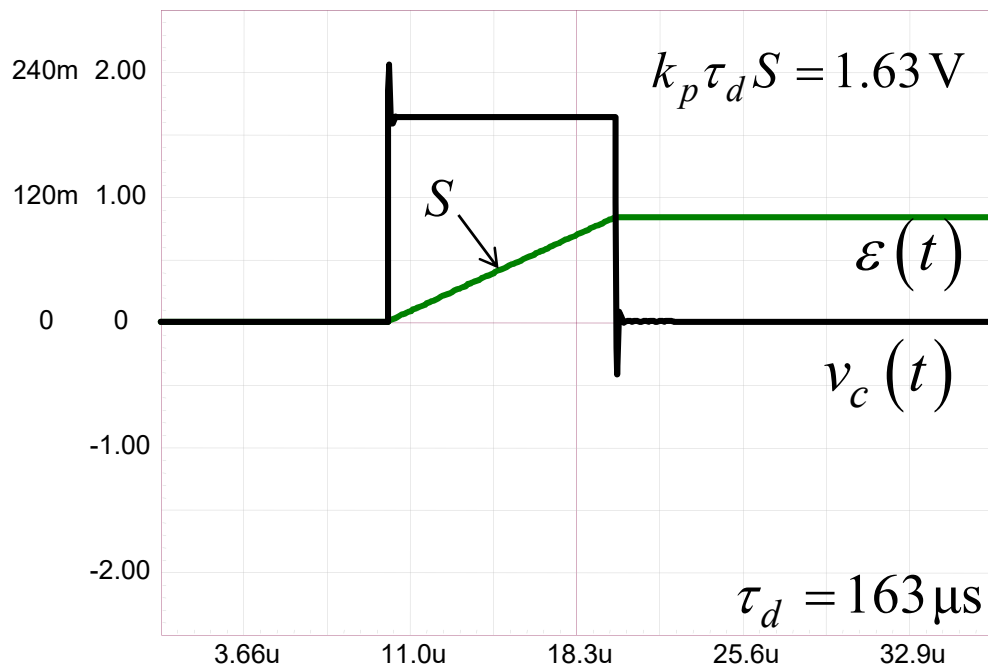
# The PID Compensator

□ A PID offers a Derivative block

$$\varepsilon(t) \rightarrow \left[ k_p \tau_d \frac{d}{dt} \right] \rightarrow v_c(t) = k_p \tau_d \frac{d\varepsilon(t)}{dt}$$




Derivative action:

- ✓ perturbation variation is known: anticipation
- ✓ stabilizes the response
- no static effect
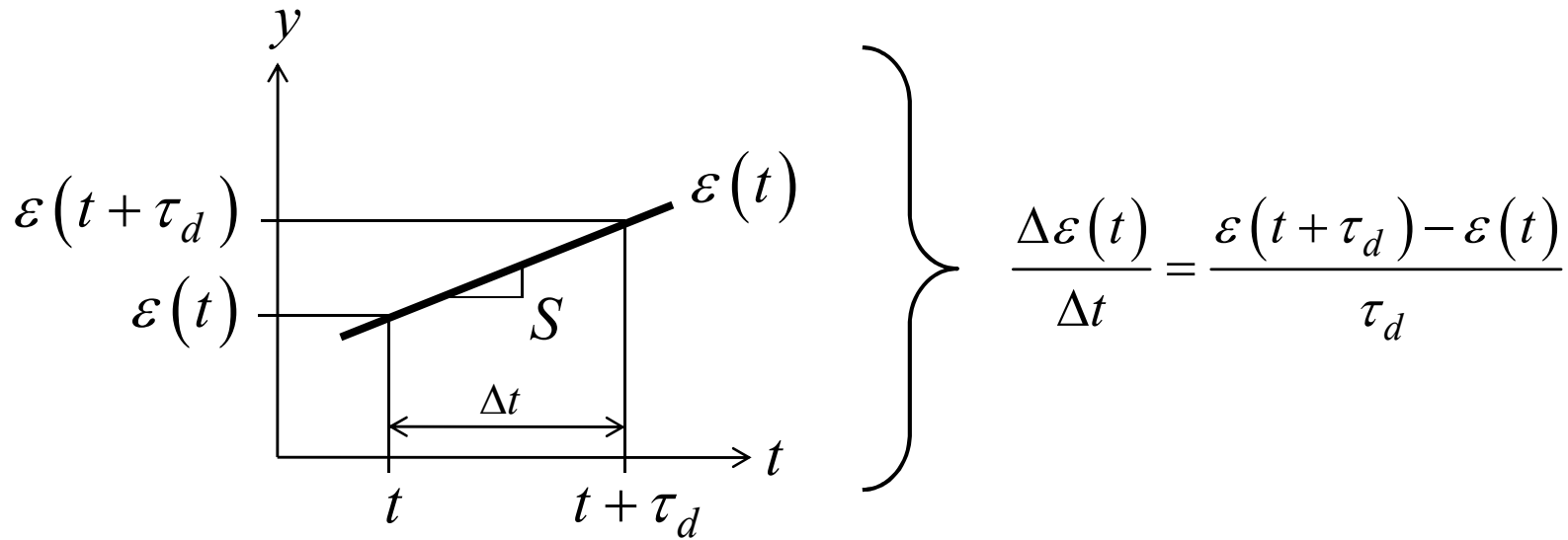
# The PID Compensator

- The Derivative block anticipates the signal evolution and speed



if  $\tau_d$  small  $\Rightarrow$

$$\varepsilon(t + \tau_d) \approx \varepsilon(t) + \tau_d \frac{d\varepsilon(t)}{dt}$$

later      now



# Combining the Blocks

❑ You can formulate the PID transfer function in different ways:

➤ differentiation:  $v_c(t) = \frac{d\varepsilon(t)}{dt} \rightarrow V_c(s) = \varepsilon(s)s$

➤ integration:  $v_c(t) = \int \varepsilon(t) dt \rightarrow V_c(s) = \frac{\varepsilon(s)}{s}$

❑ The standard form:


$$G(s) = k_p \left( 1 + \frac{1}{s\tau_i} + s\tau_d \right)$$

❑ The parallel form:

$$G(s) = k_p + \frac{k_i}{s} + sk_d$$

The derivative term cannot be physically implemented:
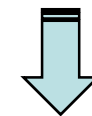
$$\lim_{s \rightarrow \infty} s\tau_d = \infty$$



Need a pole

$$s\tau_d \rightarrow \frac{s\tau_d}{1 + \frac{s\tau_d}{N}}$$



# Combining the Blocks

- The transfer function becomes a filtered PID:

$$G(s) = k_p \left( 1 + \frac{1}{s\tau_i} + \frac{s\tau_d}{1 + \frac{s\tau_d}{N}} \right)$$

- If we develop, we obtain a more familiar expression:

$$G(s) = \frac{1 + s \left( \frac{\tau_d}{N} + \tau_i \right) + s^2 \left( \frac{\tau_d \tau_i}{N} + \tau_d \tau_i \right)}{s \frac{\tau_i}{k_p} \left( 1 + \frac{\tau_d}{N} s \right)}$$

A double zero  
An origin pole  
A high-frequency pole






# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?**
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough


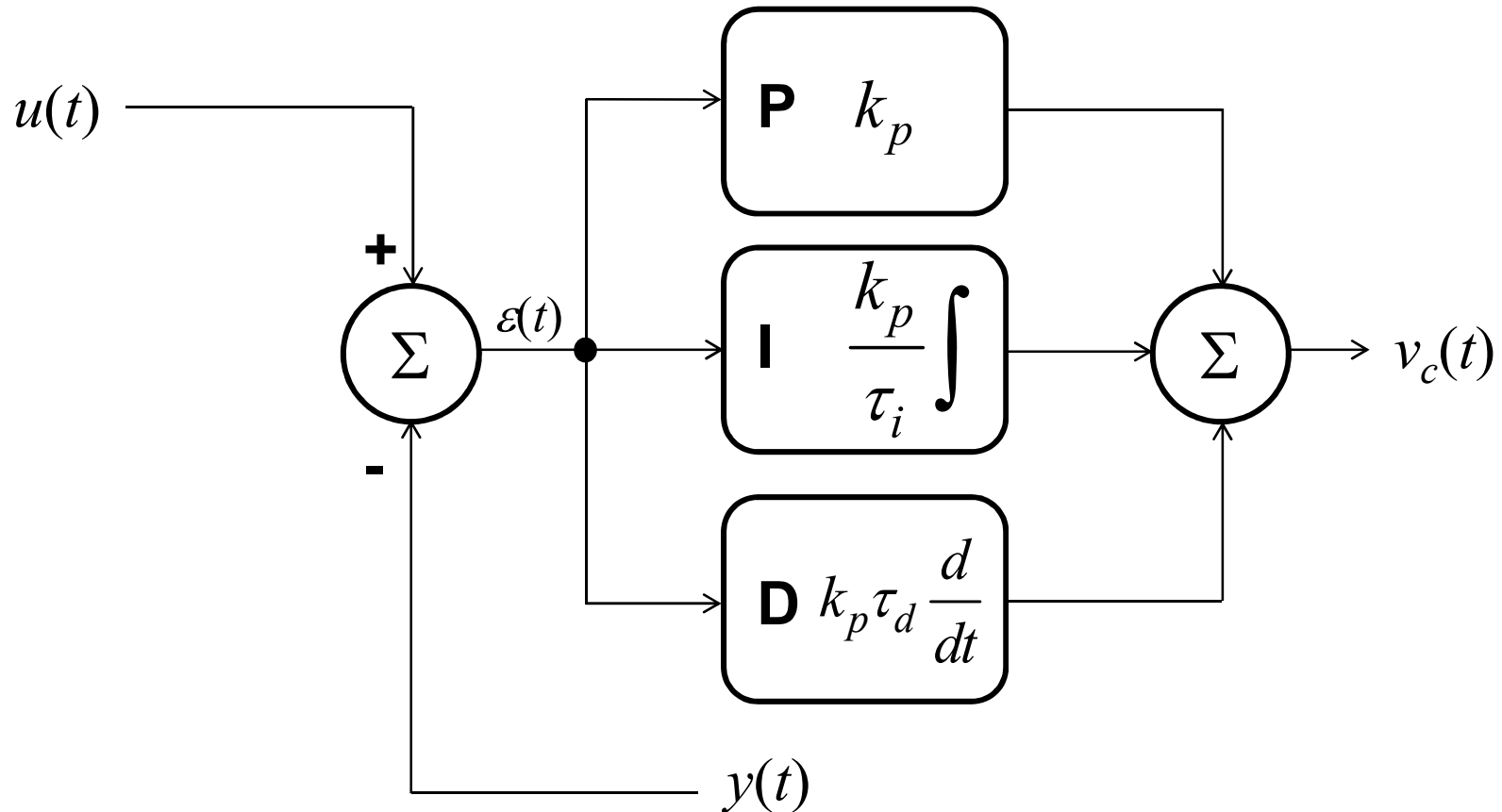
# Practical Implementation


- Sum up the output of each individual block:



- This is the parallel form of the PID

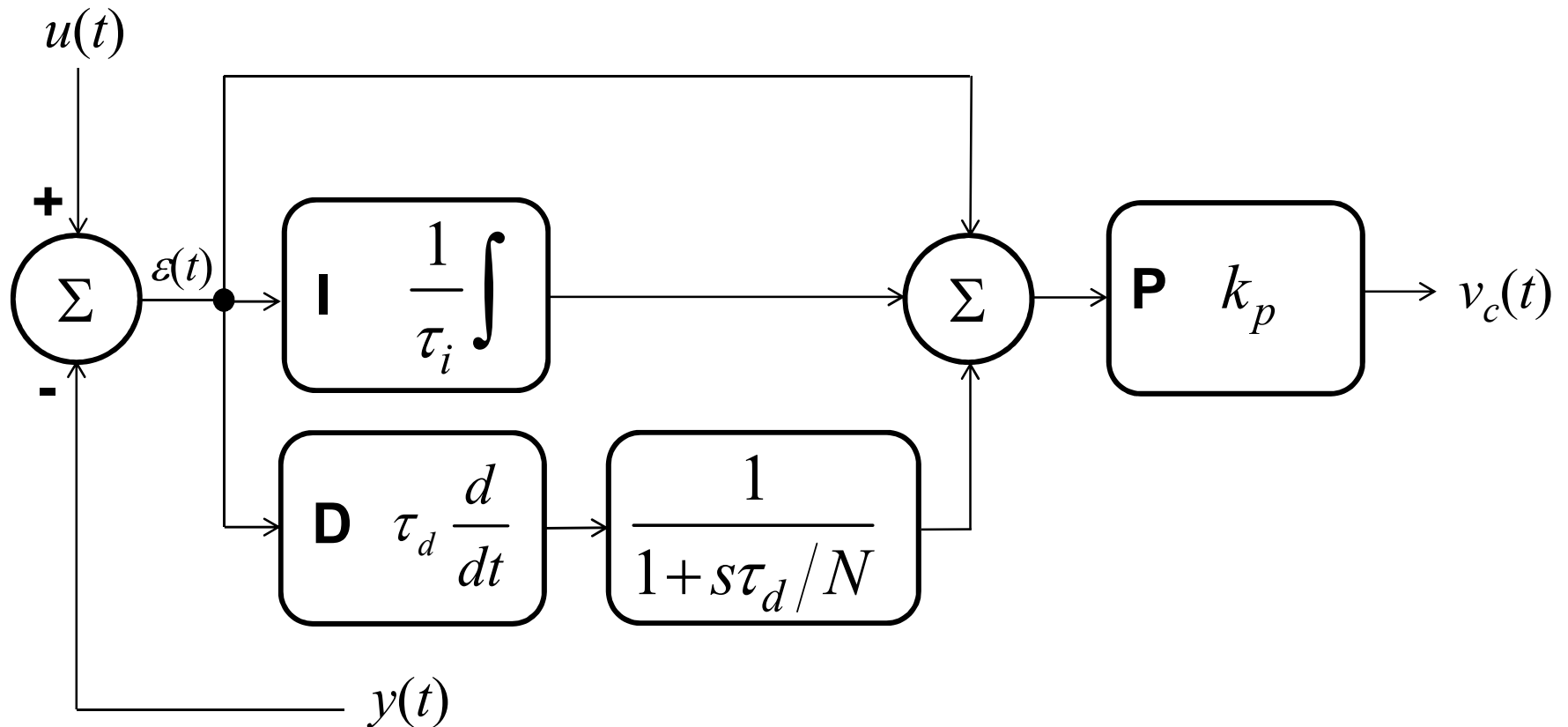
# Practical Implementation

- This is the filtered standard form of the PID


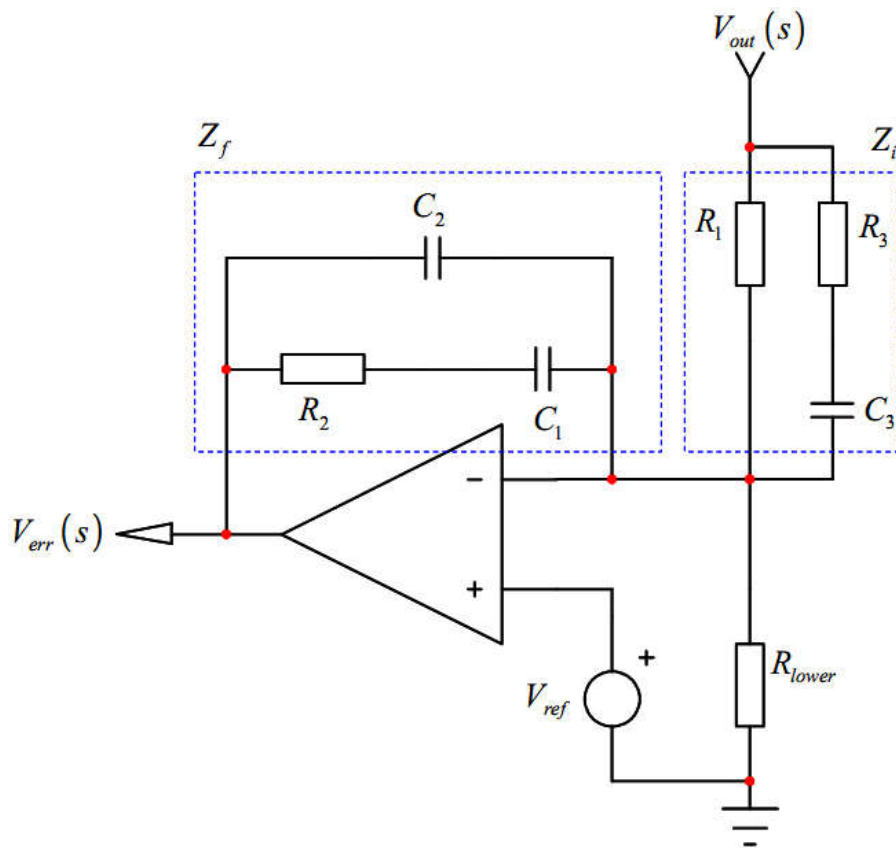
# Bridging a PID to a Type 3

- A type 3 is implemented around an op amp



$$G(s) = \frac{(1 + s/\omega_{z_1})(1 + s/\omega_{z_2})}{\frac{s}{\omega_{po}} \left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)}$$

↓

$$G(s) = \frac{1 + s \left( \frac{1}{\omega_{z_1}} + \frac{1}{\omega_{z_2}} \right) + s^2 \left( \frac{1}{\omega_{z_1} \omega_{z_2}} \right)}{\frac{s}{\omega_{po}} \left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)}$$

← Added pole

## Bridging a PID to a Type 3

- Identify the terms and write the equations:

$$G(s) = \frac{1 + s \left( \frac{\tau_d}{N} + \tau_i \right) + s^2 \left( \frac{\tau_d \tau_i}{N_1} + \tau_d \tau_i \right)}{s \frac{\tau_i}{k_p} \left( 1 + \frac{\tau_d}{N} s \right)}$$
$$G(s) = \frac{1 + s \left( \frac{1}{\omega_{z1}} + \frac{1}{\omega_{z2}} \right) + s^2 \left( \frac{1}{\omega_{z1} \omega_{z2}} \right)}{\frac{s}{\omega_{po}} \left( 1 + \frac{s}{\omega_{p1}} \right)}$$

- Four unknowns, four equations:

$$\frac{\tau_d}{N} + \tau_i = \frac{1}{\omega_{z1}} + \frac{1}{\omega_{z2}}$$

$$\frac{\tau_d \tau_i}{N} + \tau_d \tau_i = \frac{1}{\omega_{z1} \omega_{z2}}$$

$$\frac{\tau_i}{k_p} = \frac{1}{\omega_{po}}$$

$$\frac{\tau_d}{N} = \frac{1}{\omega_{p1}}$$

# Bridging a PID to a Type 3

□ From Type 3 to PID:

$$\tau_d = \frac{(\omega_{p_1} - \omega_{z_1})(\omega_{p_1} - \omega_{z_2})}{(\omega_{p_1}\omega_{z_1} + \omega_{p_1}\omega_{z_2} - \omega_{z_1}\omega_{z_2})\omega_{p_1}} \quad N = \frac{\omega_{p_1}^2}{\omega_{p_1}\omega_{z_1} + \omega_{p_1}\omega_{z_2} - \omega_{z_1}\omega_{z_2}} - 1$$

$$\tau_i = \frac{\omega_{z_1} + \omega_{z_2}}{\omega_{z_1}\omega_{z_2}} - \frac{1}{\omega_{p_1}} \quad k_p = \frac{\omega_{p_0}}{\omega_{z_1}} - \frac{\omega_{p_0}}{\omega_{p_1}} + \frac{\omega_{p_0}}{\omega_{z_2}}$$

□ From PID to Type 3:

$$f_{z_1} = \frac{\tau_d - \sqrt{-4N^2\tau_d\tau_i + N^2\tau_i^2 - 2N\tau_d\tau_i + \tau_d^2} + N\tau_i}{2\tau_d\tau_i(1+N)2\pi} \quad f_{p_1} = \frac{N}{2\pi\tau_d}$$

$$f_{z_2} = \frac{\tau_d + \sqrt{-4N^2\tau_d\tau_i + N^2\tau_i^2 - 2N\tau_d\tau_i + \tau_d^2} + N\tau_i}{2\tau_d\tau_i(1+N)2\pi} \quad f_{p_0} = \frac{k_p}{2\pi\tau_i}$$



# Testing the Conversion

□ Assume a type 3 compensator calculated for:

$$G_{f_c} = 1 \quad \text{at a crossover of} \quad f_c = 2740 \text{ Hz}$$

$$f_{z_1} = 200 \text{ Hz} \quad f_{z_2} = 600 \text{ Hz} \quad f_{p_1} = 21400 \text{ Hz} \quad f_{p_2} = 21400 \text{ Hz}$$

□ The "0-dB crossover" pole is placed at:

↑  
High-frequency  
pole

$$f_{po} = \frac{\sqrt{1 + \left(\frac{f_c}{f_{p_1}}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{p_2}}\right)^2}}{\sqrt{1 + \left(\frac{f_{z_1}}{f_c}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{z_2}}\right)^2}} G_{f_c} f_{z_1} = 43.4 \text{ Hz} = 272 \text{ rd/s}$$

⇒  $\tau_d = 194\mu$      $\tau_i = 1.05\text{m}$      $N = 25.6$      $k_p = 0.287$

# What is the "0-dB Crossover" Pole?


- $s$  appears as an isolated term in  $N(s)$ , it is an origin pole

$$G(s) = \frac{1}{s(1 + s/\omega_{p1})} \quad s = 0 \text{ is the origin pole}$$

- If  $s$  is affected by a coefficient it is the "0-dB crossover pole"

$$G(s) = \frac{1 + s/s_{z1}}{As(1 + s/\omega_{p1})} = \frac{\frac{s}{s_{z1}}(s_{z1}/s + 1)}{\frac{s}{\omega_{po}}(1 + s/\omega_{p1})} = \frac{\omega_{po}}{\omega_{z1}} \frac{(s_{z1}/s + 1)}{(1 + s/\omega_{p1})} = G_0 \frac{(s_{z1}/s + 1)}{(1 + s/\omega_{p1})}$$


Dimension of a gain

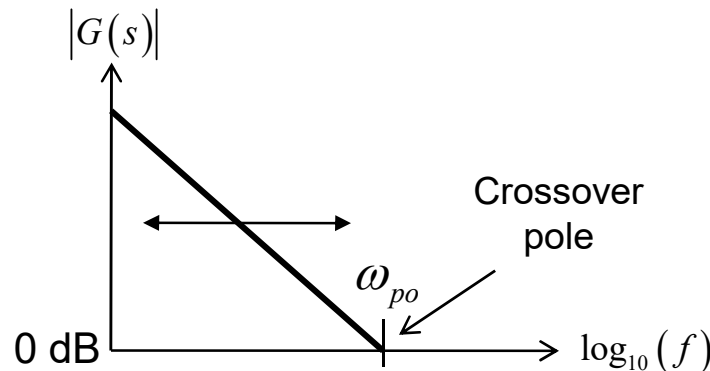



# Testing with Mathcad®

- We wanted a magnitude of 1 at 2.7 kHz

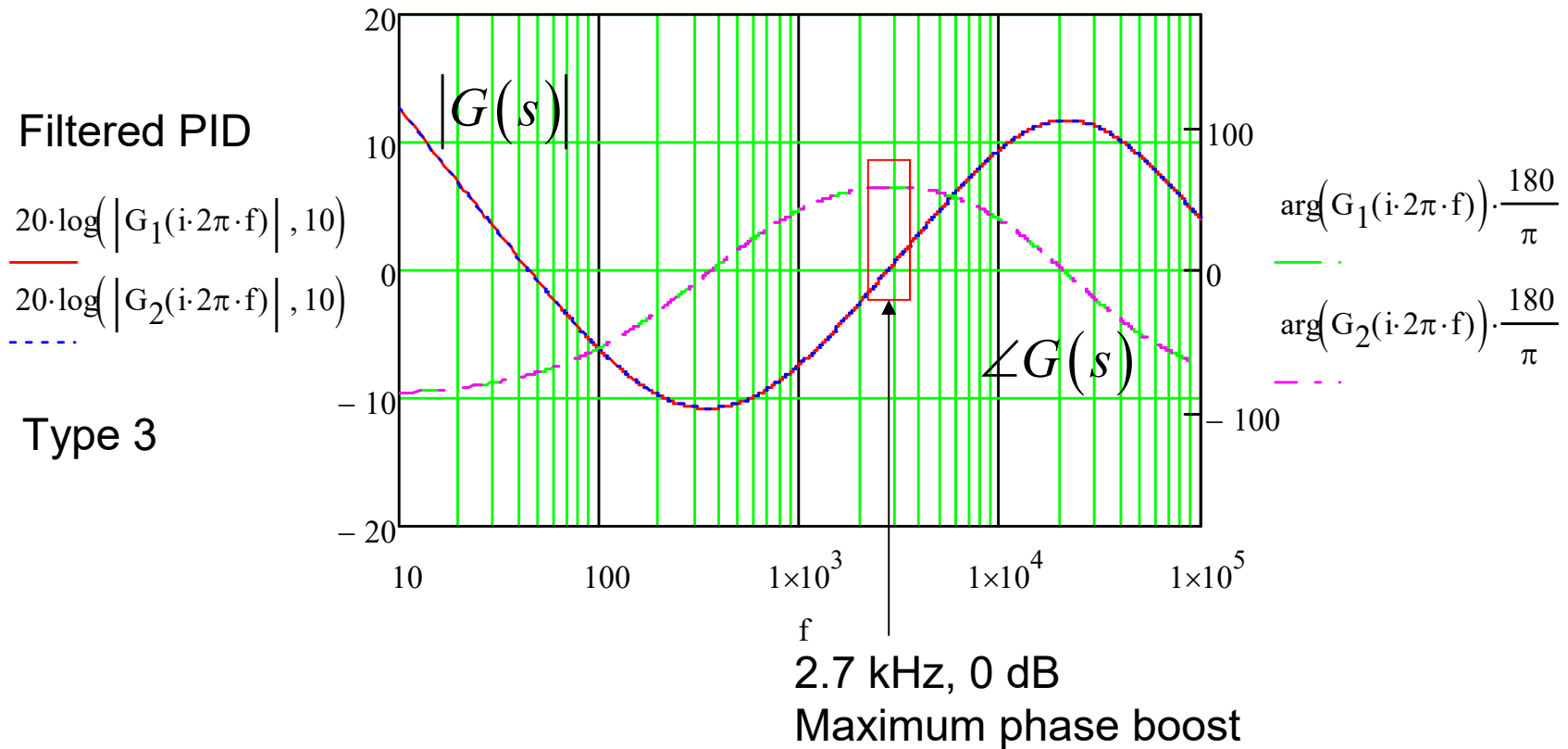

# Testing with SPICE

parameters

$$i=(1+fc^2/fp1^2)*(1+fc^2/fp2^2)$$

$$j=(1+fz1^2/fc^2)*(1+fc^2/fz2^2)$$

$$Wpi=sqrt(i/j)*G*fz1*2*pi$$

$$e=(Wp1-Wz1)*(Wp1-Wz2)$$

$$f=Wp1*Wz1+Wp1*Wz2-Wz1*Wz2$$

$$Td=e/(f*Wp1)$$

$$N=((Wp1^2)/f)-1$$

$$Ti=((Wz1+Wz2)/(Wz1*Wz2))-(1/Wp1)$$

$$kpf=(Wpi/Wz1)-(Wpi/Wp1)+(Wpi/Wz2)$$

parameters

$$fc=2740$$

$$Gfc=0$$

$$G=10^{(-Gfc/20)}$$

$$pi=3.14159$$

$$fz1=600$$

$$fz2=200$$

$$fp1=21.4k$$

$$fp2=21.4k$$

$$Wz1=2*pi*fz1$$

$$Wz2=2*pi*fz2$$


$$Wp1=2*pi*fp1$$

$$T_D = 1.929e-004$$

$$N = 2.594e+001$$

$$T_i = 1.054e-003$$


$$K_{PF} = 2.871e-001$$

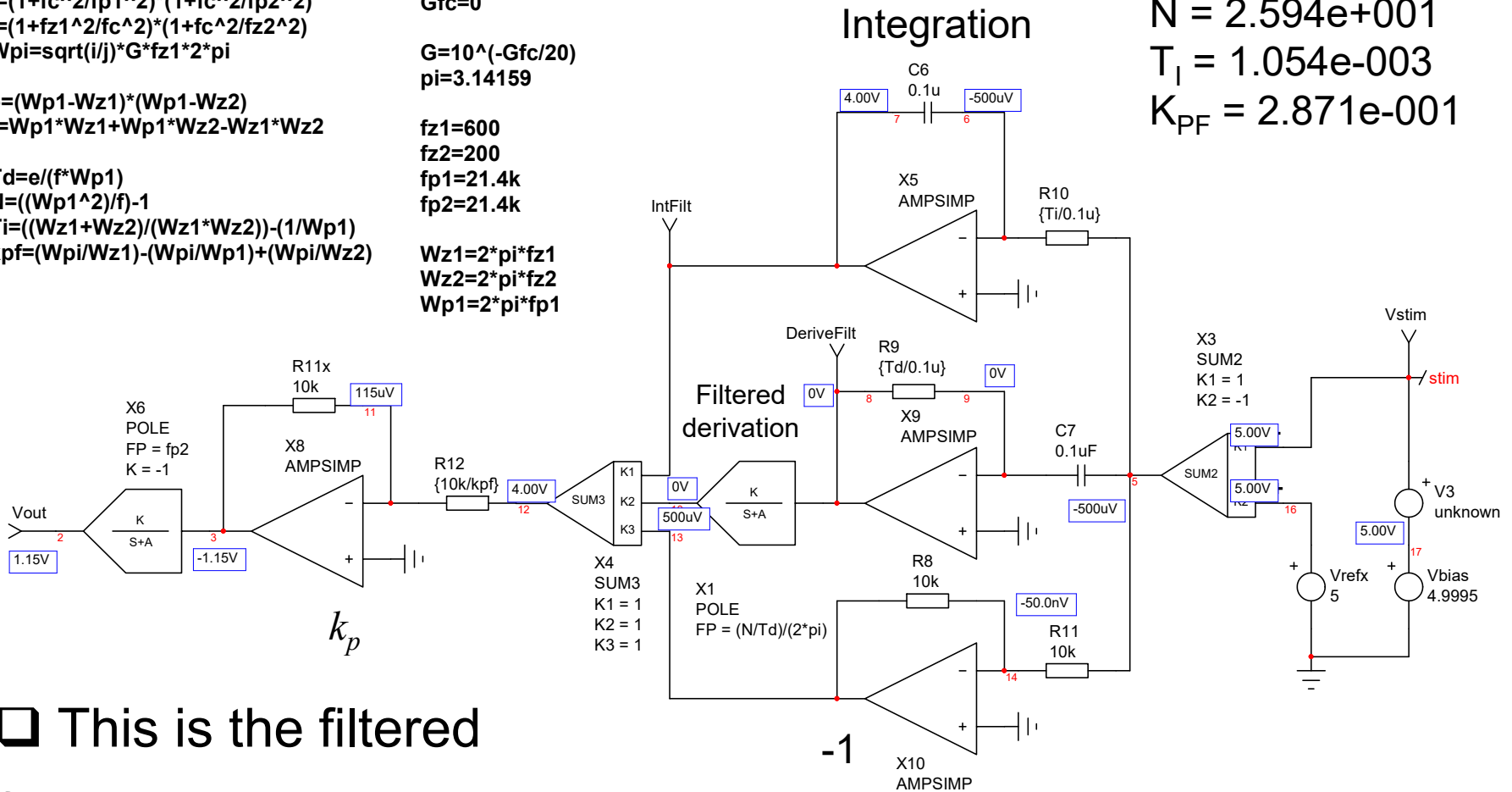

□ This is the filtered form implementation



# Testing with SPICE

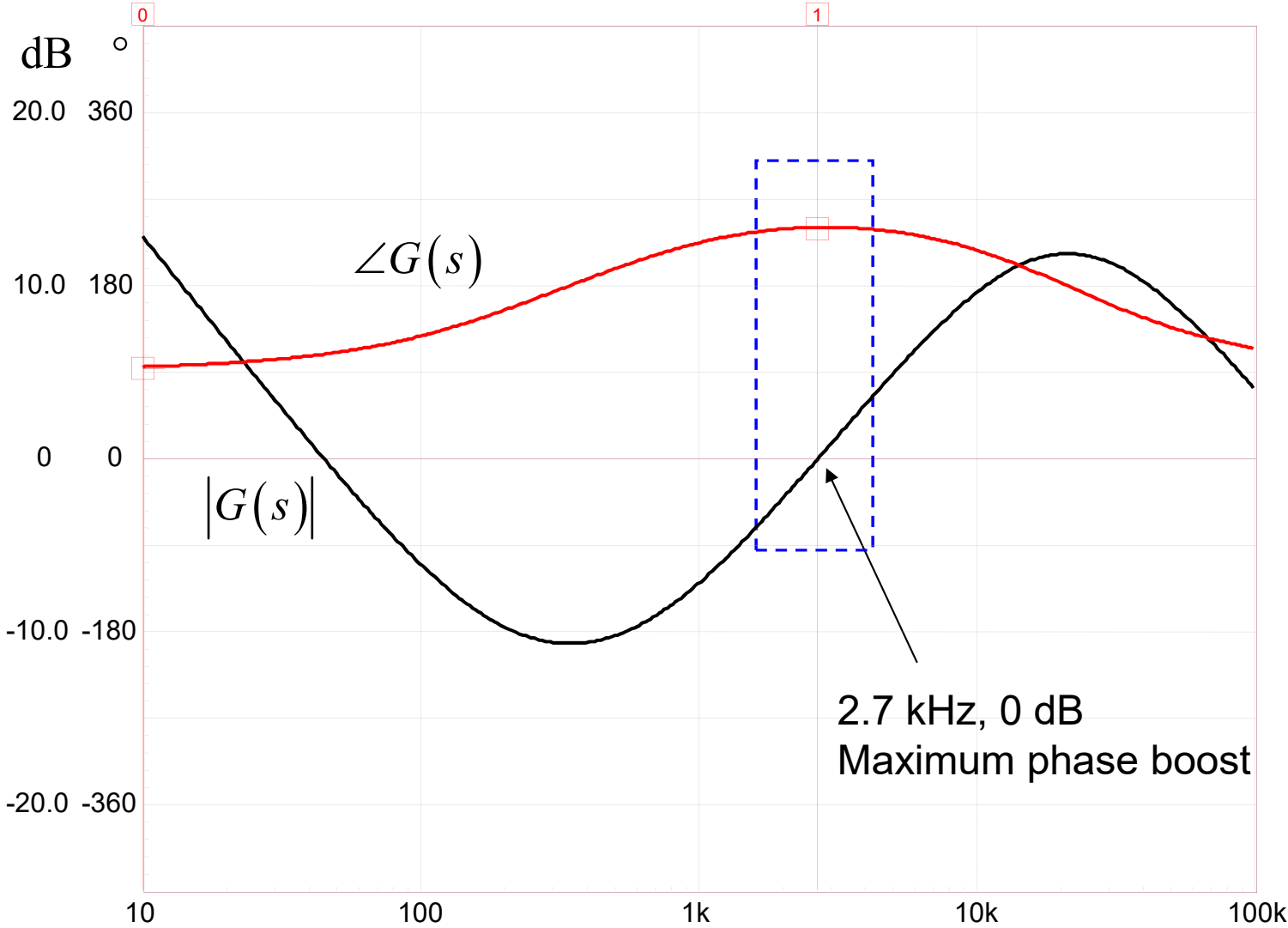


# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter**
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough


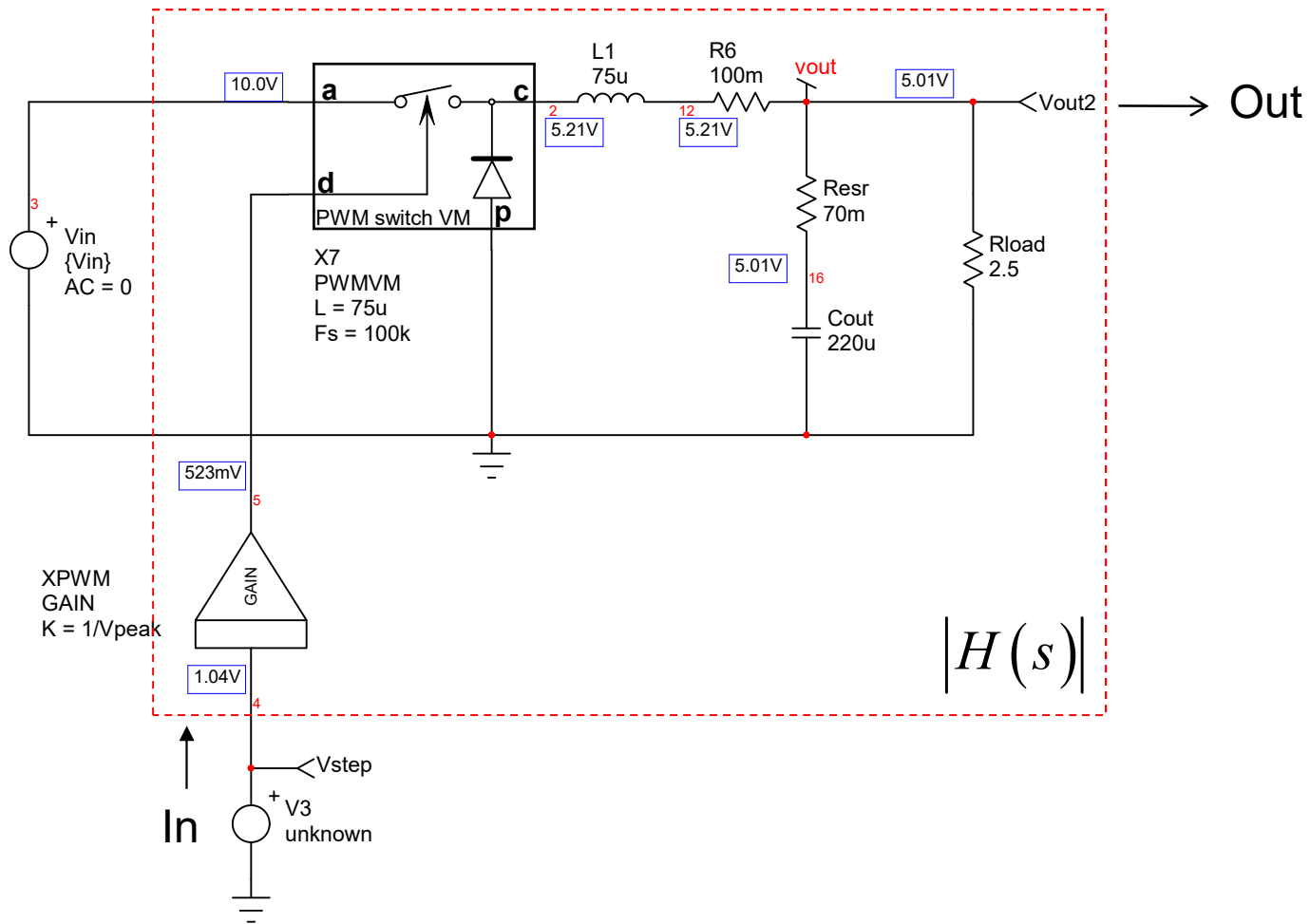
# Stabilizing a Buck with a PID

- We will use a PID to stabilize a voltage-mode Buck converter





The Plant


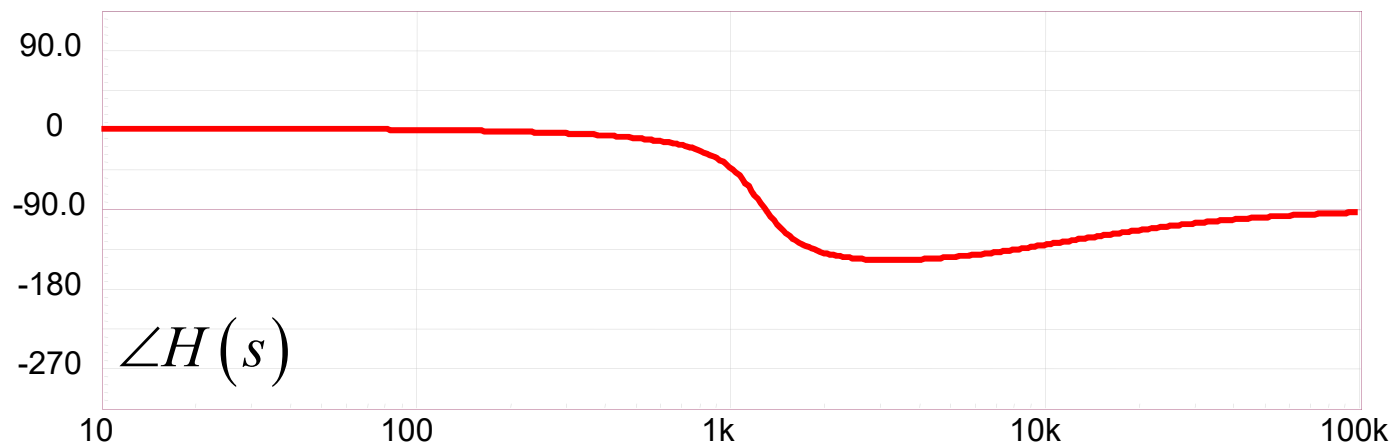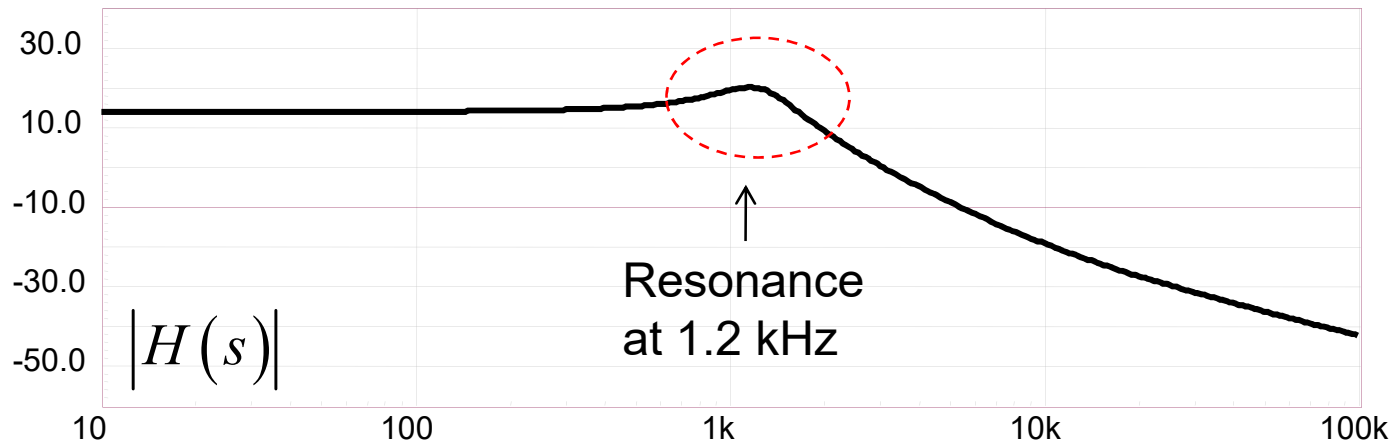
# Small-Signal Response of the Buck

- The transfer function shows a resonance at 1.2 kHz




# Compensating the Buck – Method 1

□ We will explore three different methods for compensation:

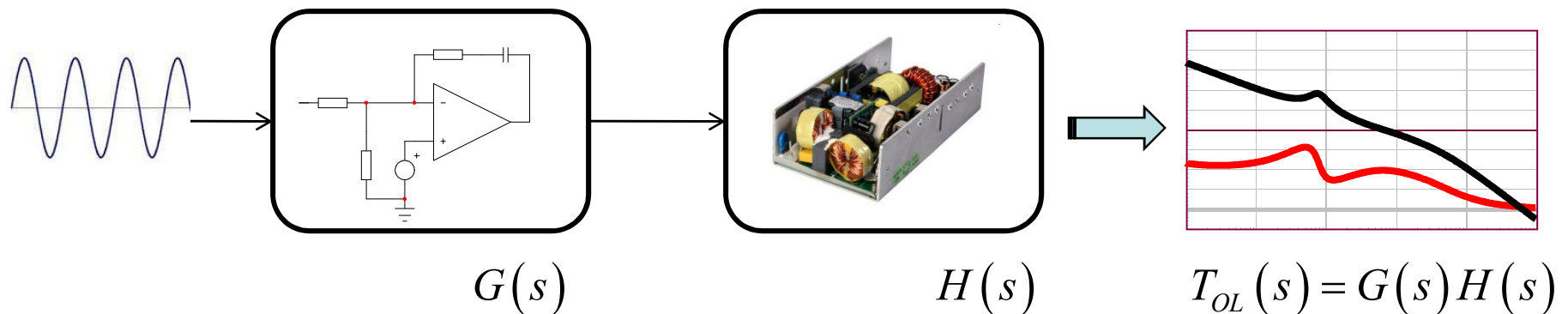1. Shape closed-loop gain to make it a 2<sup>nd</sup>-order system
2. Place poles and zeros to crossover at 10 kHz
3. Shape the output impedance only

□ Method 1 – derive the open-loop gain first




# Compensating the Buck – Method 1

- The loop gain expression is that of the PID and  $H(s)$

$$T_{OL}(s) = \frac{1 + s \left( \frac{\tau_d}{N} + \tau_i \right) + s^2 \left( \frac{\tau_d \tau_i}{N} + \tau_d \tau_i \right)}{s \frac{\tau_i}{k_p} \left( 1 + \frac{\tau_d}{N} s \right)} H_0 \frac{1 + s/\omega_{z_1}}{\left( \frac{s}{\omega_0} \right)^2 + \frac{s}{Q_0 \omega_0} + 1} N(s) D(s)$$

- To simplify the expression, we can neutralize  $D(s)$  by  $N(s)$

 Place a double zero at the double pole position:

$$1 + s \left( \frac{\tau_d}{N} + \tau_i \right) + s^2 \left( \frac{\tau_d \tau_i}{N} + \tau_d \tau_i \right) = \left( \frac{s}{\omega_0} \right)^2 + \frac{s}{Q_0 \omega_0} + 1$$



# Compensating the Buck – Method 1

□ The loop gain expression is now well simplified:

$$T_{OL}(s) = \frac{H_0 (1 + s/\omega_{z_1})}{s \frac{\tau_i}{k_p} \left(1 + \frac{\tau_d}{N} s\right)}$$


□ For a unity feedback control system, the closed-loop gain is:

$$T_{CL}(s) = \frac{\frac{H_0 (1 + s/\omega_{z_1})}{s \frac{\tau_i}{k_p} \left(1 + \frac{\tau_d}{N} s\right)}}{1 + \frac{H_0 (1 + s/\omega_{z_1})}{s \frac{\tau_i}{k_p} \left(1 + \frac{\tau_d}{N} s\right)}} = \frac{1 + s/\omega_{z_1}}{1 + s \left( \frac{1}{\omega_{z_1}} + \frac{\tau_i}{H_0 k_p} \right) + s^2 \left( \frac{\tau_d \tau_i}{N H_0 k_p} \right)}$$
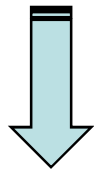
# Compensating the Buck – Method 1

- We want a damped second-order response:

$$1 + s \left( \frac{1}{\omega_{z_1}} + \frac{\tau_i}{H_0 k_p} \right) + s^2 \left( \frac{\tau_d \tau_i}{N H_0 k_p} \right) = 1 + \frac{s}{\omega_c Q_c} + \left( \frac{s}{\omega_c} \right)^2$$



Closed-loop denominator



Second-order canonical form

- Choose a crossover frequency and a quality factor:

$$Q_c = 0.5 \quad \text{Non-ringing response} \quad \omega_c = 27.3 \text{ rd/s} \rightarrow 10 \text{ kHz}$$



# Compensating the Buck – Method 1

□ Four unknowns, four equations:

$$\frac{1}{\omega_{z_1}} + \frac{T_i}{H_0 k_p} = \frac{1}{\omega_c Q_c} \quad \frac{T_d T_i}{N H_0 k_p} = \frac{1}{\omega_c^2} \quad \frac{T_d}{N} + T_i = \frac{1}{\omega_0 Q_0} \quad \frac{T_d T_i}{N_1} + T_d T_i = \frac{1}{\omega_0^2}$$

$$T_d = \frac{Q_0 Q_c^2 \omega_{z_1}^2 \omega_0^2 + Q_c^2 \omega_{z_1} \omega_0 \omega_c^2 + Q_0 Q_c^2 \omega_c^4 - Q_c \omega_{z_1}^2 \omega_0 \omega_c - 2 Q_0 Q_c \omega_{z_1} \omega_c^3 + Q_0 \omega_{z_1}^2 \omega_c^2}{\omega_0 \omega_c (Q_c \omega_c - \omega_{z_1}) (Q_c \omega_c^2 - \omega_{z_1} \omega_c + Q_0 Q_c \omega_{z_1} \omega_0)} = 1.116 \text{ ms}$$

$$N = -\frac{Q_0 Q_c^2 \omega_{z_1}^2 \omega_0^2 + Q_c^2 \omega_{z_1} \omega_0 \omega_c^2 + Q_0 Q_c^2 \omega_c^4 - Q_c \omega_{z_1}^2 \omega_0 \omega_c - 2 Q_0 Q_c \omega_{z_1} \omega_c^3 + Q_0 \omega_{z_1}^2 \omega_c^2}{\omega_0 Q_c \omega_{z_1} (Q_c \omega_c^2 - \omega_{z_1} \omega_c + Q_0 Q_c \omega_{z_1} \omega_0)} = 72.4$$


$$T_i = -\frac{Q_c \omega_c^2 - \omega_{z_1} \omega_c + Q_0 Q_c \omega_{z_1} \omega_0}{Q \omega_{z_1} \omega_0 \omega_c - Q_0 Q_c \omega_0 \omega_c^2} = 14.6 \mu\text{s} \quad k_p = -\frac{Q_c \omega_{z_1} (Q_c \omega_c^2 - \omega_{z_1} \omega_c + Q_c Q_0 \omega_{z_1} \omega_0)}{H_0 Q_0 \omega_0 (\omega_{z_1} - Q_c \omega_c)^2} = 0.178$$




# Compensating the Buck – Method 1

□ We can now compute our transfer functions in Mathcad®

Compensator  
response  $G(s)$

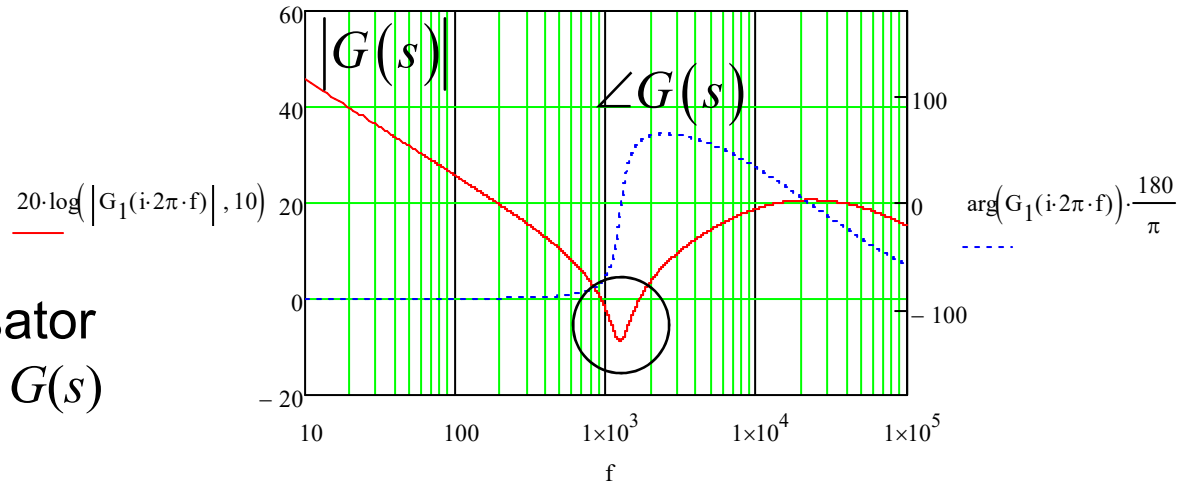


Open-loop gain  
response  $T_{OL}(s)$

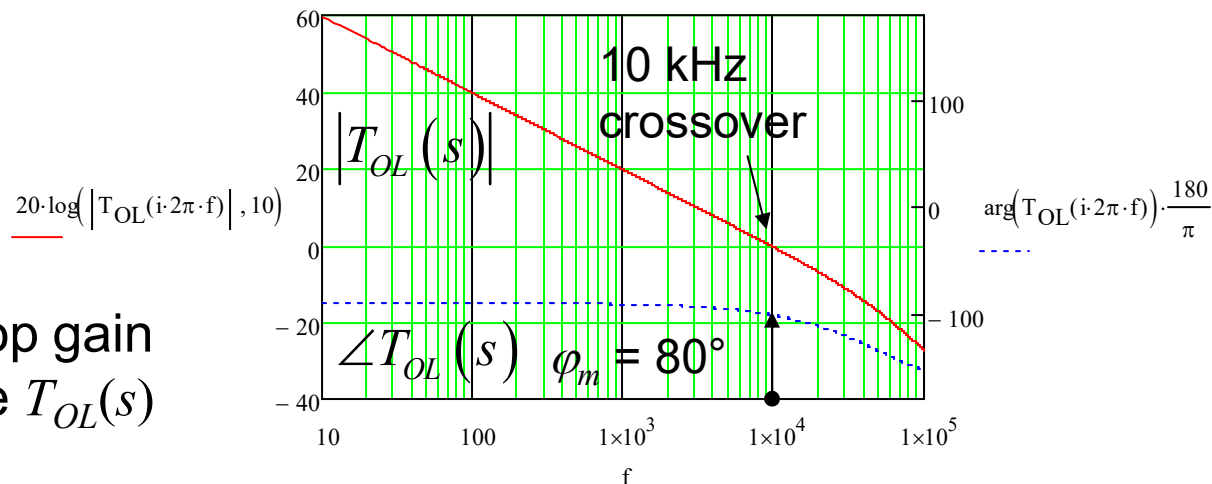
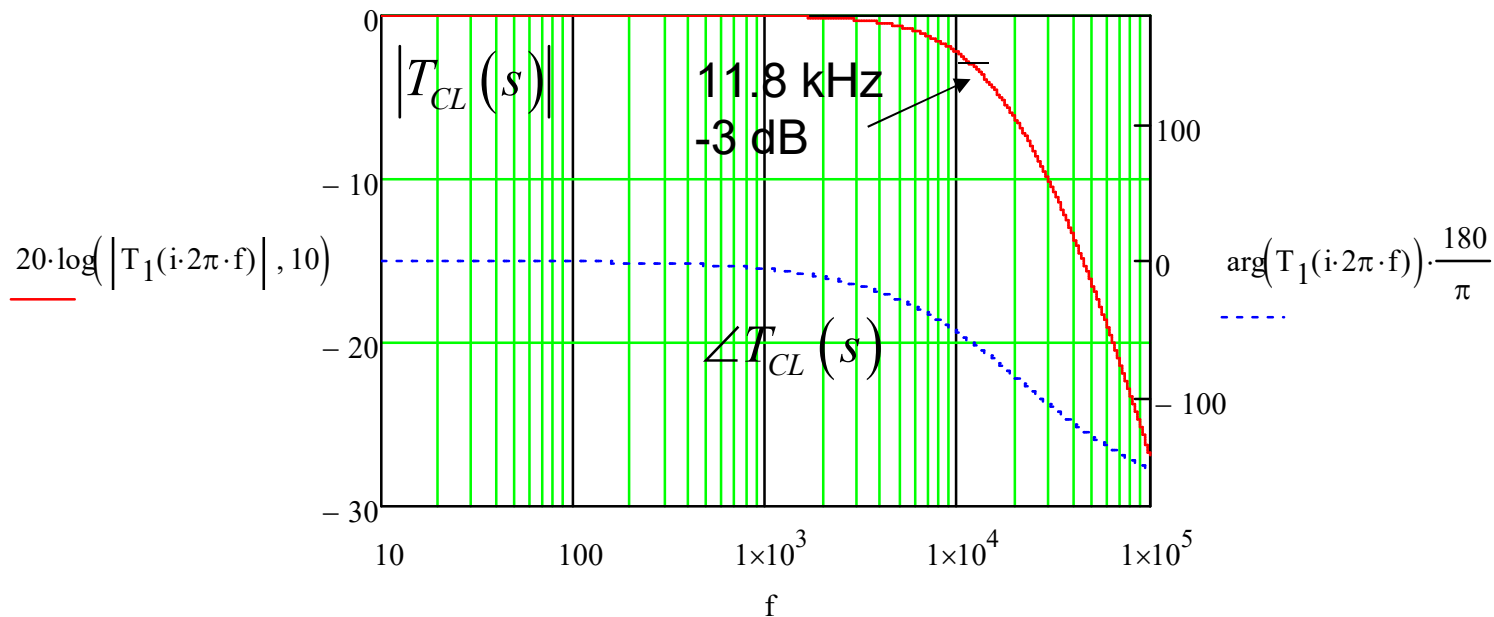
# Compensating the Buck – Method 1

- The closed-loop system is perfectly compensated



$$T_{CL}(s) = \frac{T_{OL}(s)}{1 + T_{OL}(s)}$$

# Compensating the Buck – Method 1

□ We can test the compensation with SPICE

parameters

$f_c = 10k$   
 $G_{fc} = -20$   
 $V_{in} = 10$   
 $V_{peak} = 2$

$G = 10^{-(G_{fc}/20)}$   
 $\pi = 3.14159$

$f_{z1} = 1.2k$   
 $f_{z2} = 1.2k$   
 $f_{p1} = 10k$   
 $f_{p2} = 50k$


$W_{z1} = 2 * \pi * f_{z1}$   
 $W_{z2} = 2 * \pi * f_{z2}$   
 $W_{p1} = 2 * \pi * f_{p1}$

$i = (1 + f_c^2 / f_{p1}^2) * (1 + f_c^2 / f_{p2}^2)$   
 $j = (1 + f_{z1}^2 / f_c^2) * (1 + f_c^2 / f_{z2}^2)$   
 $W_{pi} = \sqrt{(i/j)} * G * f_{z1} * 2 * \pi$

$e = (W_{p1} - W_{z1}) * (W_{p1} - W_{z2})$   
 $f = W_{p1} * W_{z1} + W_{p1} * W_{z2} - W_{z1} * W_{z2}$


$T_d = e / (f * W_{p1})$   
 $N = ((W_{p1}^2) / f) - 1$   
 $T_i = ((W_{z1} + W_{z2}) / (W_{z1} * W_{z2})) - (1 / W_{p1})$   
 $k_{pf} = (W_{pi} / W_{z1}) - (W_{pi} / W_{p1}) + (W_{pi} / W_{z2})$

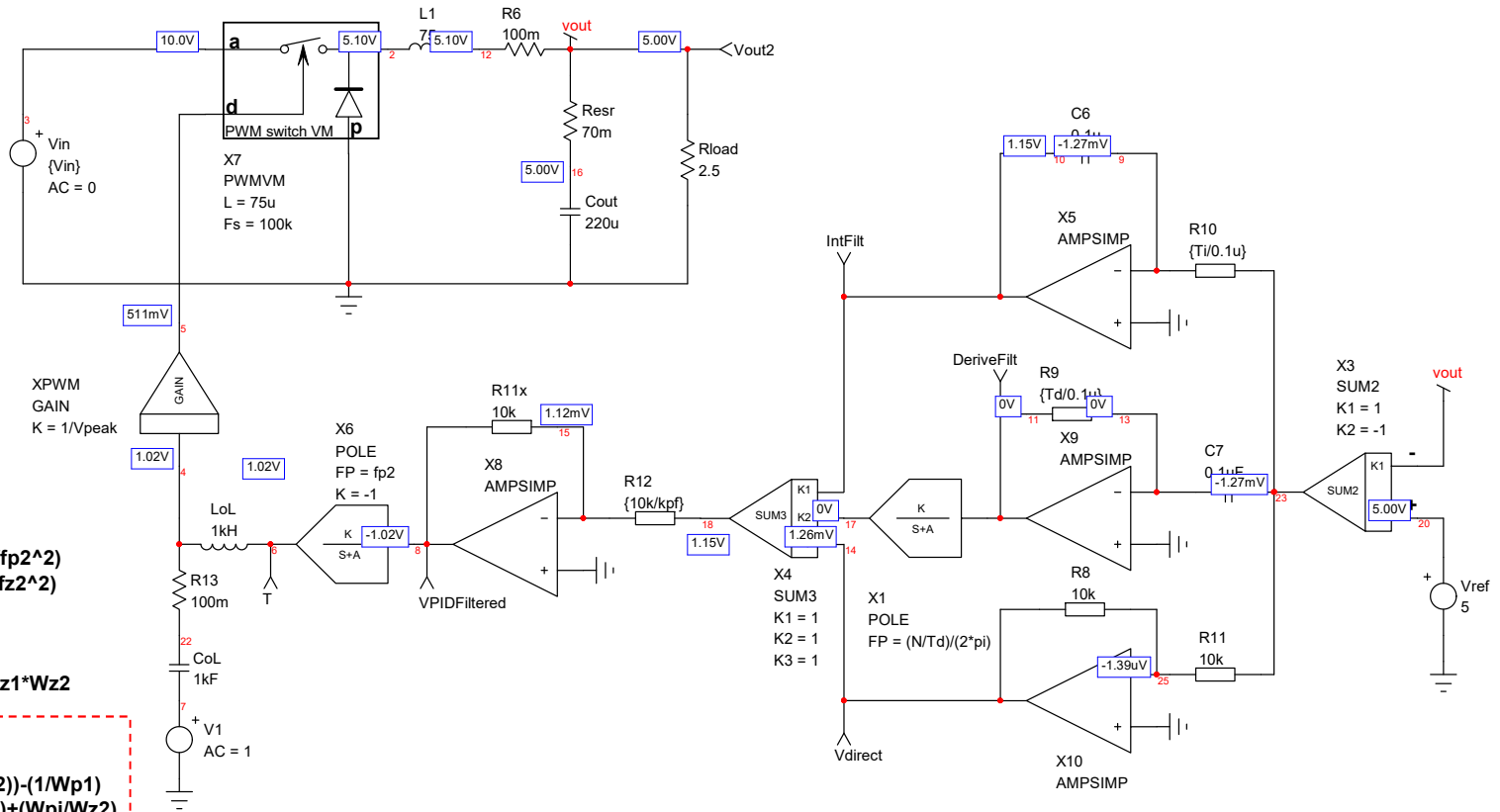$T_{dd} = 1.116m$   
 $T_{ii} = 14.6\mu$   
 $k_{pff} = 0.178$   
 $NN = 72.4$


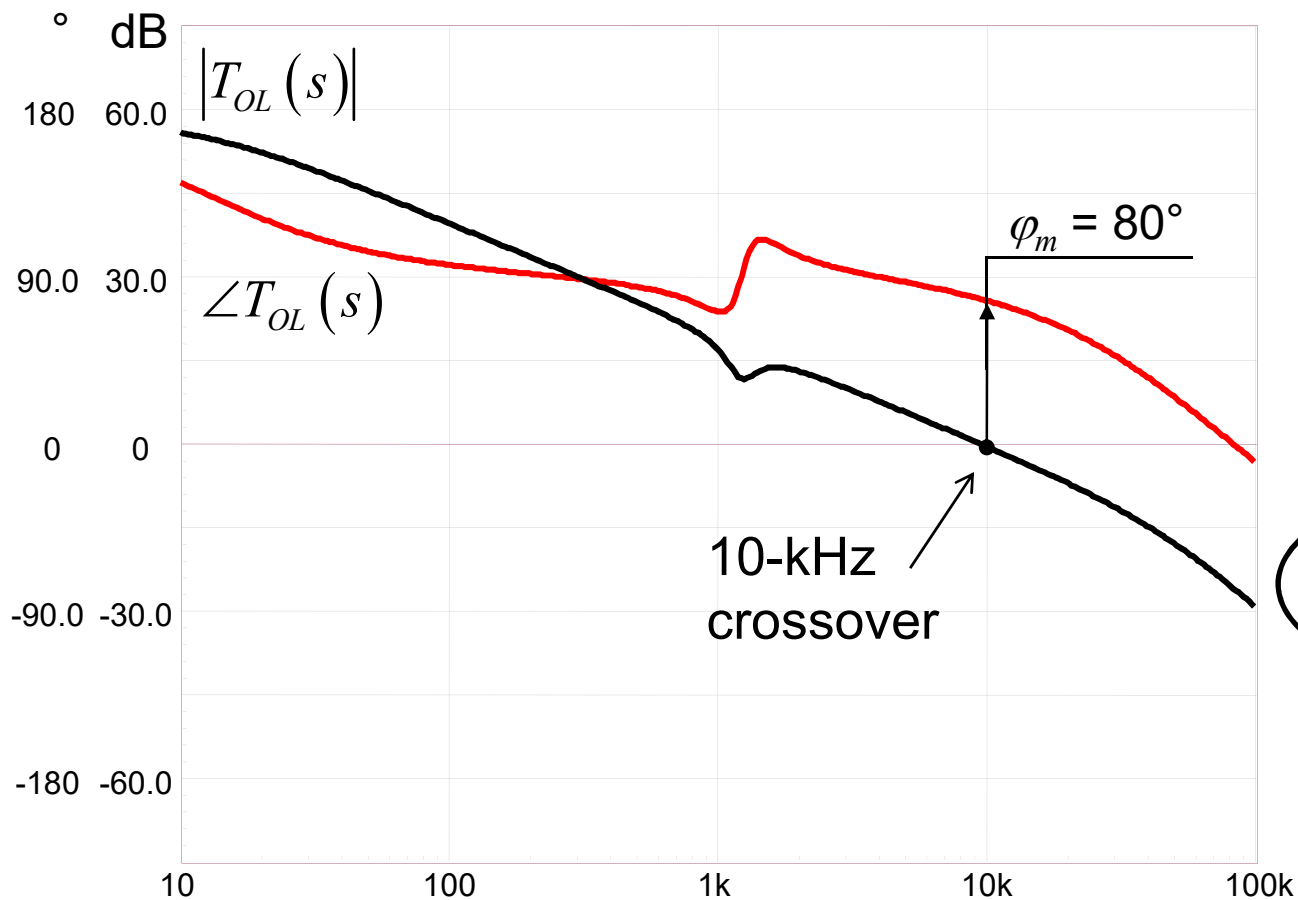
# Compensating the Buck – Method 1

- We can test the compensation with SPICE




Perfect compensation dude!


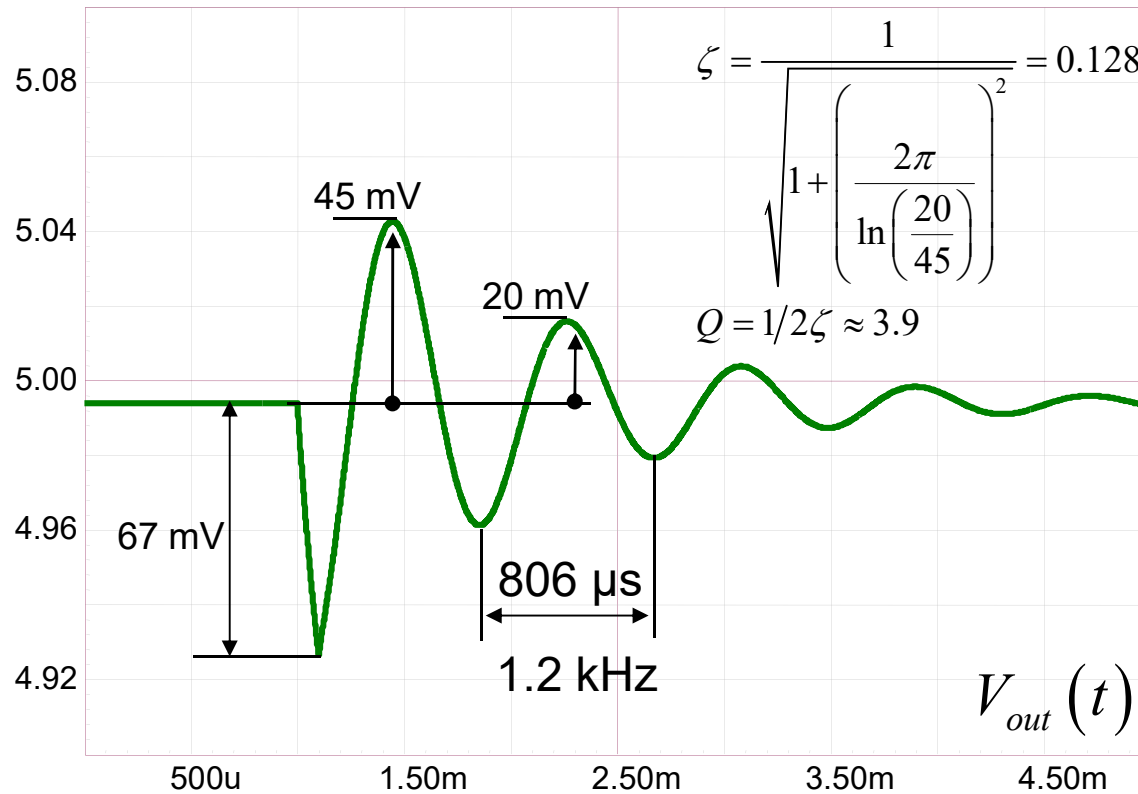
# Compensating the Buck – Method 1

❑ We have a stable but oscillatory response!



Wasn't it supposed to be perfect, uh?




$$\Delta I_{out} = 1 \text{ A in } 100 \mu\text{s}$$






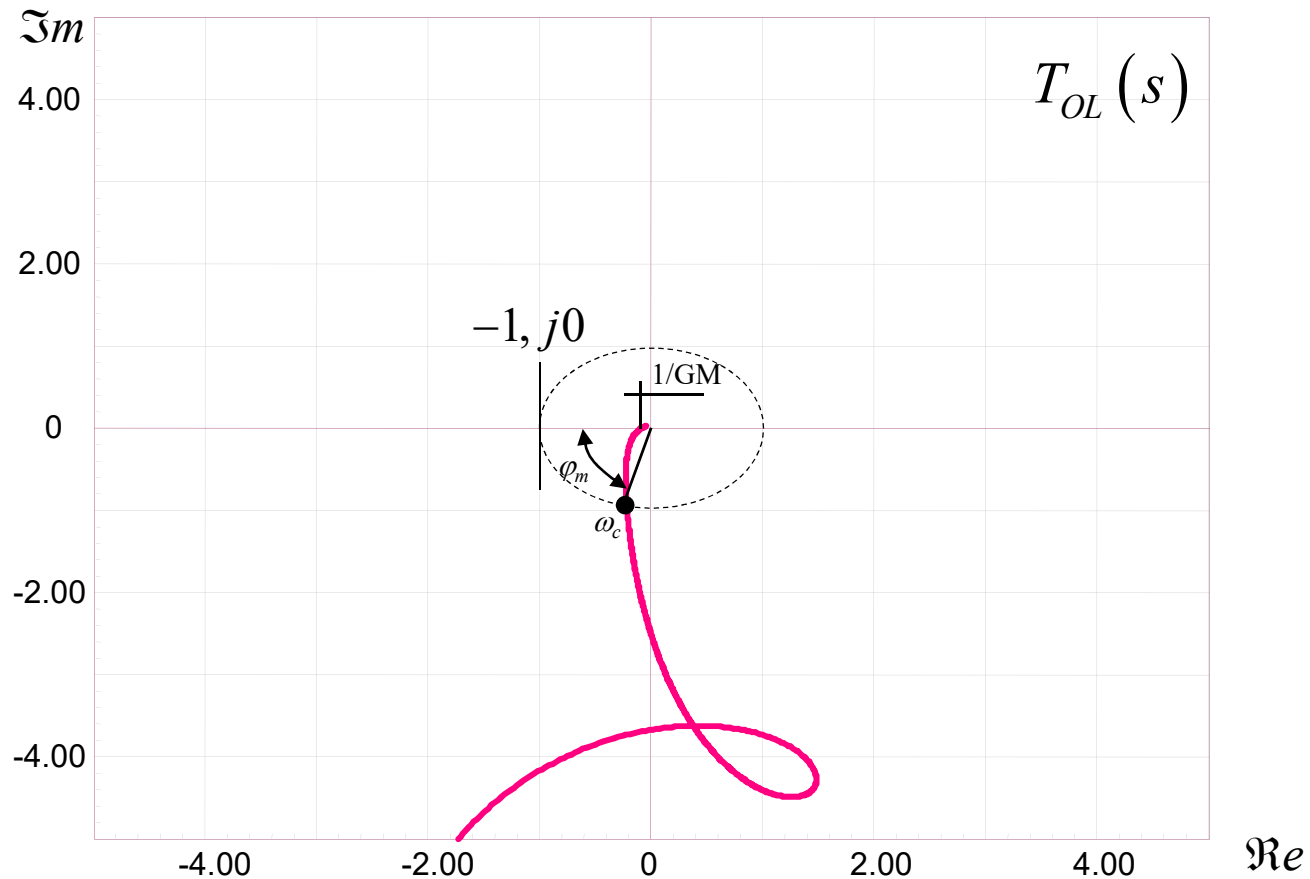
# Compensating the Buck – Method 1

- ❑ Bode or Nyquist do not predict the oscillatory response



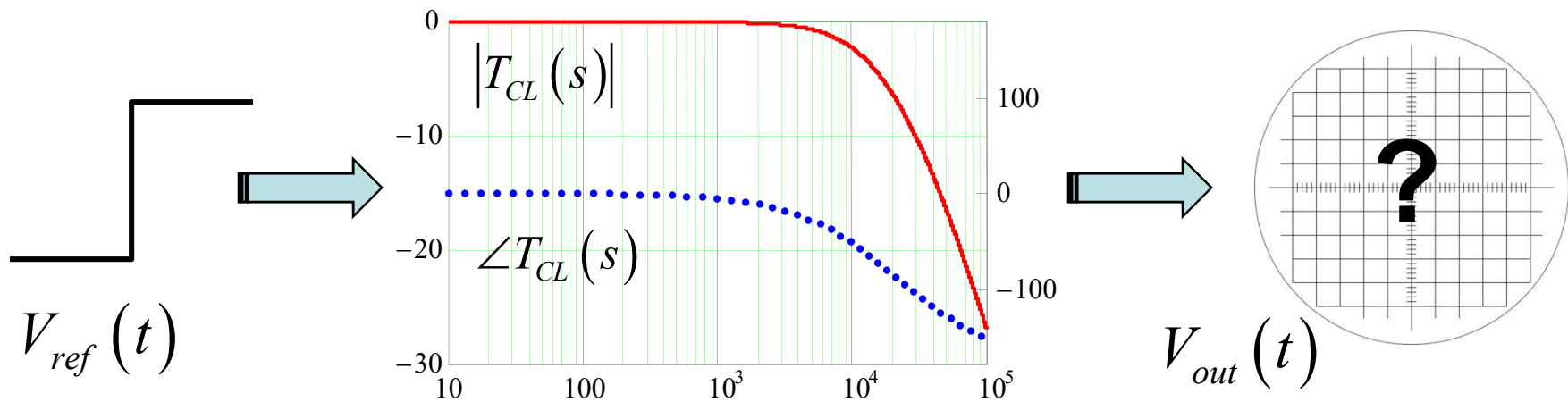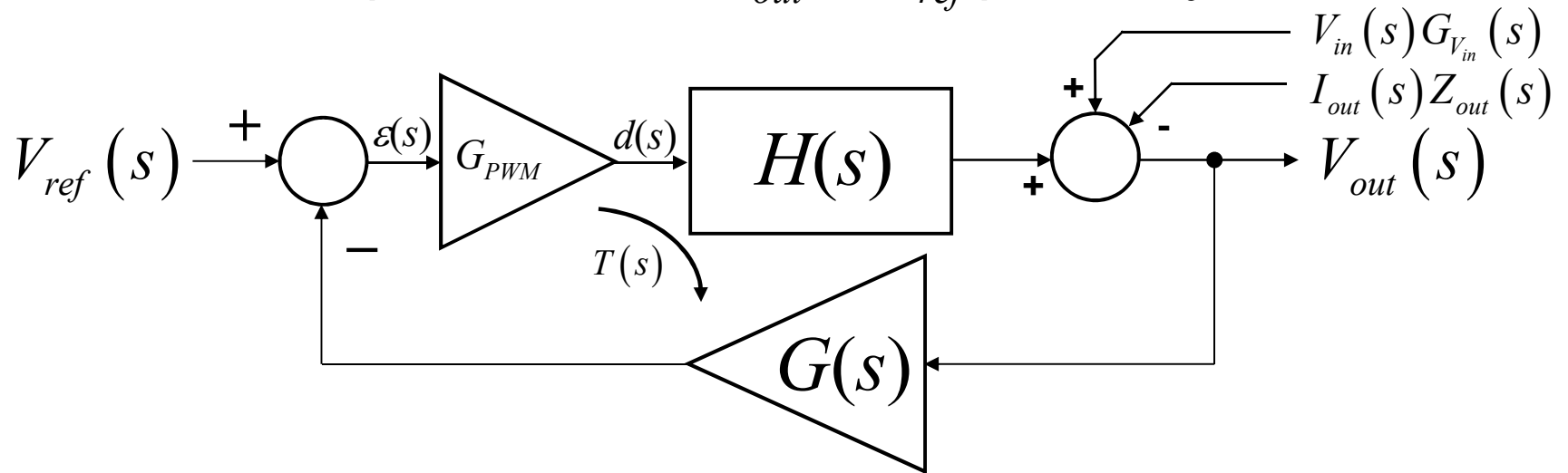
# Compensating the Buck – Method 1

□ We compensated the  $V_{out}$  to  $V_{ref}$  path only!



# Compensating the Buck – Method 1

- ❑ The output response is as expected

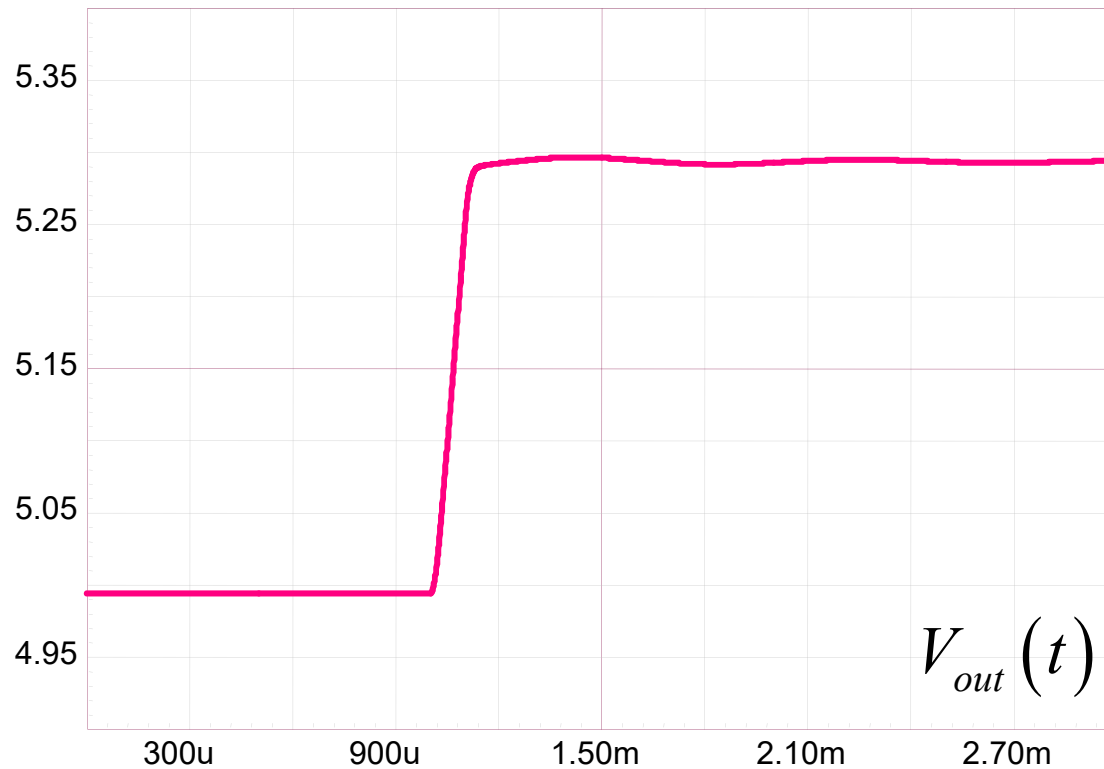

- ❑ Where is the issue coming from then?


# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance**
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough


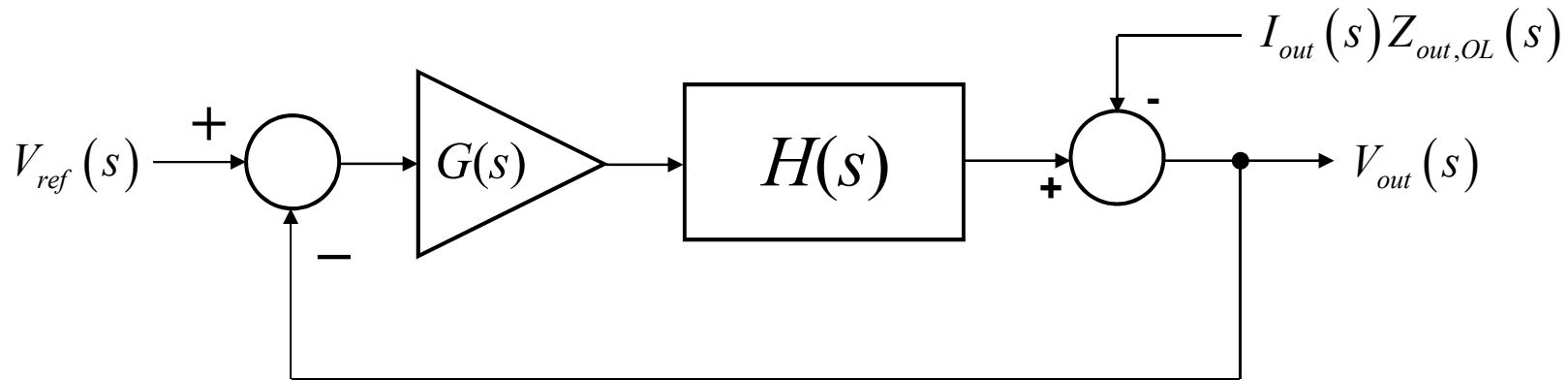
# Compensating the Buck – Method 1


- In reality,  $V_{ref}$  is fixed: "we have a regulator, stupid!"



- Because the system is linear, superposition applies

$$V_{out1}(s) = V_{ref}(s) \frac{T_{OL}(s)}{1 + T_{OL}(s)} \quad V_{out2}(s) = I_{out}(s) Z_{out,OL}(s) - V_{out}(s) T_{OL}(s)$$

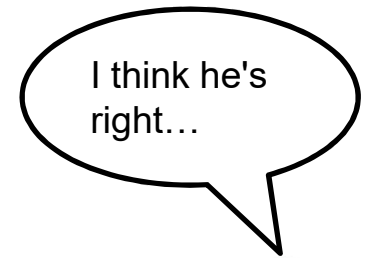
$$V_{out}(s) = V_{out1}(s) + V_{out2}(s) = V_{ref}(s) \frac{T_{OL}(s)}{1 + T_{OL}(s)} - I_{out}(s) \frac{Z_{out,OL}(s)}{1 + T_{OL}(s)} Z_{out,CL}$$




- During the load step,  $\hat{v}_{ref} = 0$ :  $Z_{out}$  fixes the response!
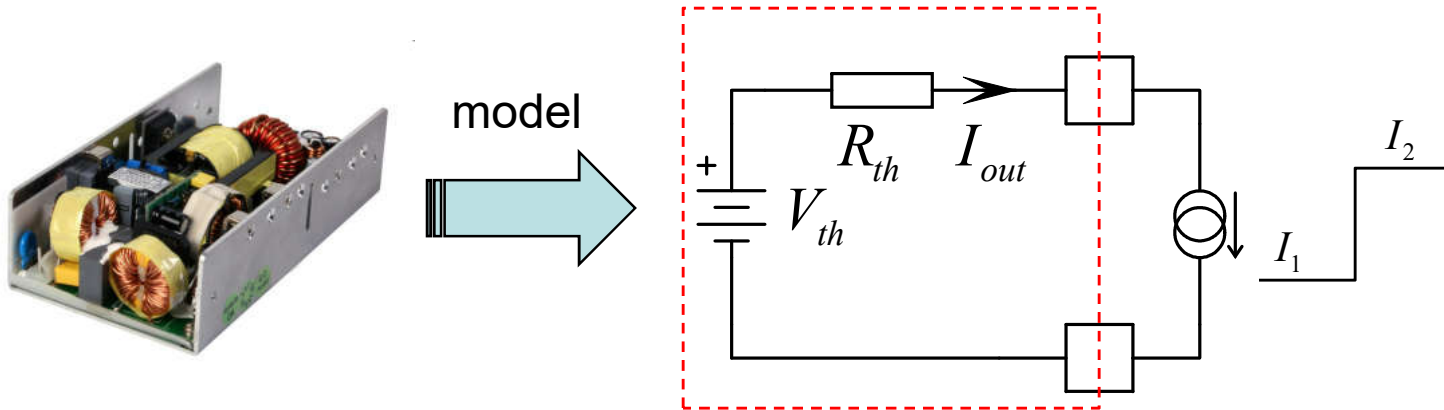
# Compensating the Buck – Method 1

- What matters is the output impedance  $Z_{out,CL}$



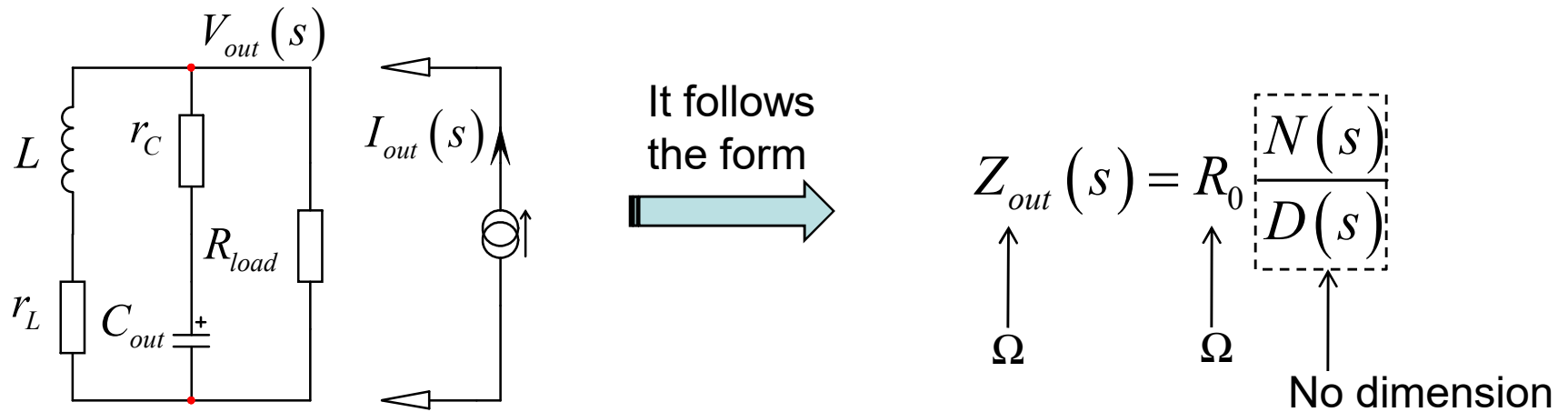- What is the output impedance of a buck converter?




# Compensating the Buck – Method 1

- The output impedance is a transfer function


$$Z_{out}(s) = \frac{V_{out}(s)}{I_{out}(s)}$$

← response  
 ← excitation

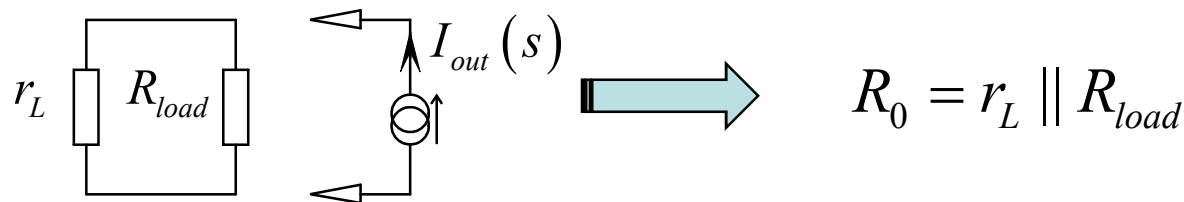- Let's find the term  $R_0$  in dc: open caps, short inductors



- The zeros cancel the response

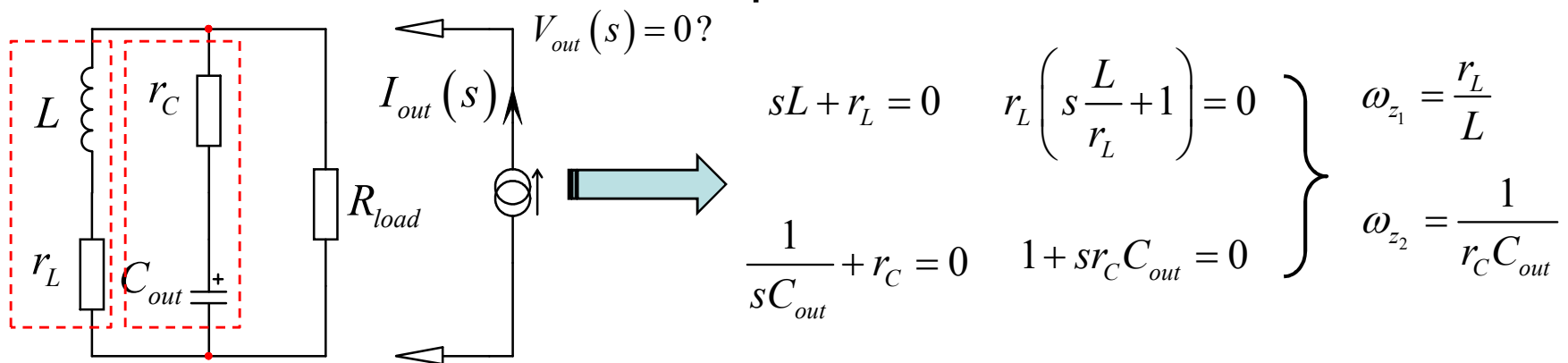

# Compensating the Buck – Method 1

- ❑ The denominator is solely dependent on the structure
- It is independent from the excitation: set it to zero!
- ❑ There are two storage elements: this is a 2<sup>nd</sup>-order network

➡  $D(s) = 1 + a_1s + a_2s^2 = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2$

- ❑  $D$  must be dimensionless thus:  $a_1 \equiv (\text{Hz})^{-1}$   $a_2 \equiv (\text{Hz})^{-2}$


- The two possible terms for  $a_1$  are  $\tau_1 + \tau_2$
  - The two possible terms for  $a_2$  are  $\tau_1\tau'_2$   
 $\tau'_1\tau_2$
- }  $\tau = \frac{L}{R}$  or  $\tau = RC$




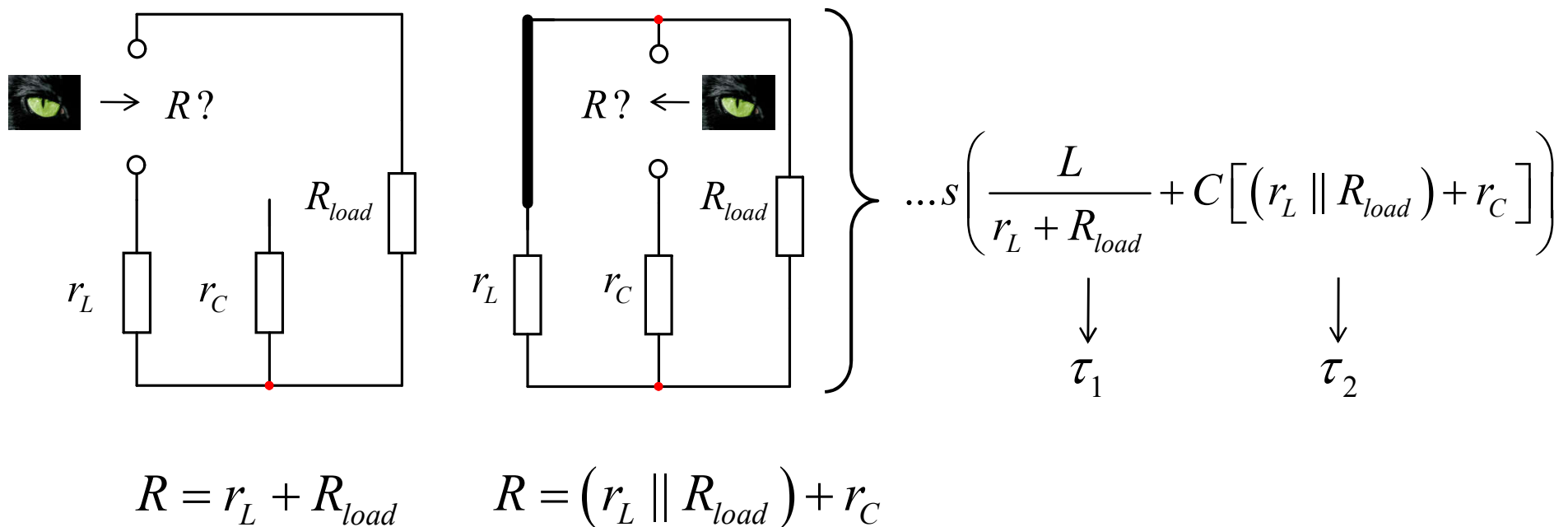
# Compensating the Buck – Method 1


- For  $a_1$  look at the resistance  $R$  driving  $L$  and  $C$
- Look at the driving impedance at  $L$  while  $C$  is in its dc state
- Look at the driving impedance at  $C$  while  $L$  is in its dc state


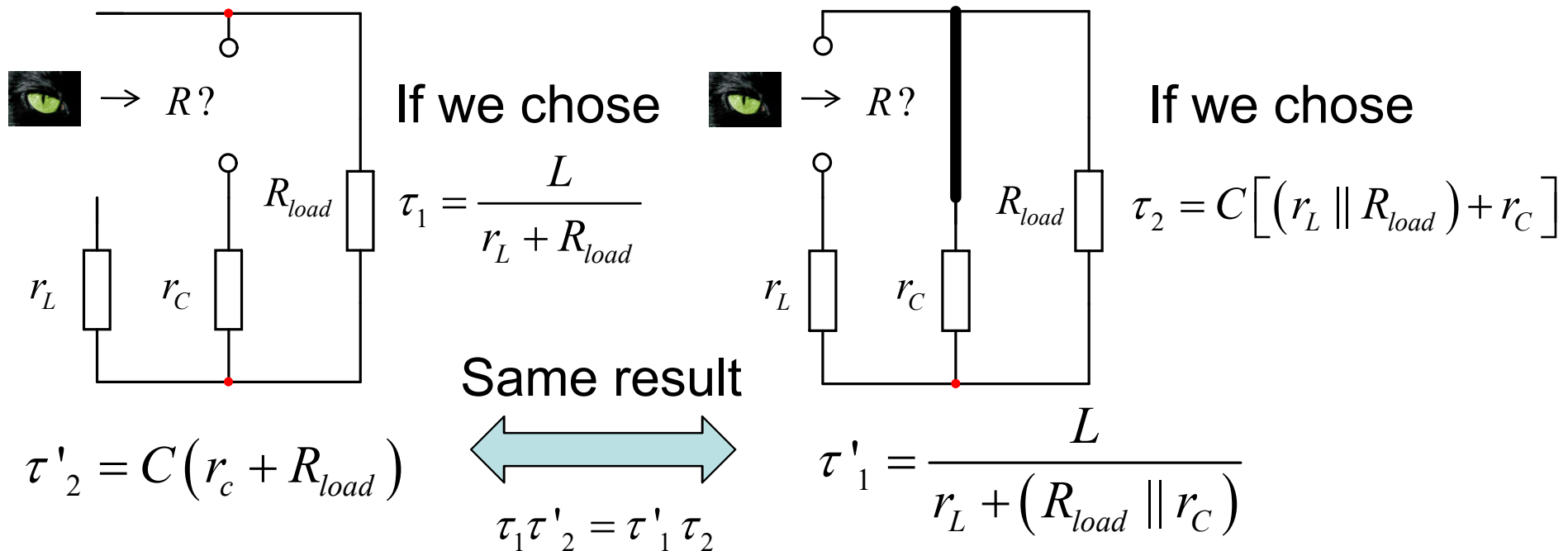
# Compensating the Buck – Method 1

- ❑ how  $\tau_1$  (involving  $L$ ) combines with  $\tau'_2$  (involving  $C$ )? }  $a_2$
- ❑ how  $\tau_2$  (involving  $C$ ) combines with  $\tau'_1$  (involving  $L$ )? }

- Look at the driving impedance at  $C$  while  $L$  is in its HF state
- Look at the driving impedance at  $L$  while  $C$  is in its HF state



# Compensating the Buck – Method 1

□ We have our denominator!

$$D(s) = 1 + s \left( \frac{L}{r_L + R_{load}} + C [(r_L \parallel R_{load}) + r_C] \right) + s^2 \left( LC \frac{r_C + R_{load}}{r_L + R_{load}} \right)$$

□ The complete transfer function is now:

$$Z_{out}(s) = (r_L \parallel R_{load}) \frac{\left( 1 + s \frac{L}{r_L} \right) (1 + sr_C C_{out})}{1 + s \left( \frac{L}{r_L + R_{load}} + C [(r_L \parallel R_{load}) + r_C] \right) + s^2 \left( LC \frac{r_C + R_{load}}{r_L + R_{load}} \right)}$$

See "Fast Analytical Techniques" from Vatché Vorperian, Cambridge Press



# Compensating the Buck – Method 1

□ It can be put under the following form:

$$Z_{out}(s) = R_0 \frac{(1 + s/\omega_{z_1})(1 + s/\omega_{z_2})}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

□ Where we can identify the terms:


$$R_0 = r_L \parallel R_{load} \quad \omega_{z_1} = \frac{r_L}{L} \quad \omega_{z_2} = \frac{1}{r_C C_{out}}$$

$$\omega_0 = \frac{1}{\sqrt{LC_{out}}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}} \quad Q = \frac{LC_{out} \omega_0 (r_C + R_{load})}{L + C_{out} (r_L r_C + r_L R_{load} + r_C R_{load})}$$


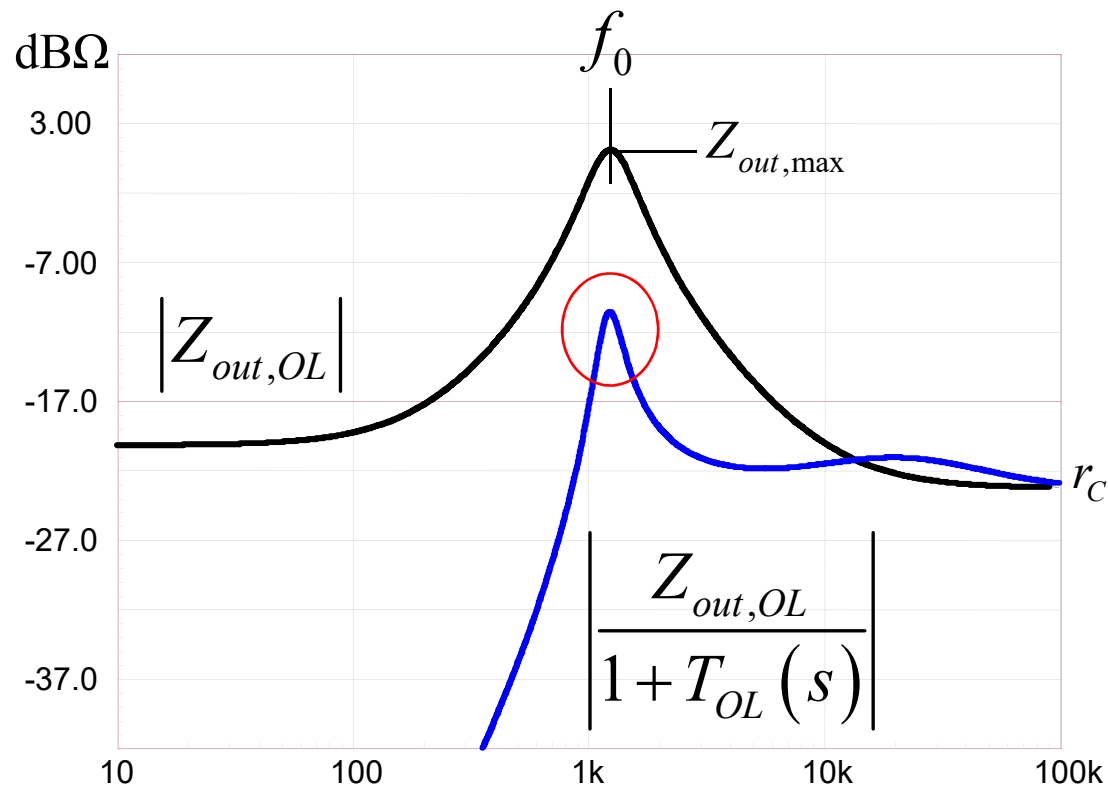
# Compensating the Buck – Method 1


- ❑ If we now plot the output impedance, we see peaking
- ❑ For an non-oscillatory response, the peaking must be damped!



- ❑ It's not, this is where the problem comes from
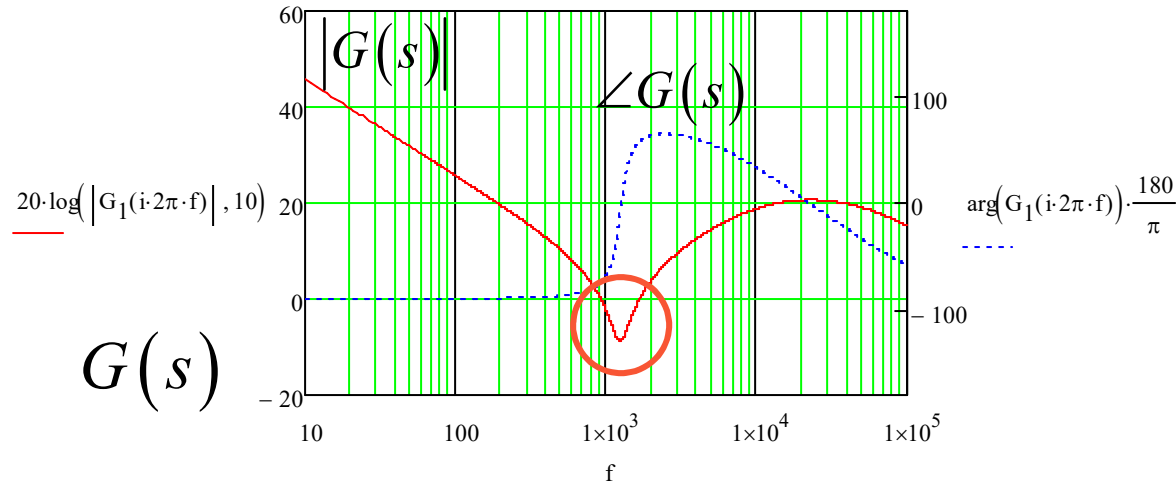
# Compensating the Buck – Method 1

- We organized a gain deficit right at the resonance!



- To tame the peaking, we must have gain at  $f_0$
- How much do we peak at  $f_0$ ?

$$|Z_{out,max}(\omega_0)| = R_0 \frac{\sqrt{1 + (\omega_0/\omega_{z_1})^2} \sqrt{1 + (\omega_0/\omega_{z_2})^2}}{\sqrt{\left(1 - \omega_0^2 \left( LC_{out} \frac{r_C + R_{load}}{r_L + R_{load}} \right)\right)^2 + \left(\omega_0 \left( \frac{L}{r_L + R_{load}} + C_{out} (r_C + r_L \parallel R_{load}) \right)\right)^2}}$$

# Compensating the Buck – Method 1

- ❑ We can impose a magnitude to stay below  $r_C$
- evaluate the needed gain to fulfill this goal:

$$\left| \frac{Z_{out,max}(f_0)}{1 + T_{OL}(f_0)} \right| \leq r_C \quad \xrightarrow{\approx} \quad \frac{|Z_{out,max}(f_0)|}{|T_{OL}(f_0)|} \leq r_C \quad \Rightarrow \quad |T_{OL}(f_0)| \geq \frac{|Z_{out,max}(f_0)|}{r_C}$$

Closed-loop  
output impedance

- ❑ Applying the numerical values of the buck:


$$|T_{OL}(f_0)| \geq \frac{1.12}{70m} \geq 16 \text{ or } 24 \text{ dB}$$

- ❑ Is this enough to obtain a ringing-free response?


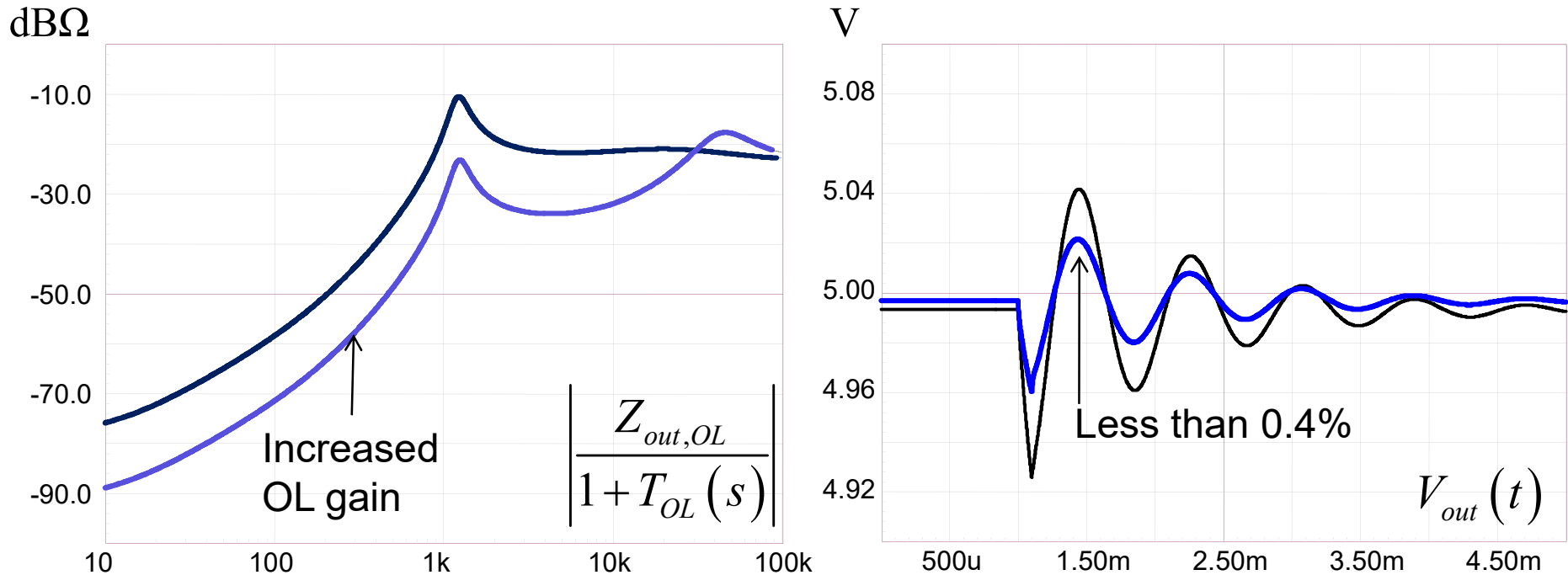
# Compensating the Buck – Method 1

- ❑ No, ringing is reduced but not eliminated




- ❑ The peaking in the output impedance is still there!
- ❑ The notched zeros are the cause for the gain dip at  $f_0$
- We must find a different compensation method


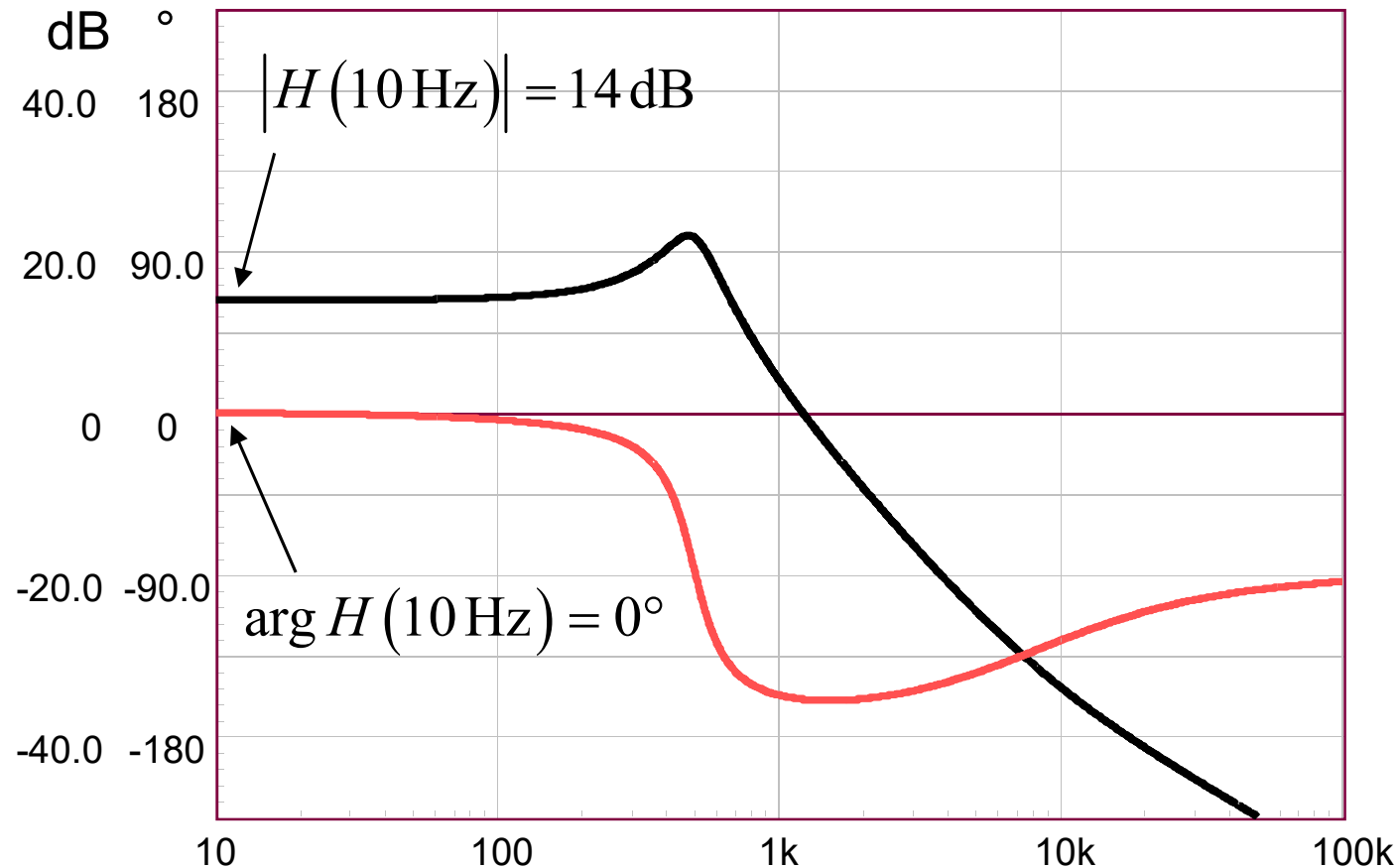
## Another (Bad) Example

- ❑ Can we crossover at 10 Hz according to this plot?



- ❑ We have no phase lag at 10 Hz, a type 1 could do?

# Rolling-off the BW at Low Frequencies


- ❑ SPICE gives us the open-loop gain snapshot

parameters

Vout=5V  
Rupper=10k  
fc=10  
Gfc=14


$G=10^{(-Gfc/20)}$   
 $\pi=3.14159$

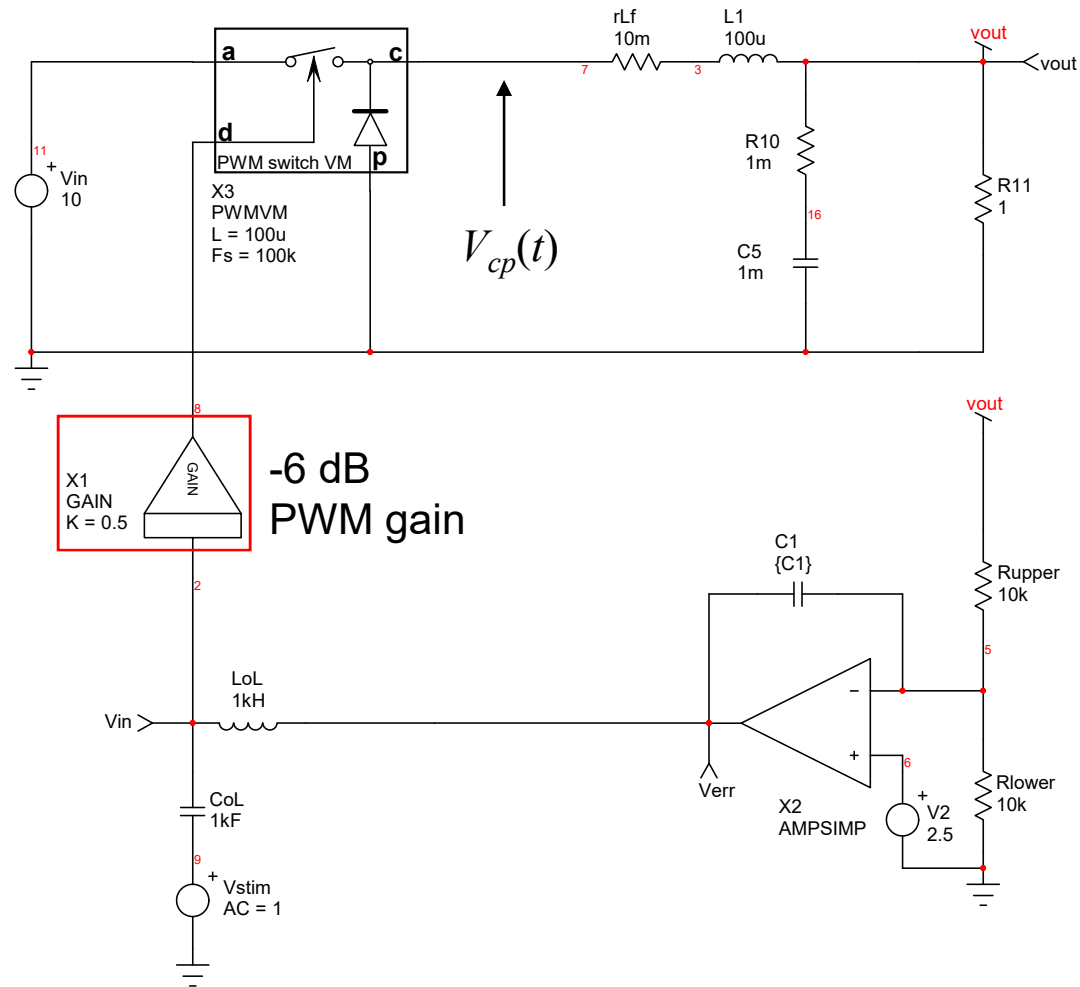$C1=1/(2*\pi*fc*G*Rupper)$   
 $fp0=1/(2*\pi*C1*Rupper)$




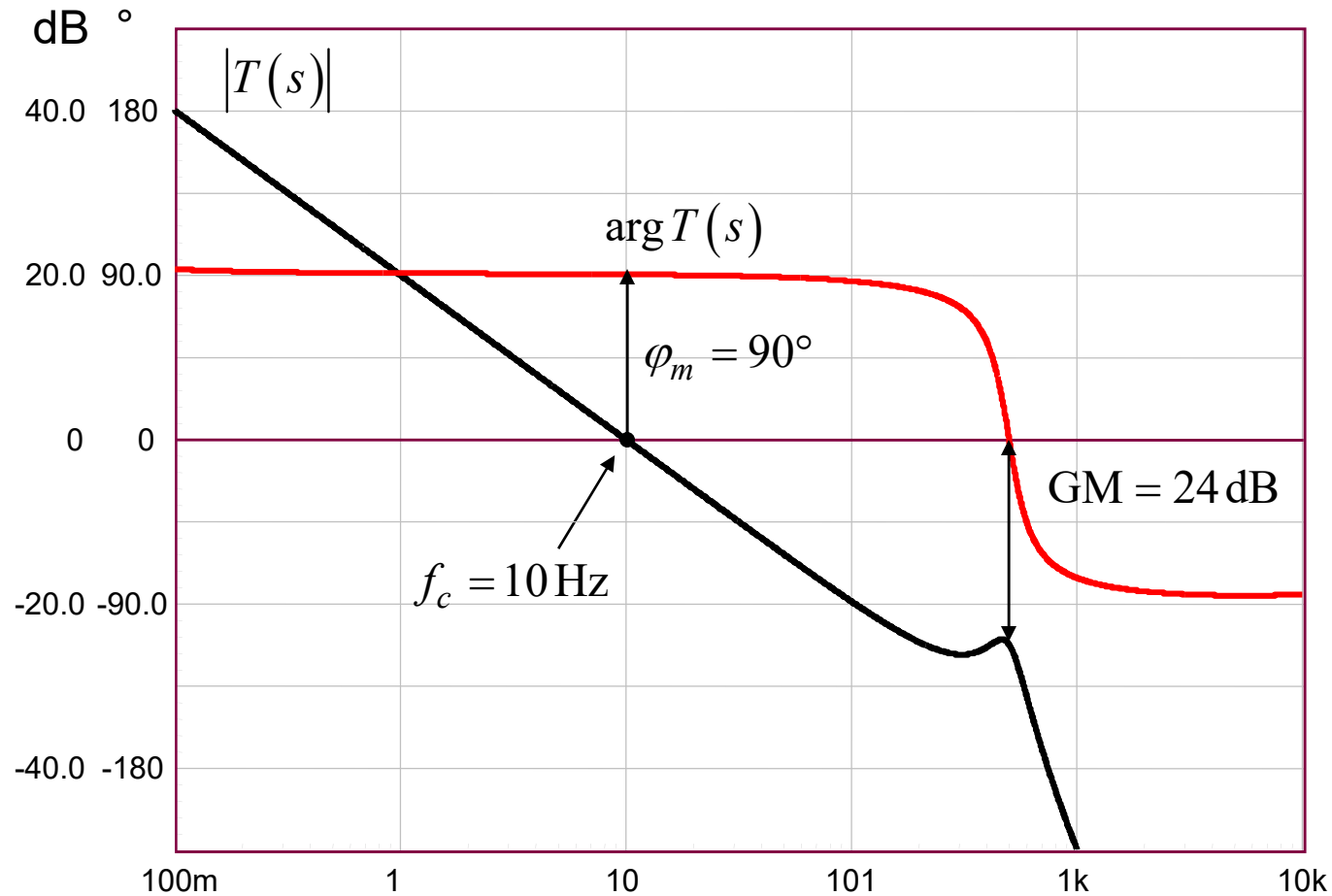
# The Open-Loop Gain Looks Good...

- ❑ The type 1 confirms our 0-dB crossover frequency


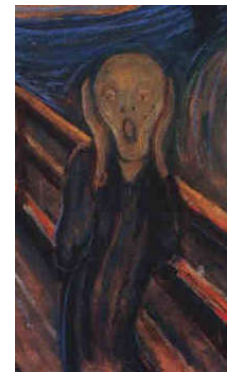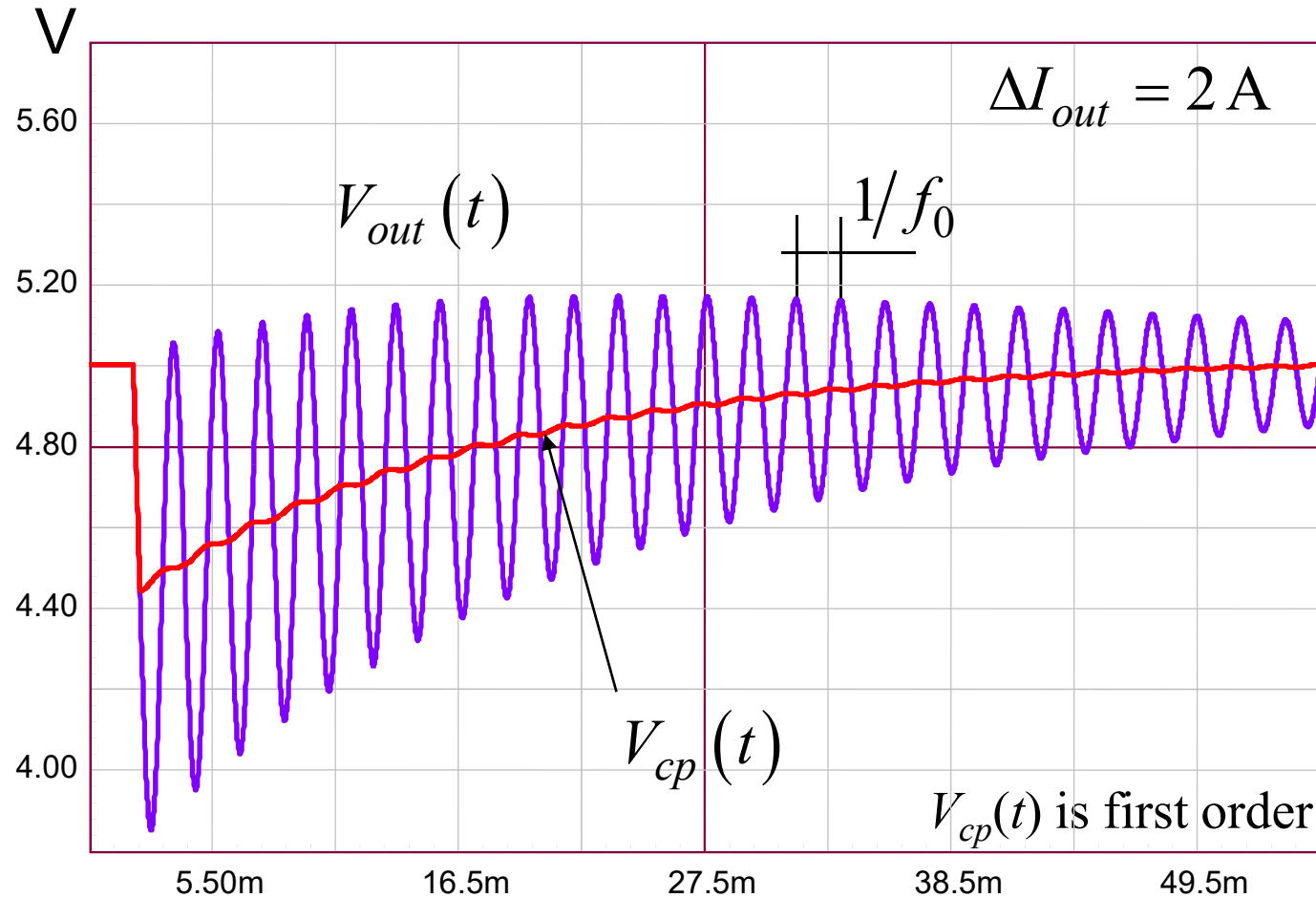
# As Expected: It is Ringing!


- The load step reveals a ringing ac output



Munch

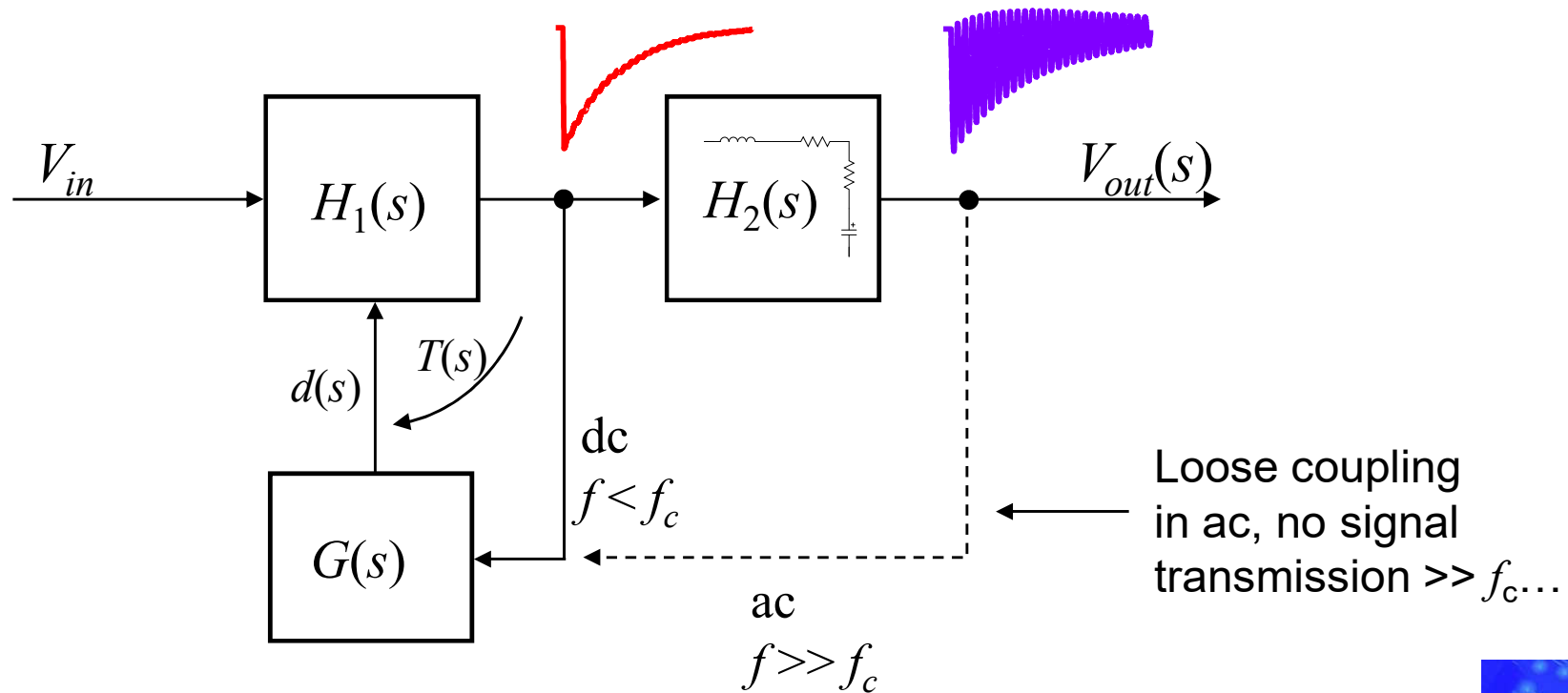
# Good dc Coupling, Weak ac Coupling

- $H_1$  is stable per Bode analysis, but  $H_2$  is out of the loop...




- The dc is fed back via the loop but not the ac...
- Oscillations are NOT due to the loop!

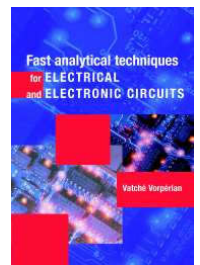"Fast Analytical Techniques for Electrical and Electronic Circuits", V. Vorpérian, Cambridge Press, 2002


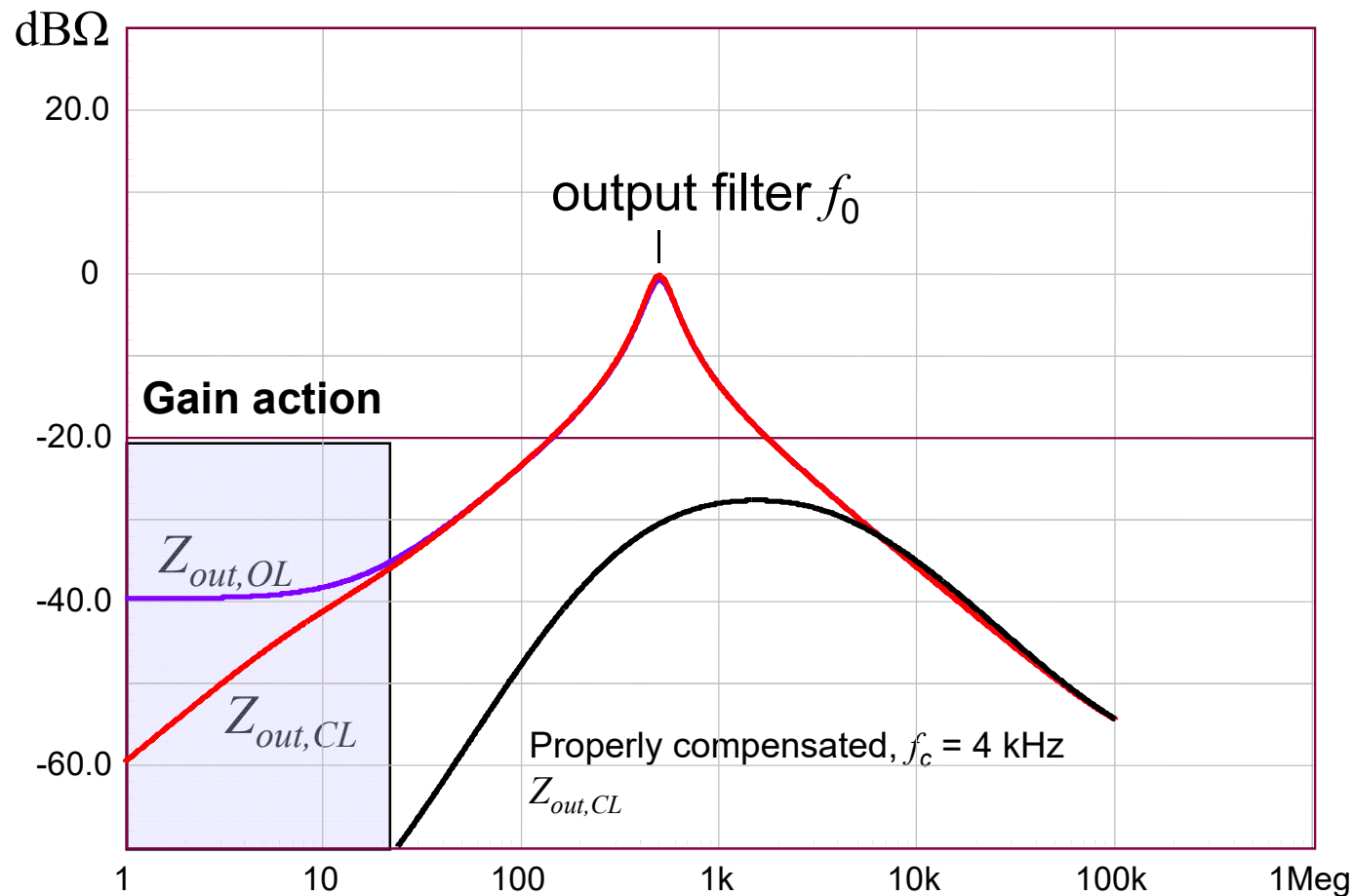
# Again, an Undamped RLC Network...

- ❑ No gain at resonance: the *RLC* network runs open loop



- ❑ The system cannot reduce the  $Q$  at the resonant frequency


# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement**
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough


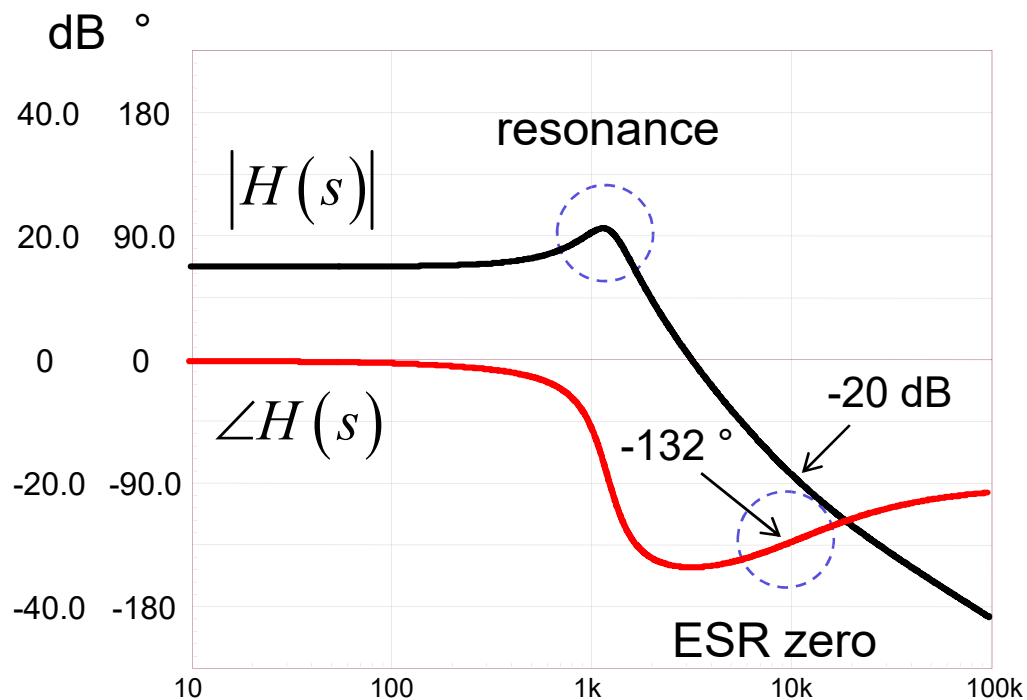
# Compensating the Buck – Method 2

- ❑ In this method, we will focus on two parameters:
  - ✓ crossover frequency  $f_c$
  - ✓ phase margin  $\varphi_m$
- ❑ First, look at the ac response of the power stage:





## Compensating the Buck – Method 2

- ❑ The peaking in  $H$  brings a severe phase lag at  $f_0$ 
  - stay away from  $f_0$ , pick  $f_c$  at least 10 times above (10 kHz)
  - extract the phase/magnitude of  $H$  at 10 kHz:

$$|H(10\text{ kHz})| = -20\text{ dB} \quad \angle H(10\text{ kHz}) = -132^\circ$$

- ❑ The compensator  $G$  must shape the loop gain  $T_{OL}$  by
  - ❖ providing a high dc gain for precision: place an origin pole
  - ❖ reducing the phase lag at 10 kHz to provide a  $\varphi_m$  of  $70^\circ$




What compensation type do we need?


# Compensating the Buck – Method 2

- ❑ The origin pole brings a permanent phase lag of  $90^\circ$ 
  - added to the op amp inversion of  $-180^\circ$ , we have  $-270^\circ$
  - total phase (op amp and  $H$ ) must be  $-360 + 70^\circ = -290^\circ$
  - the needed phase boost at  $f_c$  is thus:


$$\text{boost} = \varphi_m - \angle H(f_c) - 90 = 70 + 132 - 90 = 112^\circ$$

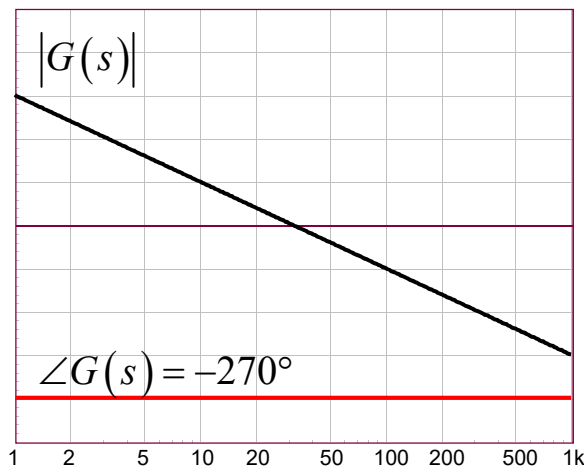

Type 1 – no boost

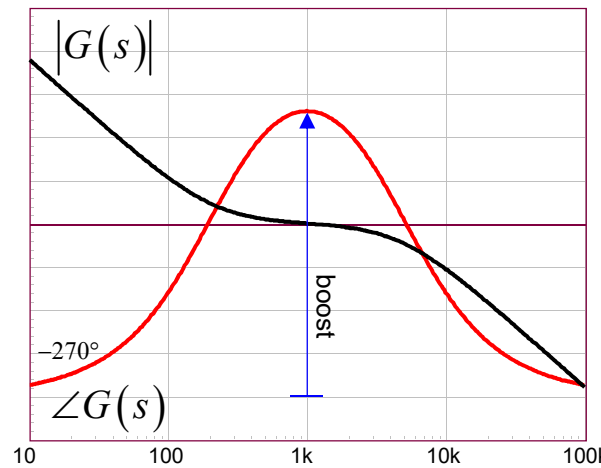

Type 2 – up to  $90^\circ$

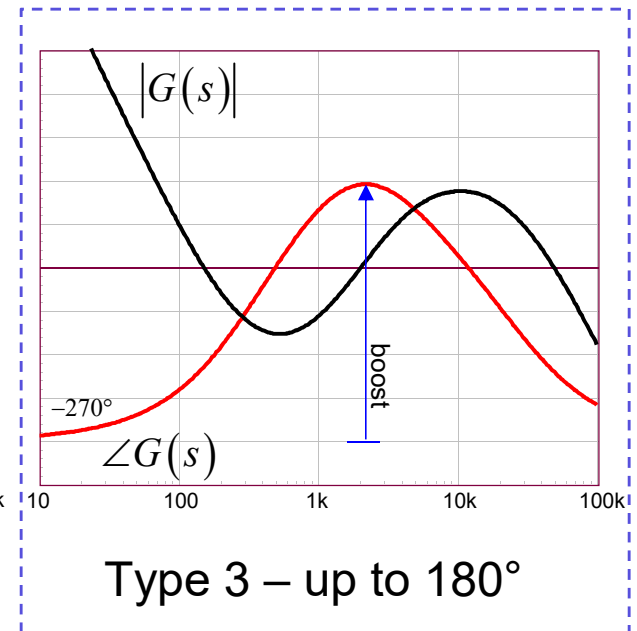

Type 3 – up to  $180^\circ$

## Compensating the Buck – Method 2

- type 3: an origin pole, a double zero and 2 poles
- this is our PID compensator!

$$G(s) = - \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)}{\frac{s}{\omega_{po}} \left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)} = \frac{\omega_{po} \left(1 + \frac{\omega_{z_1}}{s}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)}{\omega_{z_1} \left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)}$$

- The magnitude is derived as:

$$|G(f)| = \frac{f_{po} \sqrt{1 + \left(\frac{f_{z_1}}{f}\right)^2} \sqrt{1 + \left(\frac{f}{f_{z_2}}\right)^2}}{f_{z_1} \sqrt{1 + \left(\frac{f}{f_{p_1}}\right)^2} \sqrt{1 + \left(\frac{f}{f_{p_2}}\right)^2}}$$

- The argument is found to be:

$$\arg G(f) = \arg N - \arg D$$

$$\arg N = \arctan\left(-\frac{f_{z_1}}{f}\right) - \pi + \arctan\left(\frac{f}{f_{z_2}}\right)$$

$$\arg D = \arctan\left(\frac{f}{f_{p_1}}\right) + \arctan\left(\frac{f}{f_{p_2}}\right)$$

## Compensating the Buck – Method 2

- ❑ Place the double zero at  $f_0$ , the second pole at  $F_{sw}/2$
- ❑ The 0-dB crossover pole is adjusted to provide +20 dB at  $f_c$
- ❑ The first pole is adjusted to provide the right  $\phi_m$

$$\arg G(f_c) = \arctan\left(-\frac{f_{z_1}}{f_c}\right) - \pi + \arctan\left(\frac{f_c}{f_{z_2}}\right) - \arctan\left(\frac{f_c}{f_{p_1}}\right) - \arctan\left(\frac{f_c}{f_{p_2}}\right)$$


$$\Rightarrow f_{p_1} = \frac{f_c}{\tan\left(\arg G + \tan^{-1}\left(\frac{f_c}{f_{p_2}}\right) + \tan^{-1}\left(\frac{f_{z_1}}{f_c}\right) - \tan^{-1}\left(\frac{f_c}{f_{z_2}}\right)\right)} = 10.8 \text{ kHz}$$

# Compensating the Buck – Method 2

- The 0-dB crossover pole is adjusted to give 20 dB at 10 kHz

$$f_{po} = |G(f_c)| f_{z_1} \frac{\sqrt{1 + \left(\frac{f_c}{f_{p_1}}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{p_2}}\right)^2}}{\sqrt{1 + \left(\frac{f_{z_1}}{f_c}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{z_2}}\right)^2}} \approx 2 \text{ kHz}$$

- The final configuration is as follows:

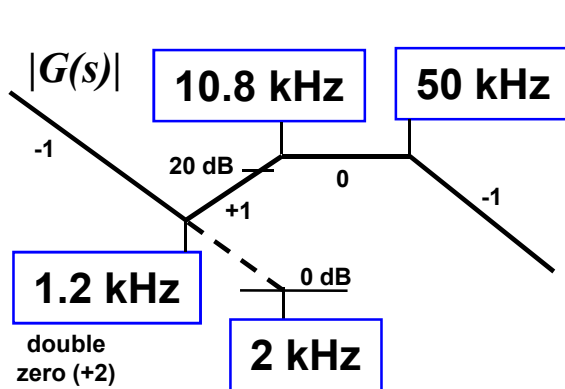


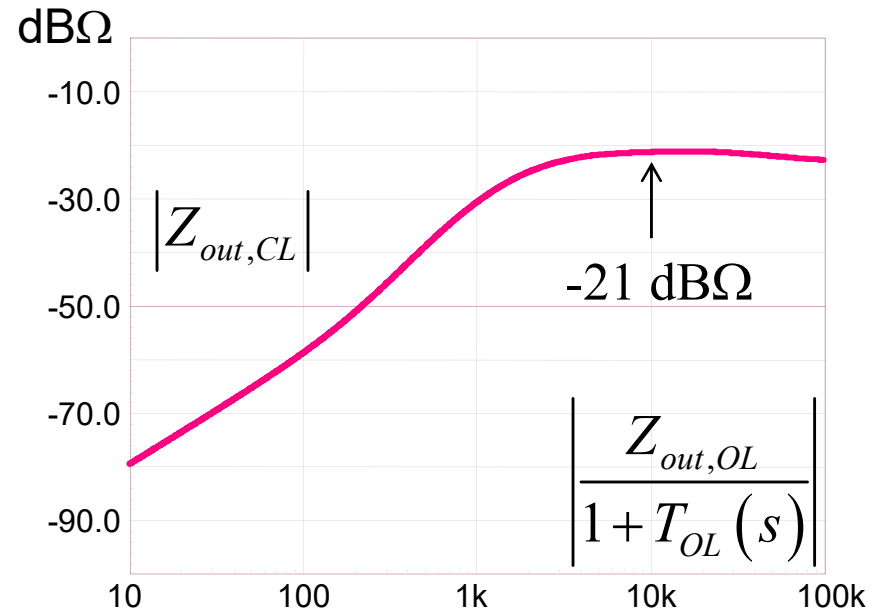
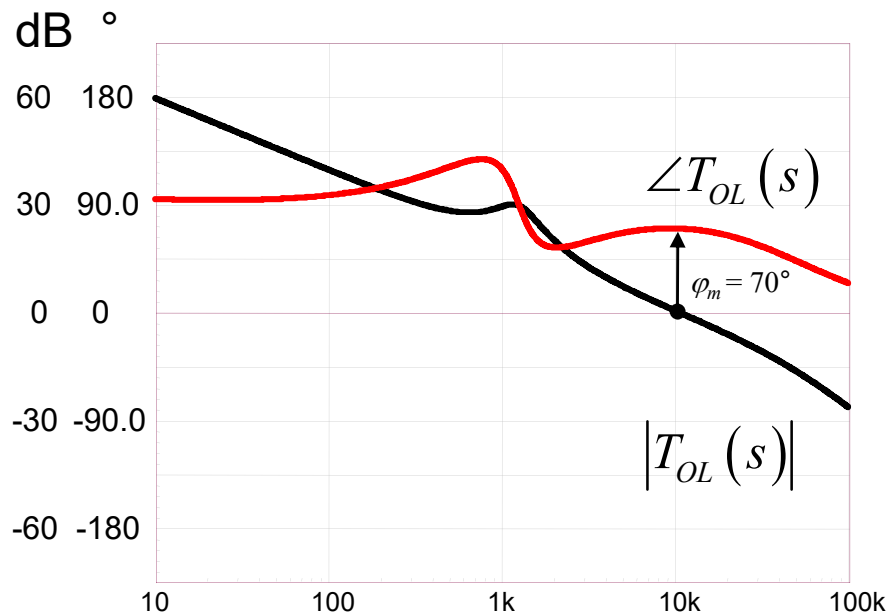
$$|T_{OL}(1.2 \text{ kHz})| = |G(1.2 \text{ kHz})| |H(1.2 \text{ kHz})| = 37 \text{ dB}$$

It should be ok to damp  $Z_{out}$

# Compensating the Buck – Method 2

- Enter the PID coefficients from the poles/zeros positions

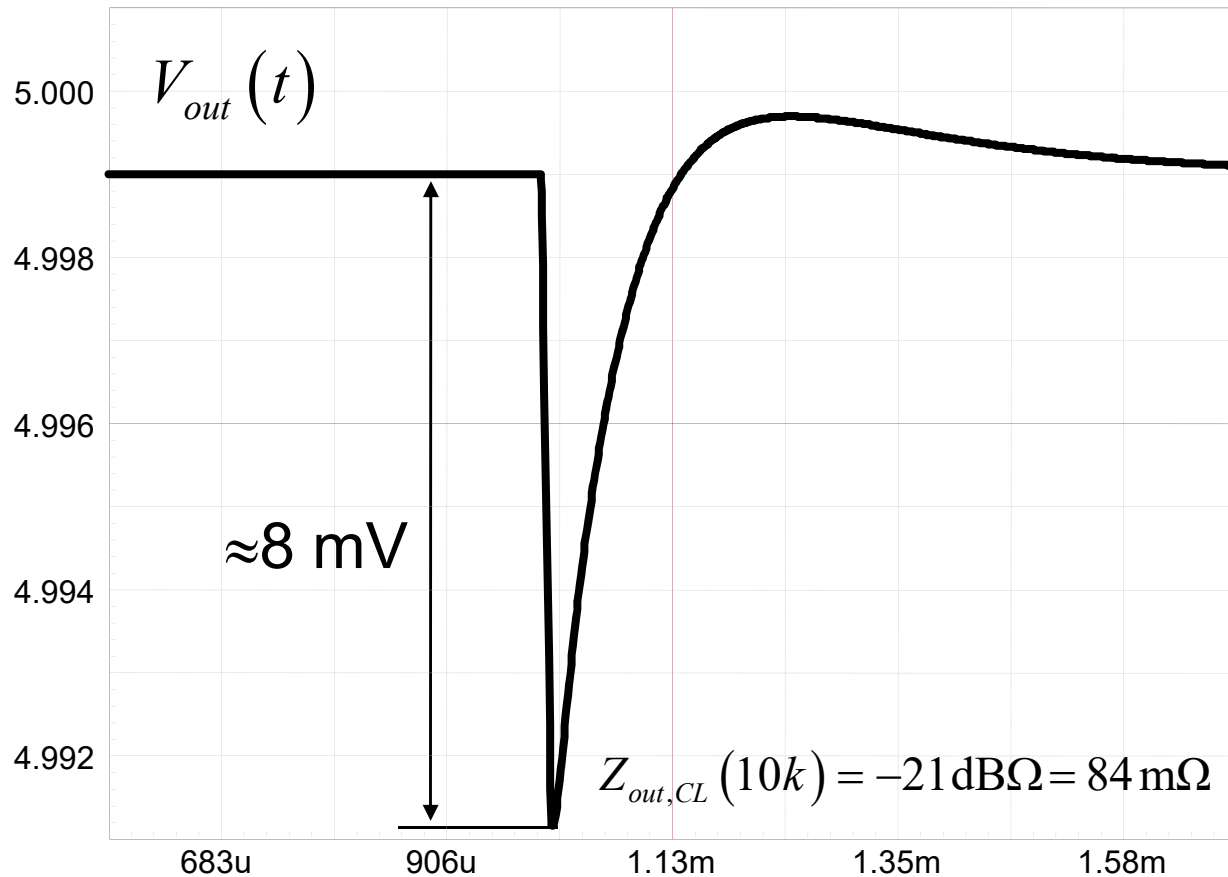

 $\tau_d = 55.5\mu$      $\tau_i = 250\mu$      $N = 3.76$      $k_p = 3.1$



- More than 30 dB at  $f_0$  and absolutely no peaking in  $Z_{out}$

# Compensating the Buck – Method 2

- The transient response with a 0.1-A load step is excellent



# Course Agenda


- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance**
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough




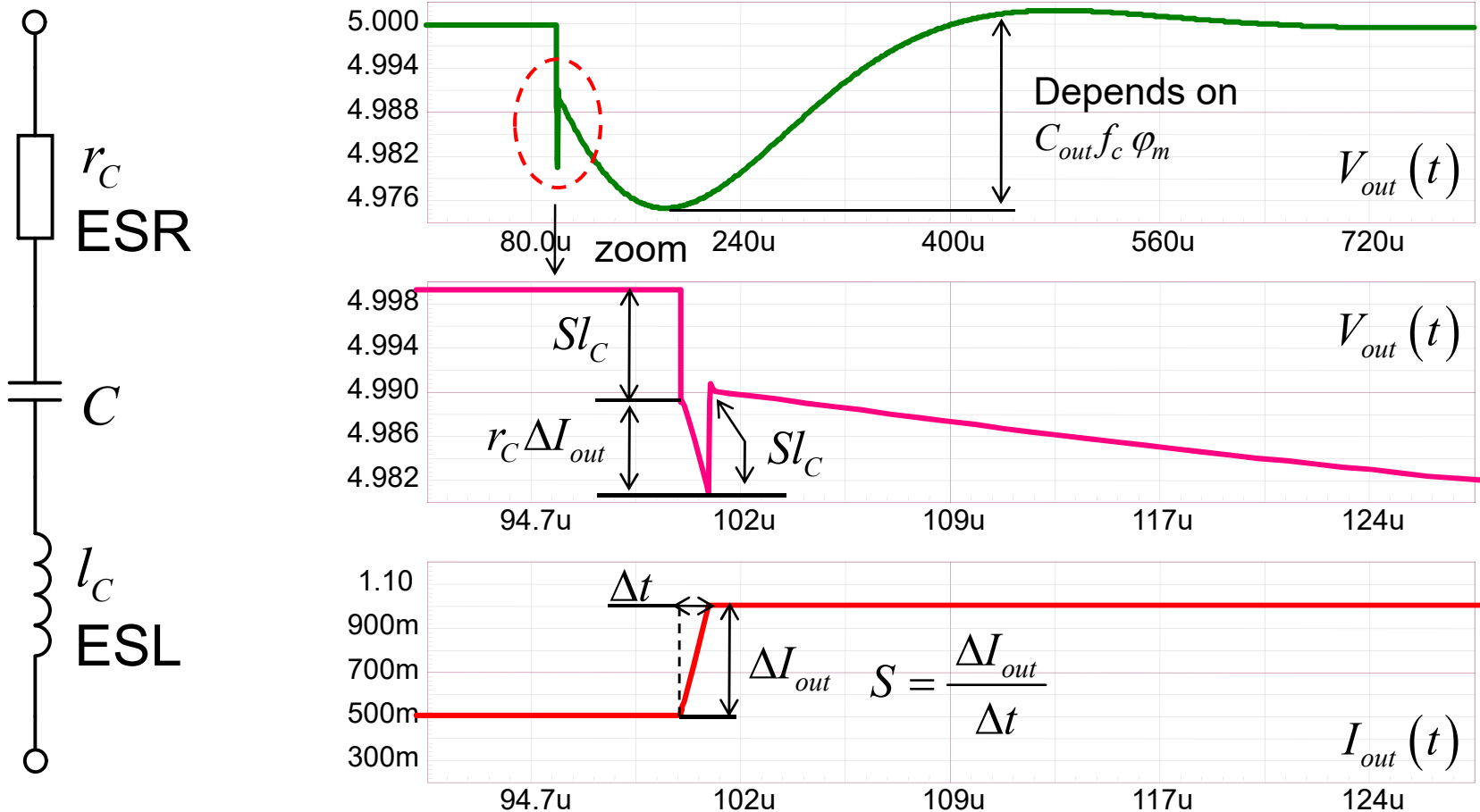
# Compensating the Buck – Method 3


- The capacitor stray elements affect the transient response



R. Redl et al. "Optimizing the Load Transient Response of the Buck Converter", APEC 1998

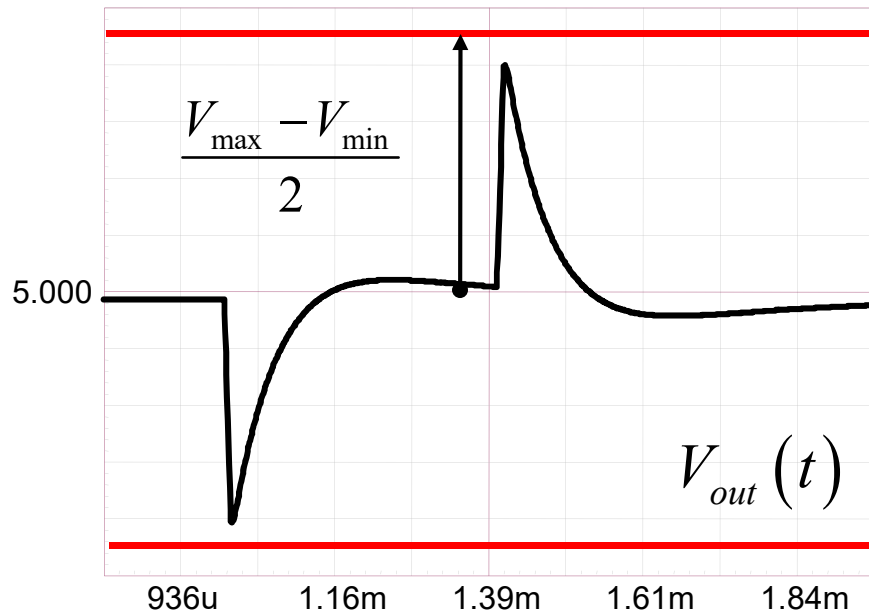
# Compensating the Buck – Method 3

- During a step load, the converter fights the current change



- Traditional compensation:
  - inductive output impedance

➡ Limited excursion

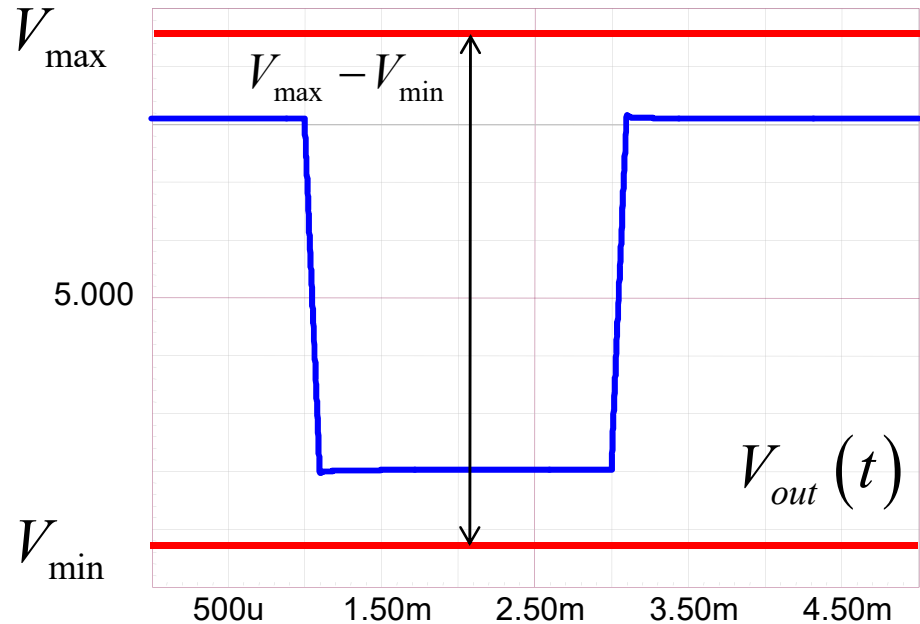


- Adaptive Voltage Positioning
  - resistive output impedance

➡ Full-span excursion
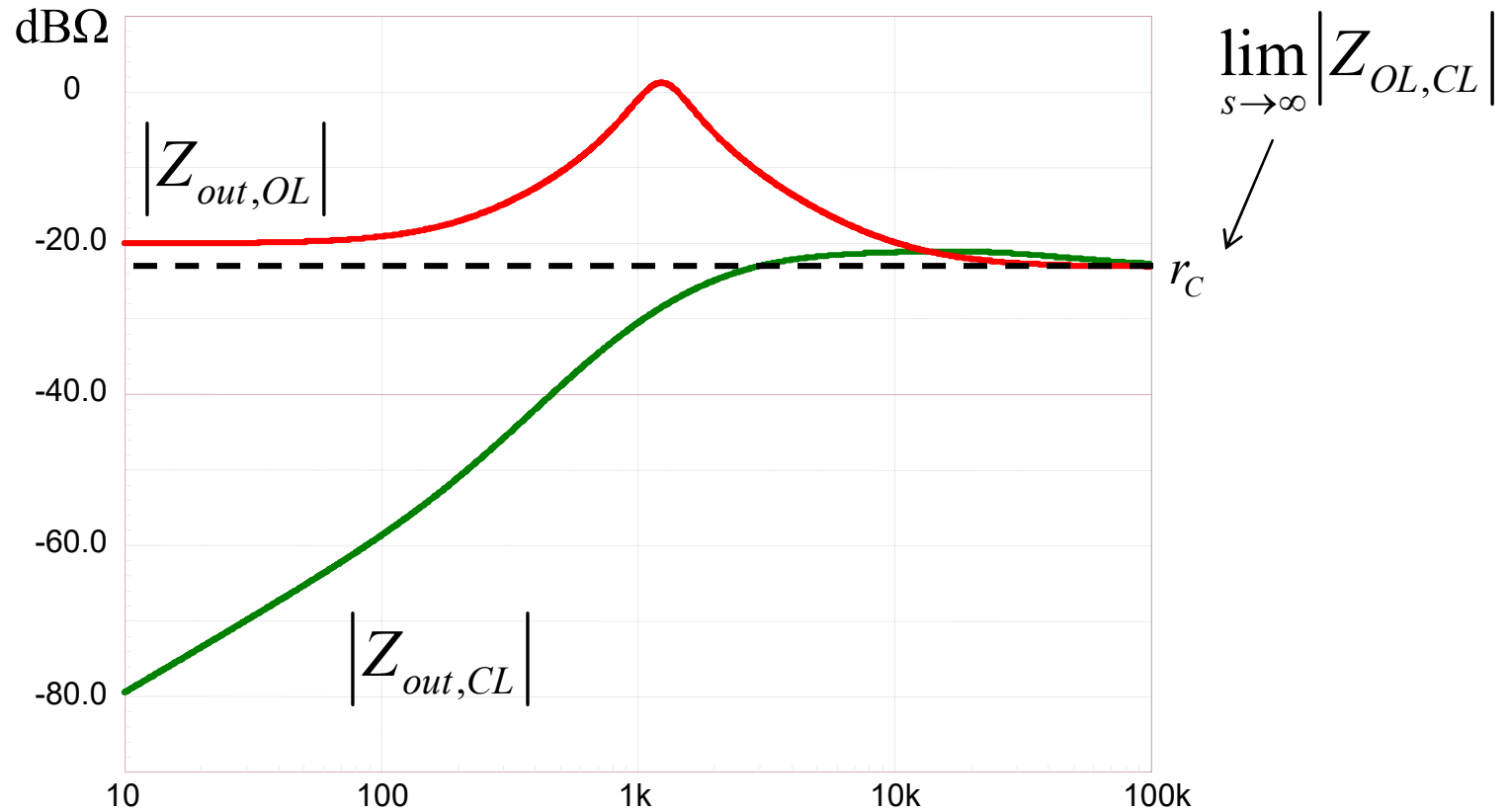
# Compensating the Buck – Method 3

- Whatever the gain,  $Z_{out}$  meets the open-loop value beyond  $f_c$




- Make the output impedance equal to  $r_C$  along the freq. range

# Compensating the Buck – Method 3

□ How to force the output impedance to be resistive?

$$Z_{out,CL} = \frac{Z_{out,OL}}{1+T(s)} = R_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{\omega_0 Q} + 1} \frac{1}{1 + H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{\omega_0 Q} + 1} G(s)}$$

Extract  $G(s)$   
to have:

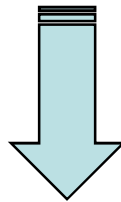


$$Z_{out,CL} = r_C$$


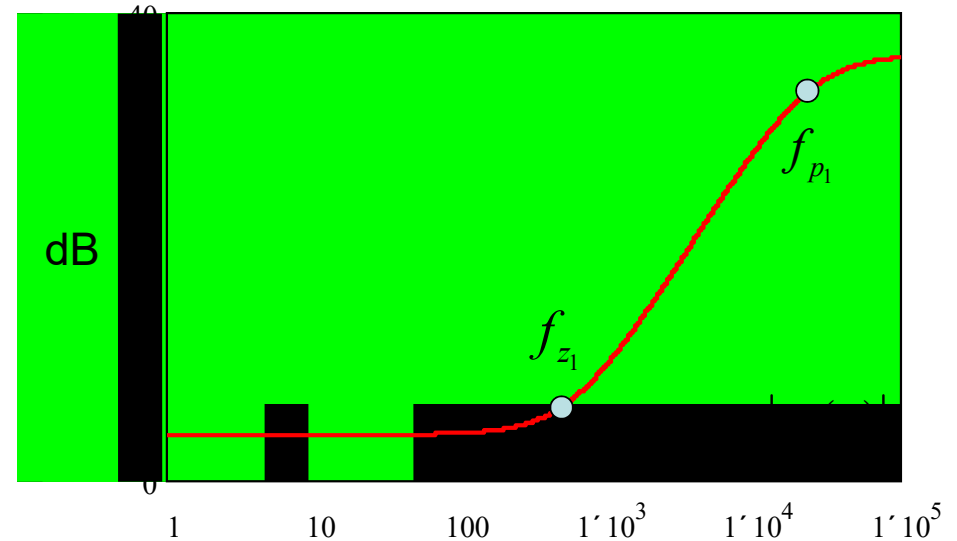
# Compensating the Buck – Method 3

□ Once  $G(s)$  is extracted, what filter is that?

$$G(s) = \frac{R_0 \left(1 + \frac{s}{\omega_{z_2}}\right) \left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q\omega_0} + 1}{r_C G_0 \left(1 + \frac{s}{\omega_{z_1}}\right)}$$




$$G(s) = K_0 \frac{1 + \frac{s}{\omega_{zG}}}{1 + \frac{s}{\omega_{pG}}}$$

# Compensating the Buck – Method 3

□ Some parameter identification is now needed:

$$K_0 = \frac{r_L - r_C}{H_0 r_C} = 1.8 \quad a = \frac{r_L}{\omega_{z_1} \omega_{z_2}} - \frac{r_C}{\omega_0^2} = 47.7 p \quad b = r_L \left( \frac{1}{\omega_{z_1}} + \frac{1}{\omega_{z_2}} \right) - \frac{r_C}{Q \omega_0} = 74.2 u$$

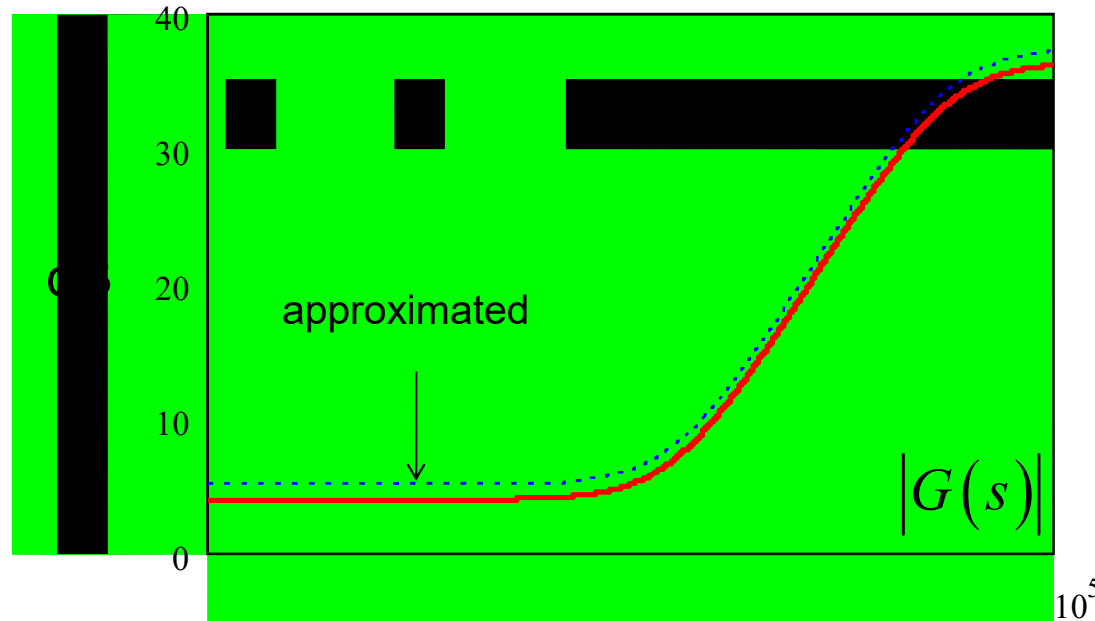
$$c = r_L - r_C = 0.27 \quad f_{pG} = f_{z_1} = 24 \text{ kHz} \quad f_{zG} = \frac{b - \sqrt{b^2 - 4ac}}{4\pi a} = 580 \text{ Hz}$$



YAO et al., "Design Considerations for VRM Transient Response Based on the Output Impedance", IEEE Proceedings, 2003
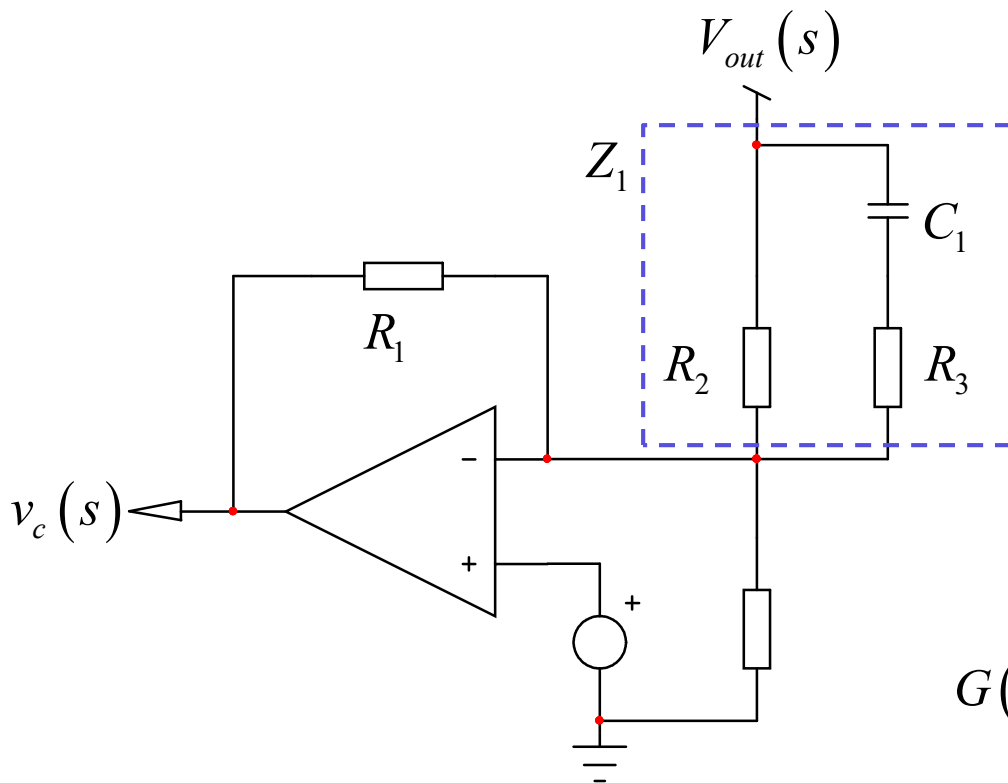
# Compensating the Buck – Method 3

- The following op amp architecture will do the job



$$\frac{v_c(s)}{V_{out}(s)} = -\frac{R_1}{Z_1}$$

$$Z_1 = \frac{R_2 \left( R_3 + \frac{1}{sC_1} \right)}{R_2 + \left( R_3 + \frac{1}{sC_1} \right)}$$

$$G(s) = -\frac{R_2 \left[ 1 + sC_1 (R_2 + R_3) \right]}{R_1 (1 + sR_3C_1)}$$

➔  $K_0 = \frac{R_2}{R_1} \quad \omega_{z_1} = \frac{1}{C_1 (R_2 + R_3)} \quad \omega_{p_1} = \frac{1}{R_3 C_1}$

# Compensating the Buck – Method 3

- A test fixture is assembled using a buck averaged model

parameters


$V_{in}=10$   
 $V_{peak}=2$

$\pi=3.14159$

$f_z=580$   
 $f_p=24k$

$W_z=2*\pi*f_z$   
 $W_p=2*\pi*f_p$   
 $k_v=1.8$

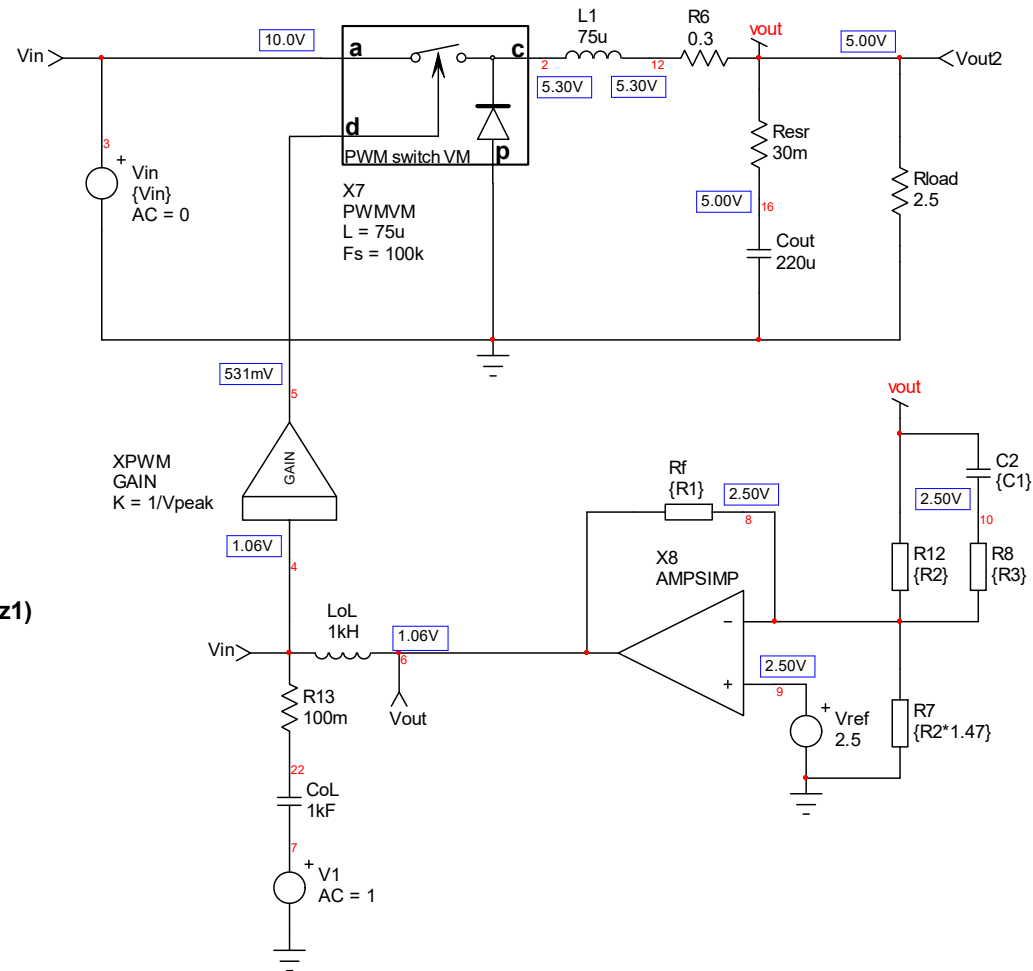
$R_1=10k$   
 $R_2=R_1/k_v$   
 $R_3=R_1*W_z1/(K_v*(W_p1-W_z1))$   
 $C_1=(K_v*(W_p1-W_z1))/(R_1*W_p1*W_z1)$




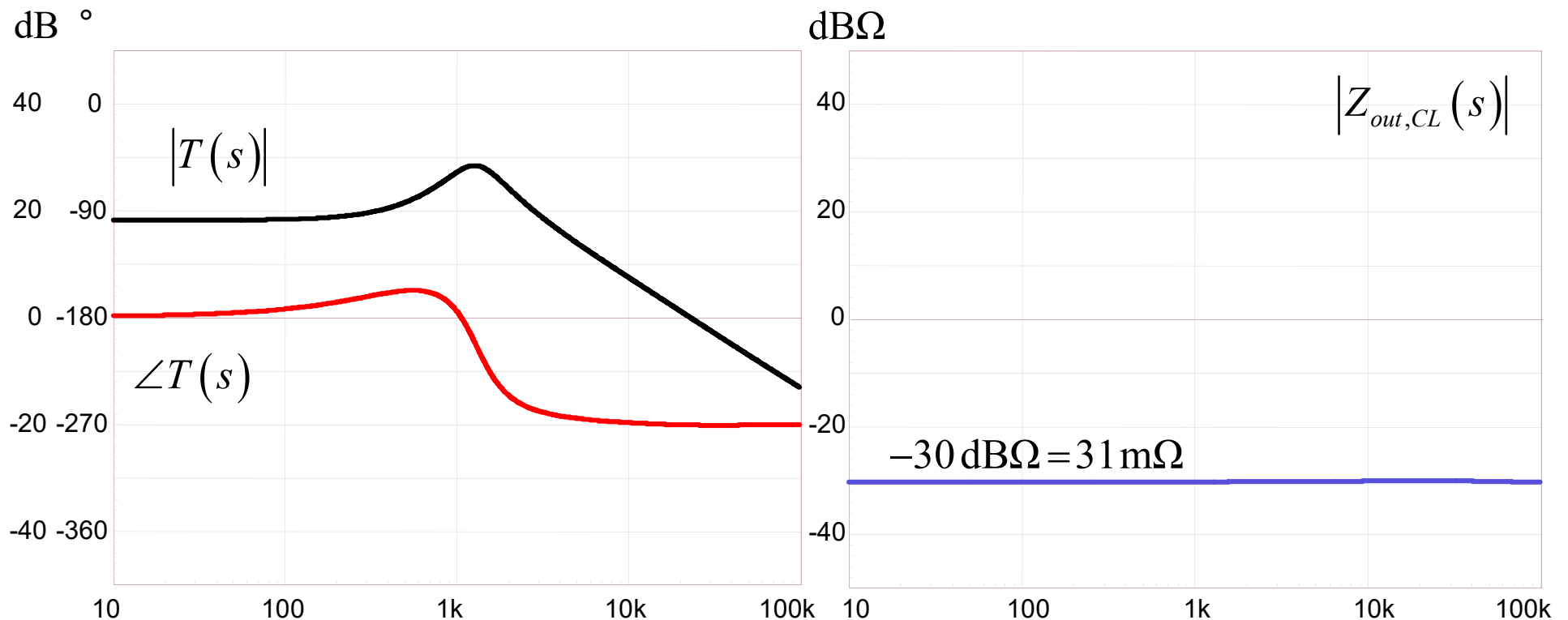
# Compensating the Buck – Method 3

- ❑ After stabilization we have good margins with a 20-kHz  $f_c$




- ❑ The output impedance is purely resistive!
- ❑ But the dc gain is low: line and load regulation problems!
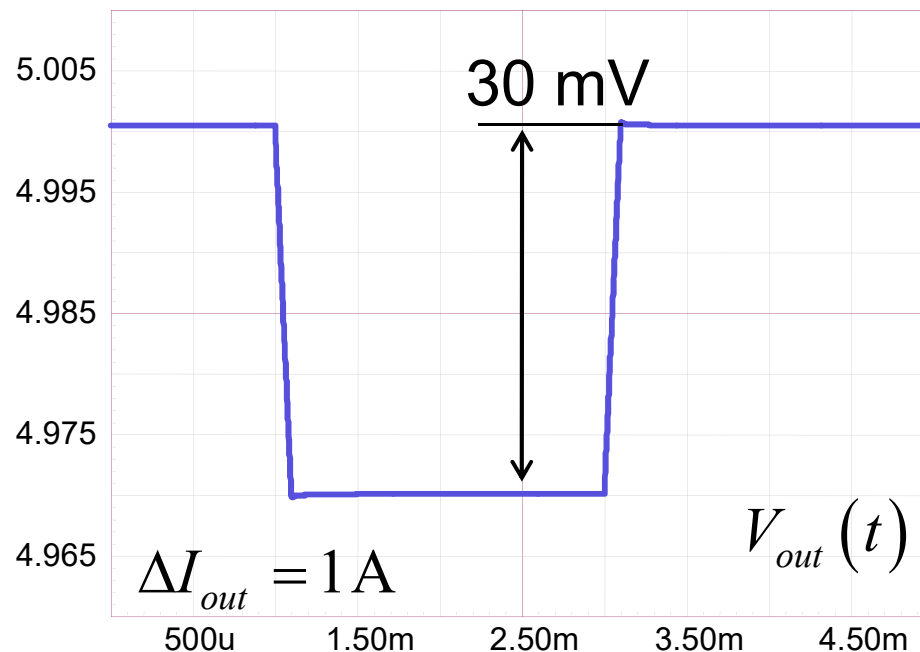
# Compensating the Buck – Method 3

□ Also, the gain expression  $K_0$  can be a problem:


$$K_0 = \frac{r_L - r_C}{G_0 r_C} > 0 \rightarrow r_L > r_C$$



➤ VM, fixed frequency, is not the best for  $Z_{out}$  resistive shaping
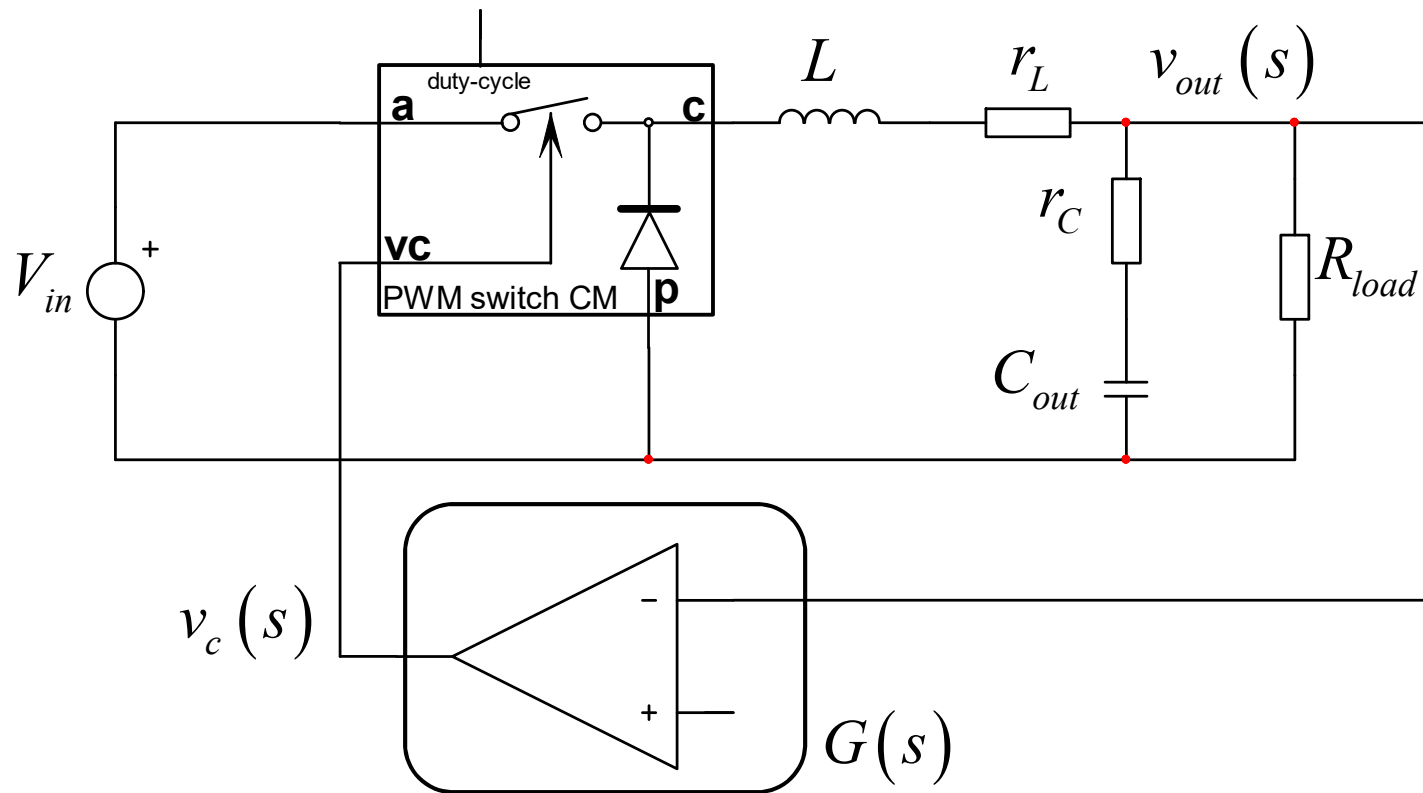
# Compensating the Buck – Method 3




- Going current-mode, fixed frequency is one way to go



- Use the PWM switch model in current-mode for  $Z_{out}$
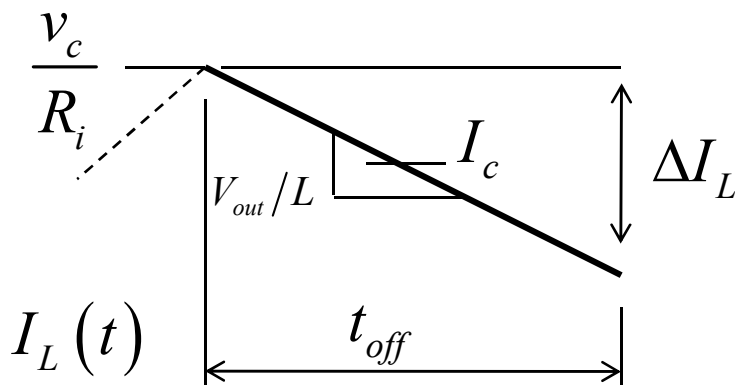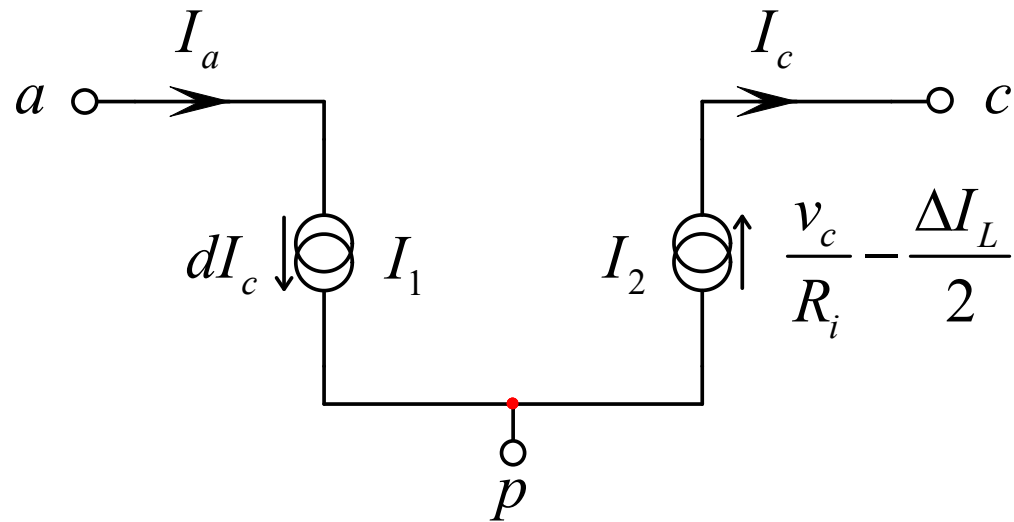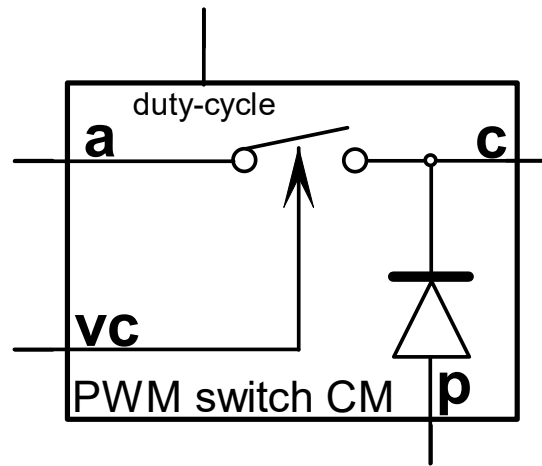
# Compensating the Buck – Method 3

- The large-signal model combines two current-sources



$$I_2 = \frac{v_c}{R_i} - \frac{(1-D)T_{sw}}{2L} V_{out}$$

## Compensating the Buck – Method 3

- For ac study, we must obtain a small-signal model

$$I_2(V_{out}, V_c) = \frac{V_c}{R_i} - \frac{(1-D)T_{sw}}{2L} V_{out} = \frac{V_c}{R_i} - \frac{\left(1 - \frac{V_{out}}{V_{in}}\right) T_{sw}}{2L} V_{out}$$

- Calculate the partial derivative coefficients to  $v_{out}$  and  $v_c$


$$\frac{\partial I_2}{\partial V_c} \hat{v}_c + \frac{\partial I_2}{\partial V_{out}} \hat{v}_{out} = \frac{\hat{v}_c}{R_i} + \frac{T_{sw}}{2L} \left( \frac{2V_{out}}{V_{in}} - 1 \right) \hat{v}_{out}$$

→ gm

- Update the schematic with this linear source
  - as  $R$ ,  $L$  and  $C$  are also linear, Laplace applies
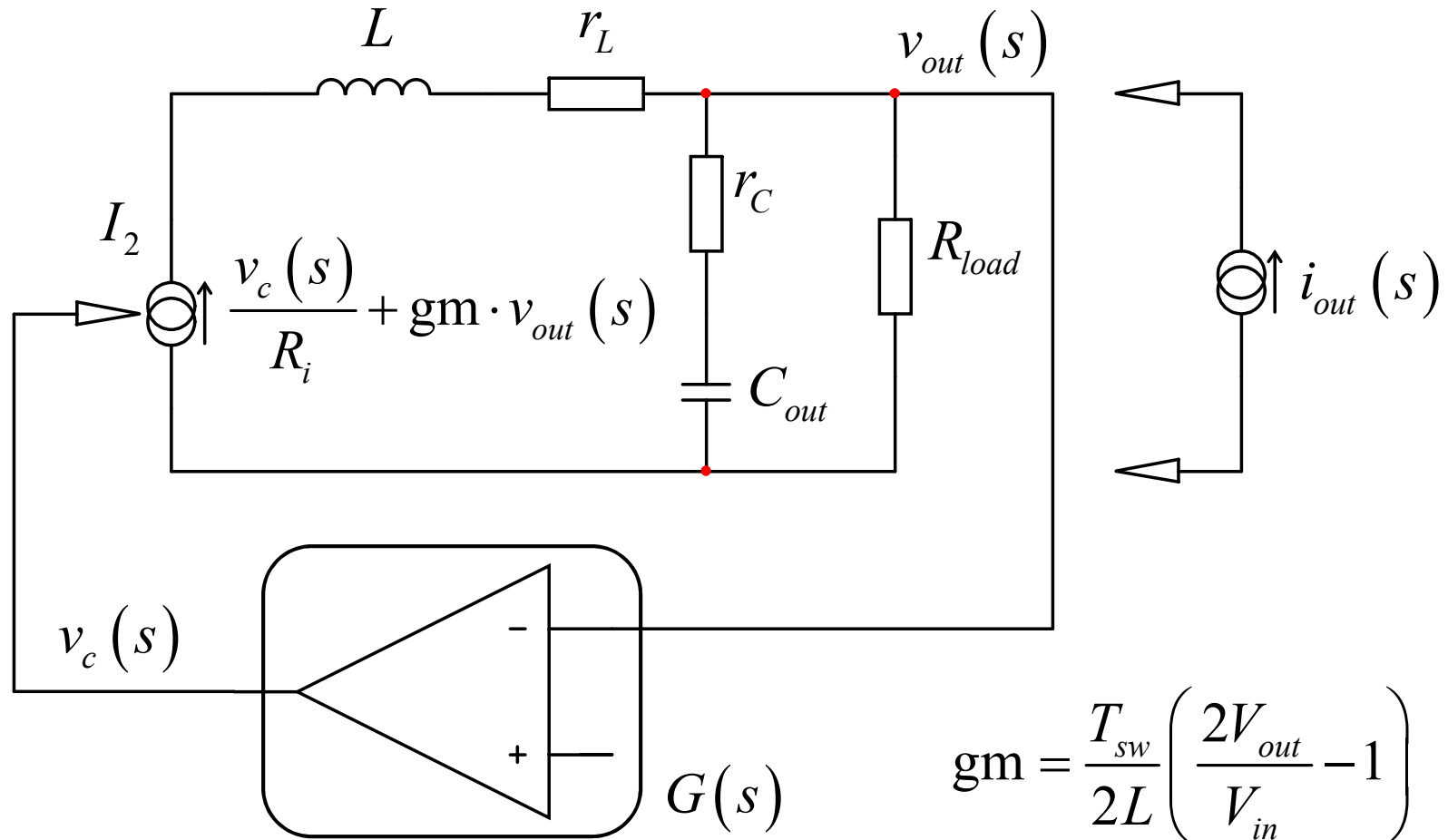
# Compensating the Buck – Method 3

- We look at the output impedance closed-loop



## Compensating the Buck – Method 3

□ We can apply the superposition theorem:

$$v_{out}(s) = \left( \frac{v_c(s)}{R_i} + gm \cdot v_{out}(s) \right) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right) \quad i_{out} \text{ is } 0$$

$$v_{out}(s) = -i_{out}(s) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right) \quad I_2 \text{ is } 0$$

□ Considering  $v_c(s) = -G(s)v_{out}(s)$  we have:

$$v_{out}(s) = v_{out}(s) \left( gm - \frac{G(s)}{R_i} \right) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right) - i_{out}(s) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right)$$

$$v_{out}(s) \left( 1 - \left( gm - \frac{G(s)}{R_i} \right) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right) \right) = -i_{out}(s) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right)$$

# Compensating the Buck – Method 3

□ The output impedance is thus:

$$Z_{out,CL}(s) = -\frac{\hat{v}_{out}(s)}{\hat{i}_{out}(s)} = \frac{\left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right)}{1 - \left( gm - \frac{G(s)}{R_i} \right) \left( R_{load} \parallel \left( r_C + \frac{1}{sC_{out}} \right) \right)}$$

□ Giving a small massage, we obtain:

$$Z_{out,CL}(s) = \frac{R_{load} R_i}{R_i + G(s) R_{load} - R_i R_{load} \cdot gm} \cdot \frac{1 + sr_C C_{out}}{1 + sC_{out} \left( \frac{R_i R_{load} + R_i r_C + G(s) R_{load} r_C - R_i R_{load} r_C gm}{R_i + G(s) R_{load} - R_i R_{load} \cdot gm} \right)}$$

"There is a  
massage  
for you"





## Compensating the Buck – Method 3

□ Factoring and re-arranging, we have:

$$Z_{out,CL}(s) = R(s) \frac{1 + s/\omega_{z_1}}{1 + s/\omega_{p_1}} \quad R(s) = \frac{R_{load} R_i}{R_i + \boxed{G}(s) R_{load} - R_i R_{load} \cdot gm} \quad \omega_{z_1} = \frac{1}{r_C C_{out}}$$

$$\omega_{p_1} = \frac{1}{C_{out} \left( \frac{R_i R_{load} + R_i r_C + \boxed{G}(s) R_{load} r_C - R_i R_{load} r_C gm}{R_i + \boxed{G}(s) R_{load} - R_i R_{load} \cdot gm} \right)}$$

□ Now make  $Z_{out,CL}(s) = r_C$  and extract  $G(s)$ :


$$G(s) = \frac{R_i (R_{load} - r_C + R_{load} r_C gm)}{r_C R_{load}} \frac{1 + s C_{out} \frac{R_{load} r_C^2 gm - r_C^2}{R_{load} - r_C + R_{load} r_C gm}}{1 + s r_C C_{out}}$$

# Compensating the Buck – Method 3

- The compensator brings a single pole/zero response

$$G(s) = G_0 \frac{1 + s/\omega_{z_1}}{1 + s/\omega_{p_1}} \quad G_0 = \frac{R_i (R_{load} - r_C + R_{load} r_C g_m)}{r_C R_{load}} \approx \frac{R_i}{r_C} \quad \omega_{p_1} = \frac{1}{C_{out} r_C}$$
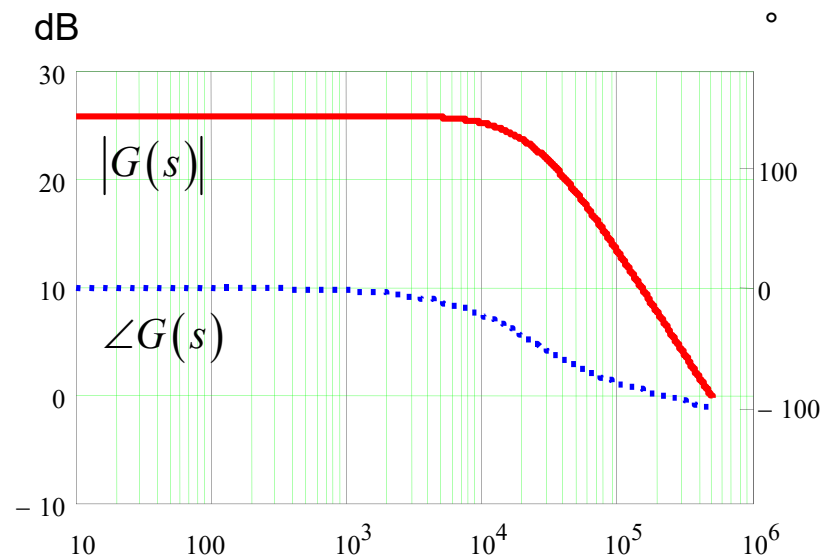
$$\omega_{z_1} = \frac{1}{C_{out} \frac{R_{load} r_C^2 g_m - r_C^2}{R_{load} - r_C + R_{load} r_C g_m}} \approx \frac{1}{C_{out} \frac{-r_C^2}{R_{load}}} \quad \Rightarrow \quad \text{Very high frequency can be neglected}$$




$$R_i = 0.6 \Omega$$

$$r_C = 30 \text{ m}\Omega$$

$$C_{out} = 220 \mu\text{F}$$
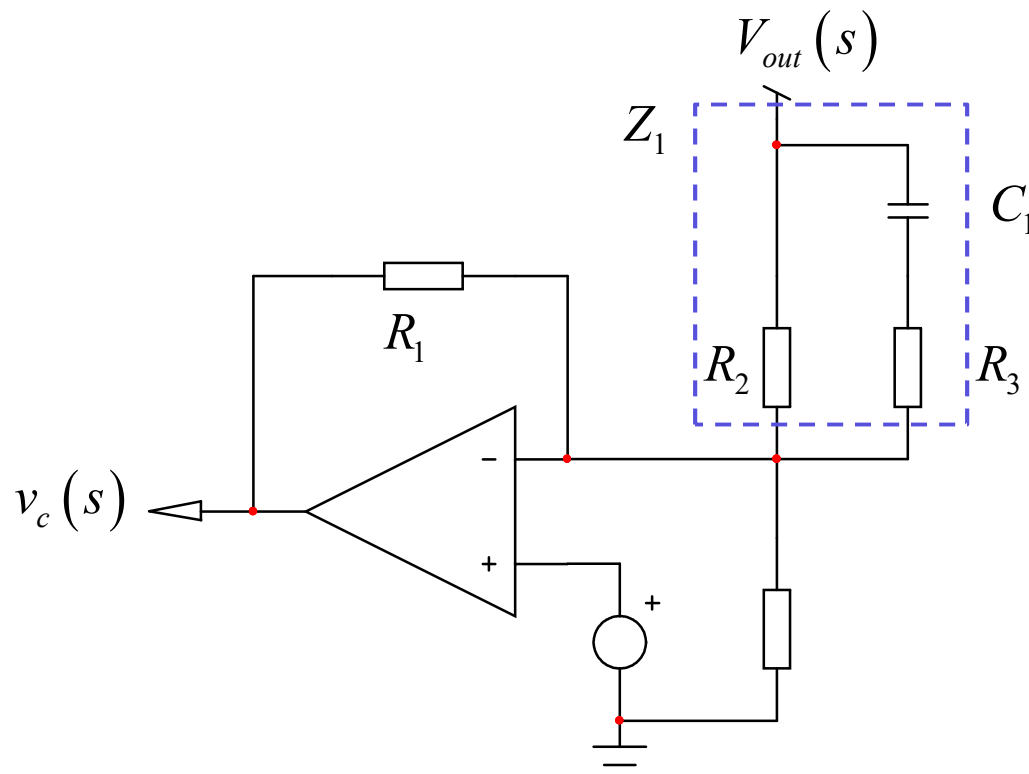
# Compensating the Buck – Method 3

- ❑ Sub-harmonic oscillations at  $F_{sw}/2$  can cause peaking
- Place a zero at  $\pi F_{sw}$  as recommended by YAO and al.



$$\frac{v_c(s)}{V_{out}(s)} = -\frac{R_1}{Z_1}$$

$$Z_1 = \frac{R_2 \left( R_3 + \frac{1}{sC_1} \right)}{R_2 + \left( R_3 + \frac{1}{sC_1} \right)}$$

$$G(s) = -\frac{R_2 \left[ 1 + sC_1 (R_2 + R_3) \right]}{R_1 (1 + sR_3C_1)}$$


➔  $G_0 = \frac{R_2}{R_1} \quad \omega_{z_1} = \frac{1}{C_1 (R_2 + R_3)} \quad \omega_{p_1} = \frac{1}{R_3 C_1}$

YAO et al. , "Design Considerations for VRM Transient Response Based on the Output Impedance", IEEE Proceedings, 2003



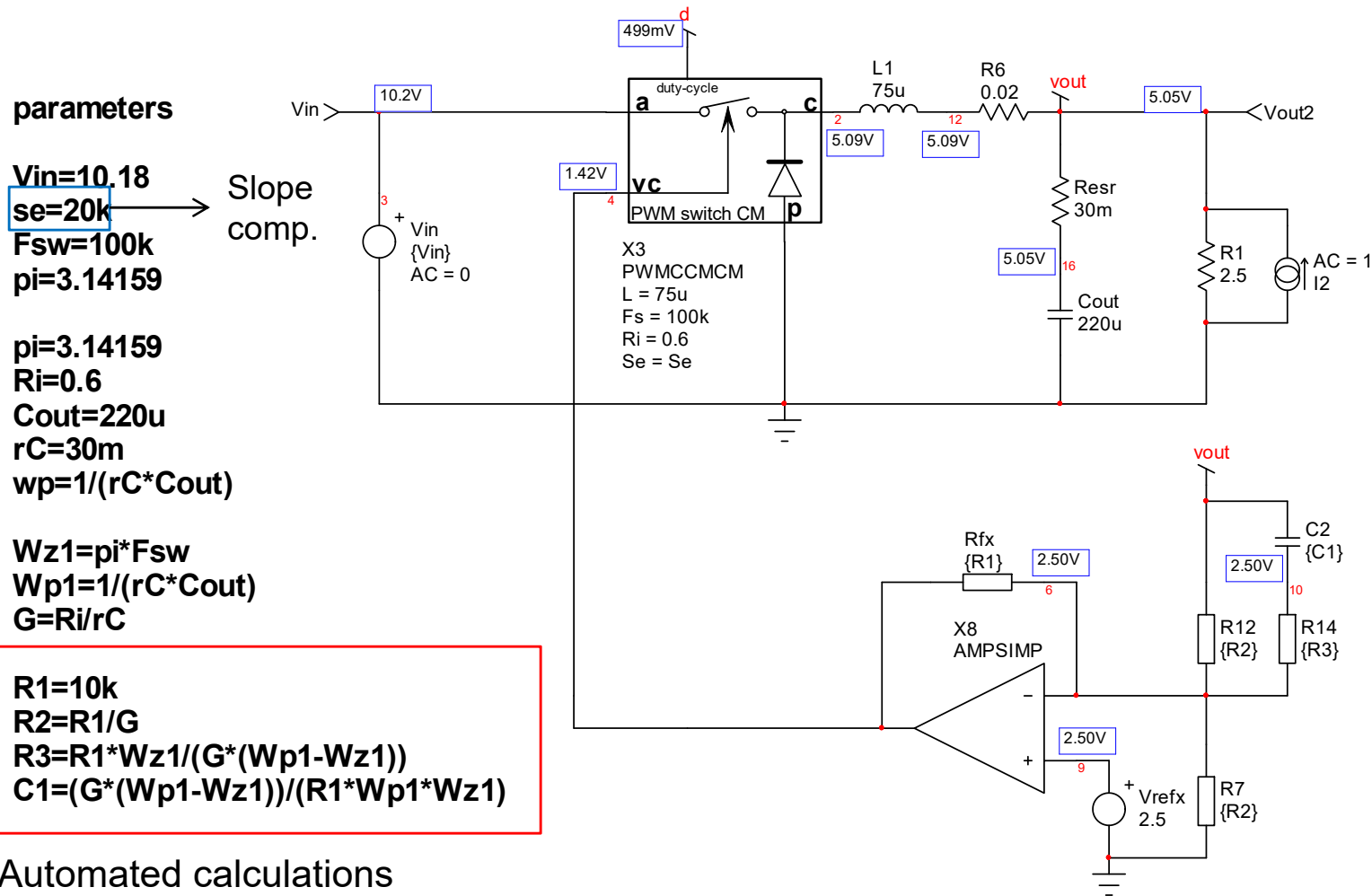
# Compensating the Buck – Method 3

- Run the SPICE simulation with the CM PWM switch model



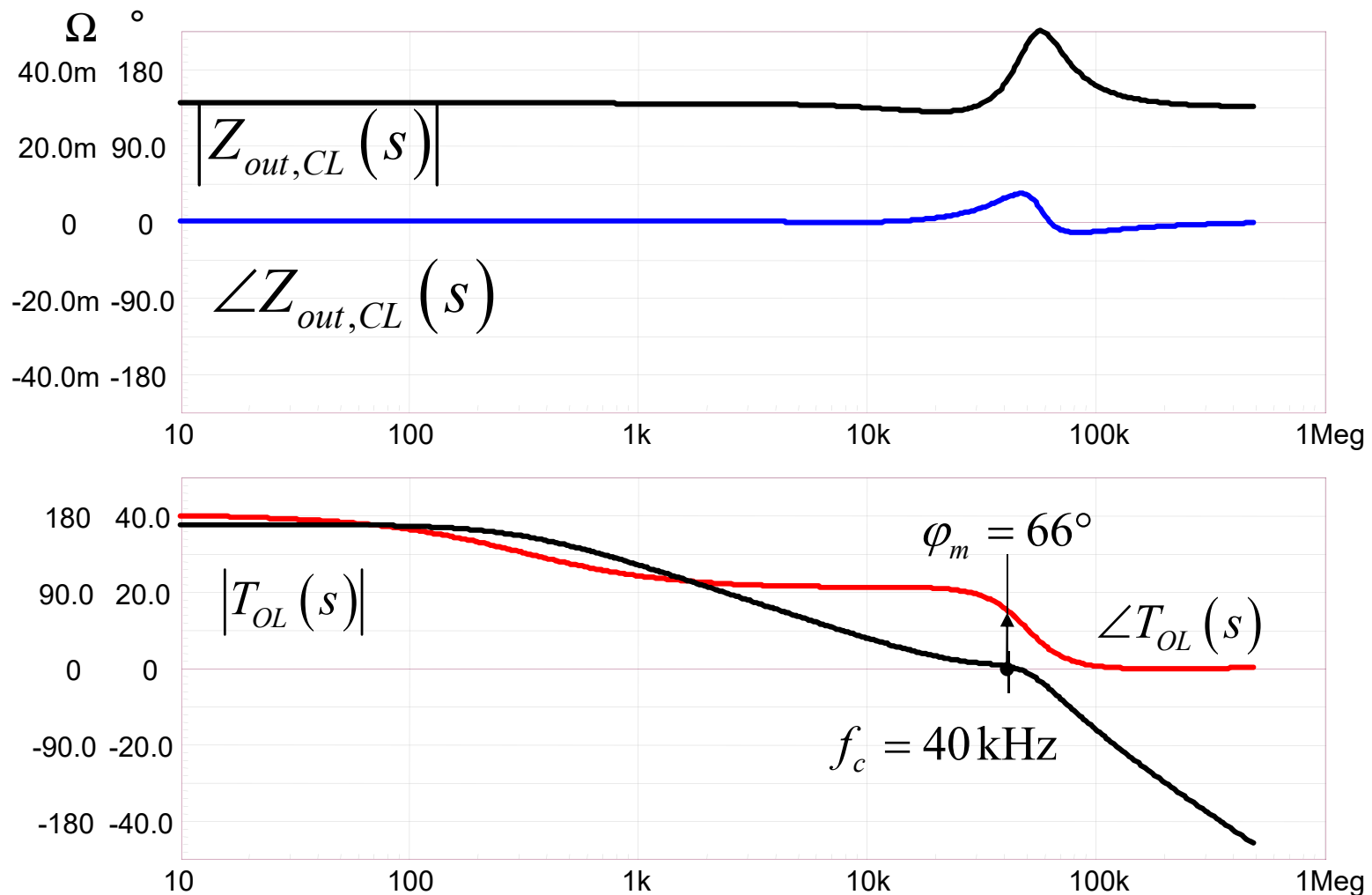
# Compensating the Buck – Method 3

- The output impedance is resistive, the system is stable.


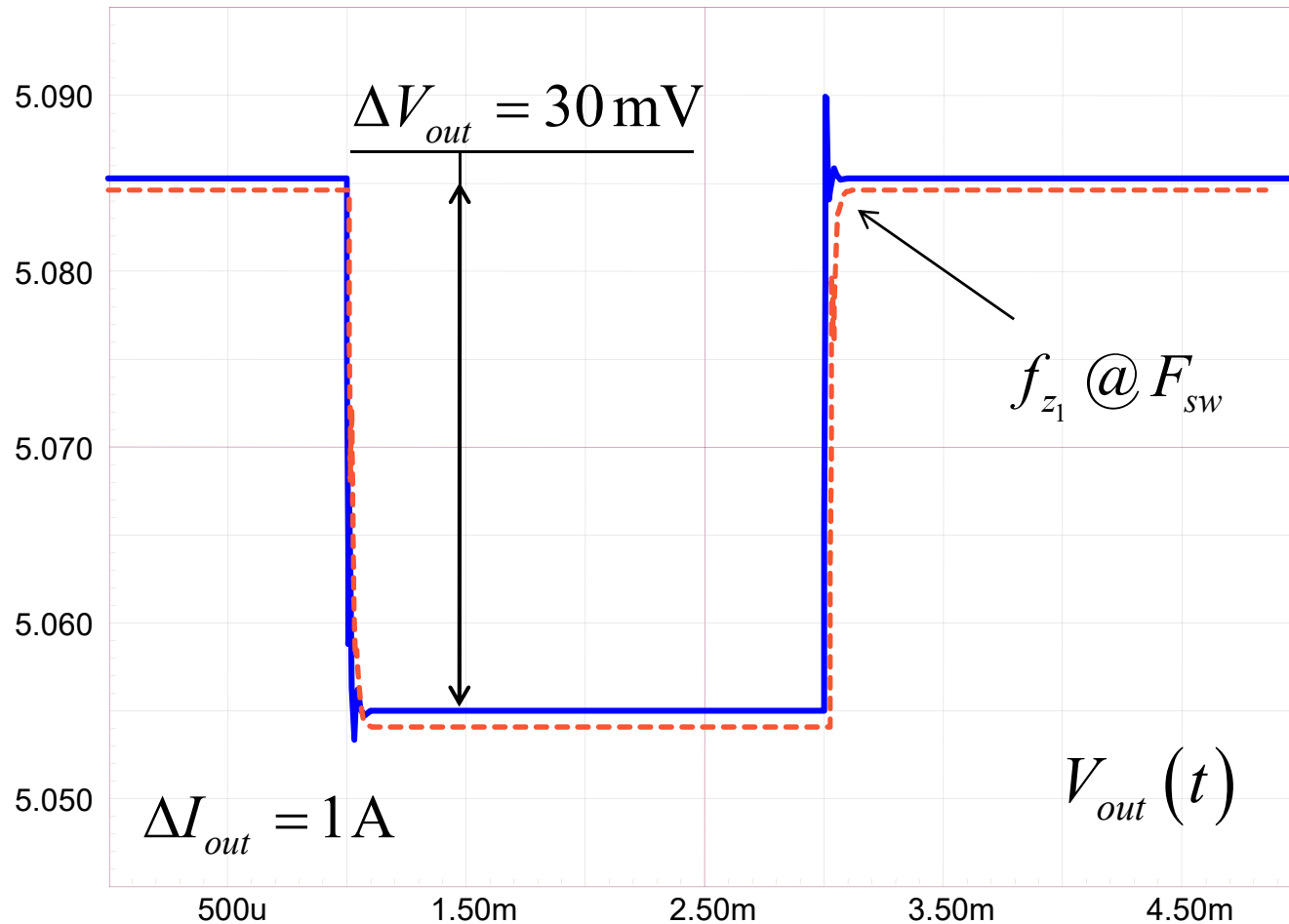
# Compensating the Buck – Method 3

- The output response is a square signal as expected




# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin**
- What is Delay Margin?
- Gain Margin is not Enough



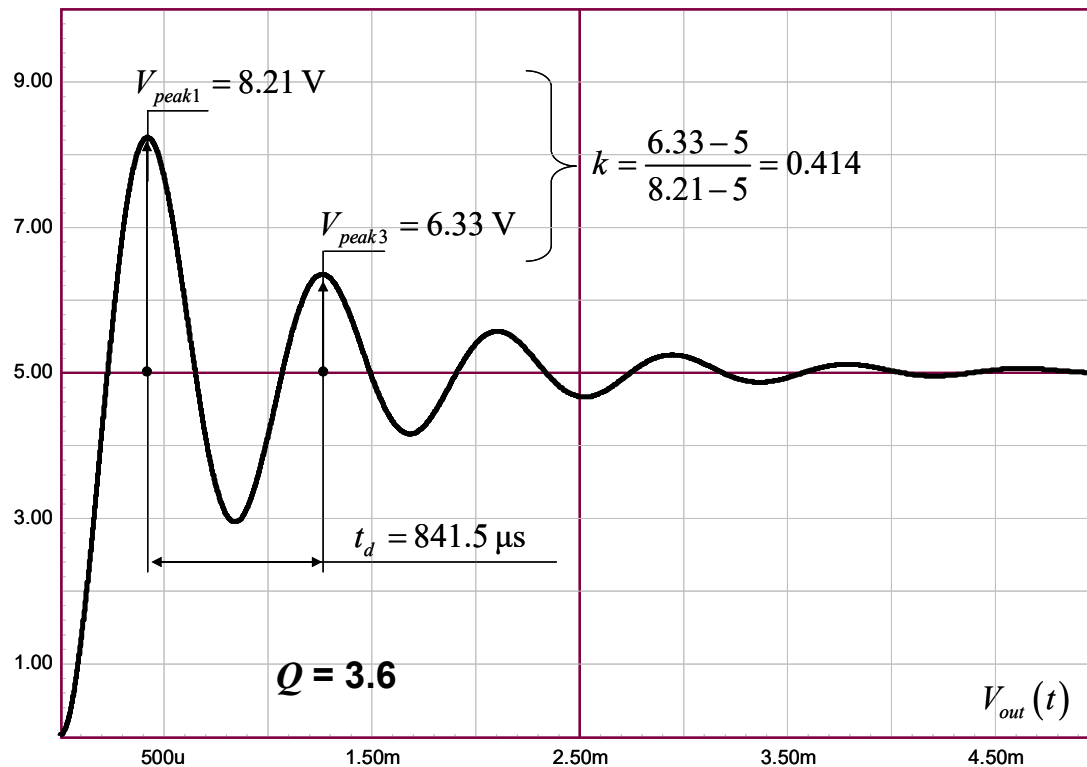
# Output Impedance and Quality Factor

□ How to get  $Q$  and  $\varphi_m$  from the available signals?



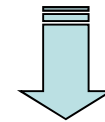You need enough signal and ringing to extract the data




Must remain small-signal!

$$Q = \sqrt{\left(\frac{\pi}{\ln k}\right)^2 + \frac{1}{4}} \quad \zeta = \frac{1}{\sqrt{\left(\frac{2\pi}{\ln k}\right)^2 + 1}} \quad f_0 = \frac{1}{t_d \sqrt{1 - \zeta^2}}$$



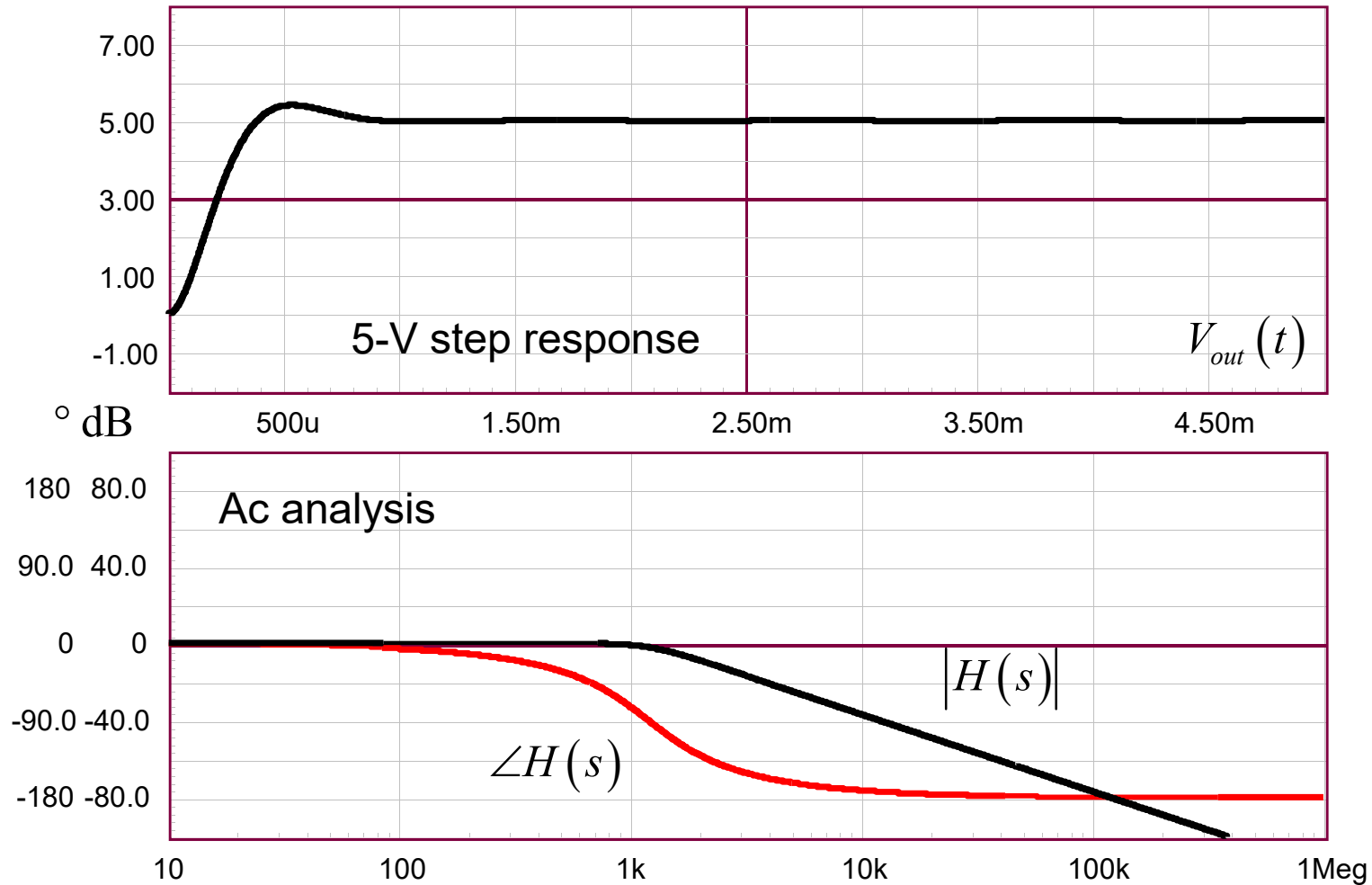
# Output Impedance and Quality Factor

- ❑ Extraction is difficult with flat ac 2<sup>nd</sup>-order responses



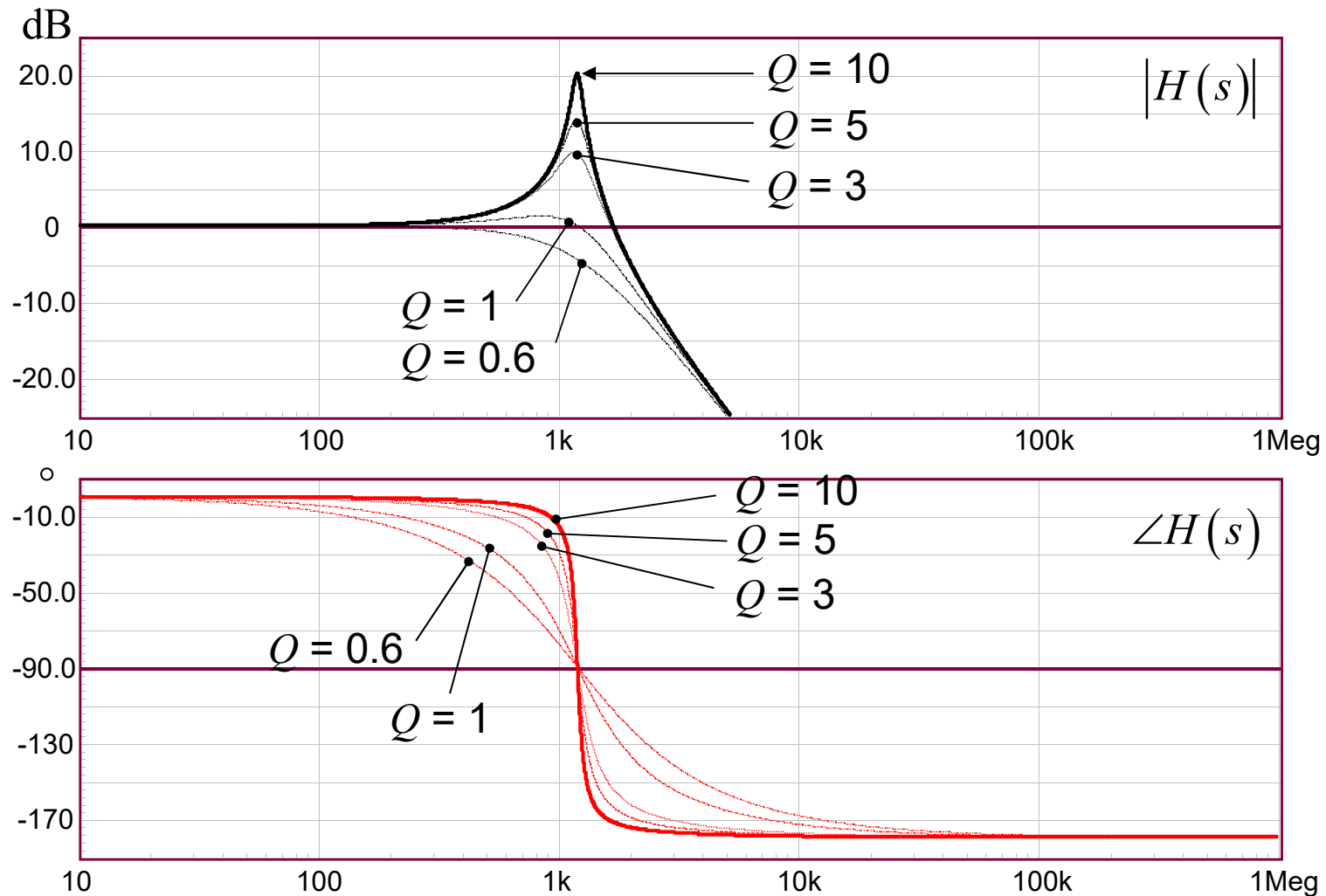
# Output Impedance and Quality Factor

- The phase drops at a different pace as  $Q$  changes



# Output Impedance and Quality Factor

- Is there a link between  $Q$  and the phase rate of change?

Group delay 

$$\tau_g = -\frac{d\phi(\omega)}{d\omega} \rightarrow [\text{s}]$$

- Let's apply the definition to a 2<sup>nd</sup>-order network:

$$H(s) = \frac{1}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \quad \xrightarrow{s = j\omega} \quad H(j\omega) = \frac{1}{\underbrace{1 - \frac{\omega^2}{\omega_0^2}}_a + j \underbrace{\frac{\omega}{\omega_0 Q}}_b}$$


$$|H(\omega)| = \sqrt{a^2 + b^2} = \frac{1}{\sqrt{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{\omega}{\omega_0 Q}\right)^2}} \quad \angle H(\omega) = \tan^{-1}\left(\frac{b}{a}\right) = \tan^{-1}\left[\frac{\omega}{\omega_0 Q} \frac{1}{\left(1 - \frac{\omega^2}{\omega_0^2}\right)}\right]$$

# Output Impedance and Quality Factor

- We can apply  $\tau_g$  definition to the argument

$$\tau_g = - \frac{d \tan^{-1} \left[ \frac{\omega}{\omega_0 Q} \left( \frac{1}{1 - \frac{\omega^2}{\omega_0^2}} \right) \right]}{d\omega} = \frac{Q\omega_0 (\omega^2 + \omega_0^2)}{Q^2\omega^4 - 2Q^2\omega^2\omega_0^2 + Q^2\omega_0^4 + \omega^2\omega_0^2}$$

$\omega = \omega_0$

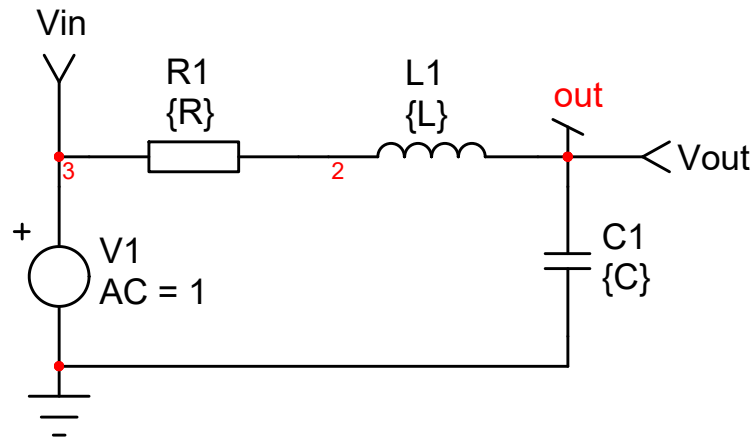

$$\tau_g = \frac{2Q}{\omega_0}$$

- At  $\omega_0$  the following formula links  $Q$  to the group delay

$$Q = \frac{\tau_g \omega_0}{2} = \tau_g \pi f_0$$

# Output Impedance and Quality Factor

- Let's apply the theory to a classical case, the *RLC* filter



parameters

$$V_p = 5$$

$$f_0 = 1.2\text{k}$$

$$L = 10\mu$$

$$C = 1 / (4 * 3.14159^2 * f_0^2 * L)$$

$$\omega_0 = (L * C)^{-0.5}$$

$$Q = 0.6$$

$$R = L * \omega_0 / Q$$

$$R_2 = 1 / (Q * C * \omega_0)$$

$$Q_1 = (\text{sqrt}(L/C)) / R$$

$$D_{\text{zeta}} = (R/2) * \text{sqrt}(C/L)$$

$$D_{\text{zeta}1} = R / (2 * L * \omega_0)$$


$$Q_3 = 1 / (2 * D_{\text{zeta}})$$

$$\text{per} = 1 / (f_0 * \text{sqrt}(1 - D_{\text{zeta}}^2))$$

$$t_p = 1 / (2 * f_0 * \text{sqrt}(1 - D_{\text{zeta}}^2))$$


- ✓ plot the ac response
- ✓ calculate the group delay
- ✓ see if we can find  $Q$

# Output Impedance and Quality Factor

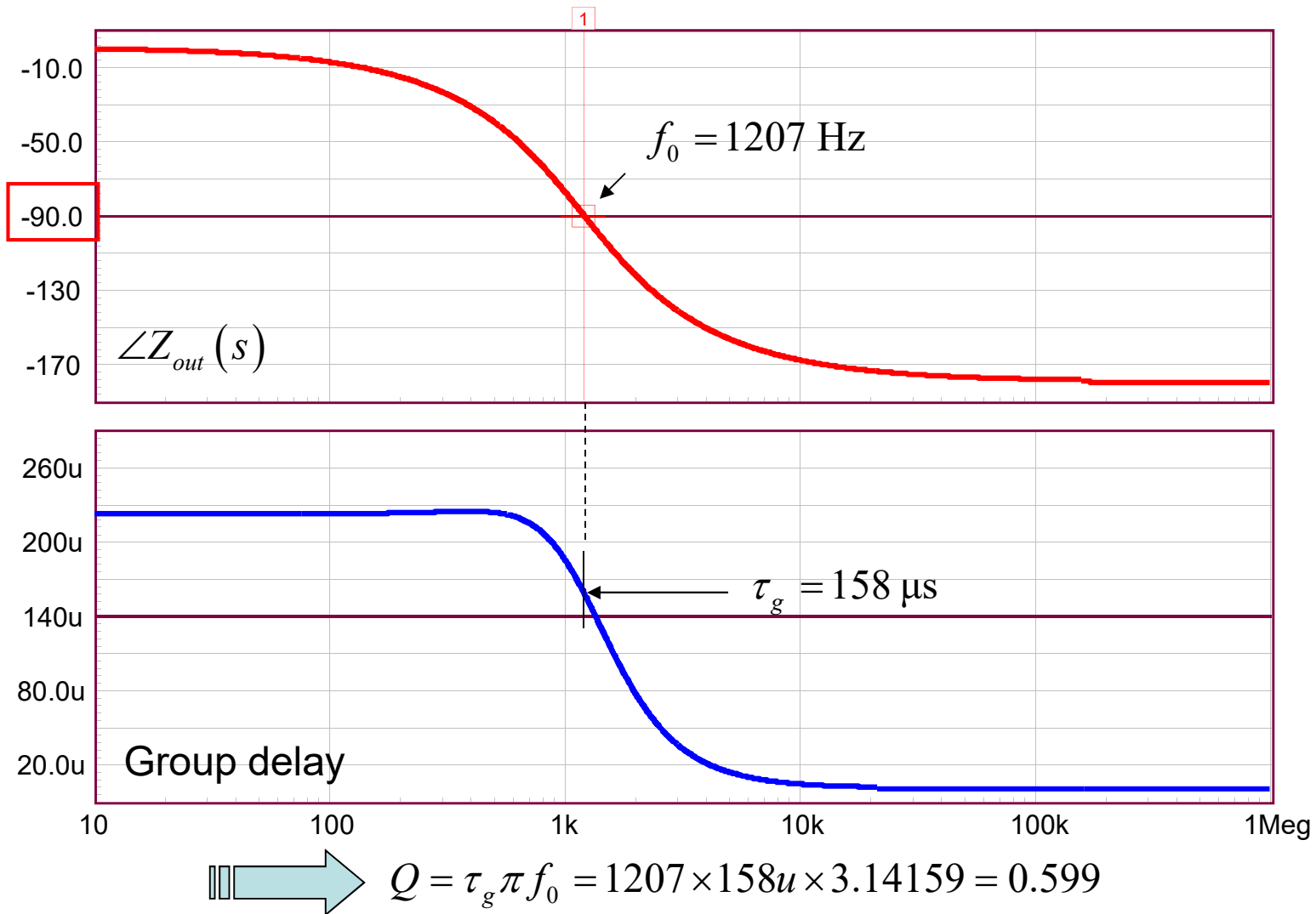

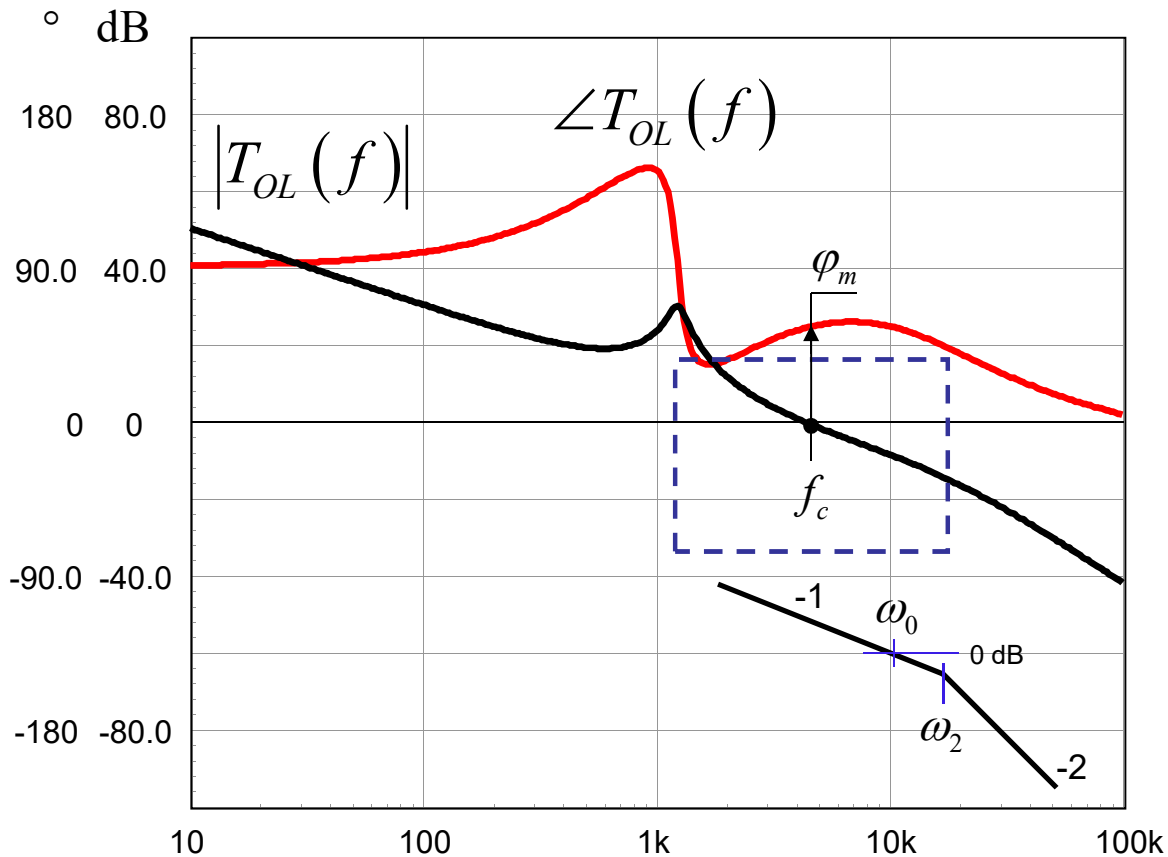
# Output Impedance and Quality Factor

- Knowing  $Q$  can also lead us to the phase margin  $\varphi_m$



Open-loop ac analysis

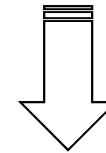Approximation of  $T(s)$   
around  $f_c$




$$T_{OL}(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)}$$



# Output Impedance and Quality Factor

- If we consider the open-loop gain around  $f_c$  only...

$$T_{OL}(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

Closed-loop  
  
 Unity return

$$\frac{T_{OL}(s)}{1 + T_{OL}(s)} = \frac{1}{\frac{s^2}{\omega_0\omega_2} + \frac{s}{\omega_0} + 1}$$

$$\frac{1}{\frac{s^2}{\omega_0\omega_2} + \frac{s}{\omega_0} + 1} = \frac{1}{\frac{s^2}{\omega_c^2} + \frac{s}{\omega_c Q_c} + 1}$$

Identify



$$Q_c = \sqrt{\frac{\omega_0}{\omega_2}}$$

$$\omega_c = \sqrt{\omega_0\omega_2}$$

↑  
Closed-loop data

↑  
Open-loop data

- We want to link  $Q_c$  and the crossover frequency

$$T_{OL}(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)}$$



$$\omega_0 = Q_c^2 \omega_2$$

$$T_{OL}(s) = \frac{1}{\left(\frac{s}{Q_c^2 \omega_2}\right)\left(1 + \frac{s}{\omega_2}\right)}$$






# Output Impedance and Quality Factor

- Calculate the  $T_{OL}$  magnitude at crossover with  $Q_c$  in:

$$\left| \frac{1}{\left(\frac{j\omega_c}{Q_c^2\omega_2}\right)\left(1 + \frac{j\omega_c}{\omega_2}\right)} \right| = \frac{Q_c^2\omega_2^2}{\sqrt{\omega_c^2\omega_2^2 + \omega_c^4}}$$



Solve  $\omega_c$  

$$|T_{OL}(\omega_c)| = 1 \quad \omega_c = \frac{\omega_2\sqrt{\left(\sqrt{1+4Q_c^4}-1\right)}}{\sqrt{2}}$$

- Derive the argument of  $T_{OL}$ , simplify it:

$$\arg T_{OL}(s) = \arg \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)} = \arg \left( \frac{jQ_c^2\omega_2^2}{-\omega_c\omega_2 - j\omega_c^2} \right) = \arg \left( -\frac{1}{-j\frac{\omega_c\omega_2}{Q_c^2\omega_2^2} + \frac{\omega_c^2}{Q_c^2\omega_2^2}} \right)$$


$$\arg T_{OL}(s) = \arg(-1) - \tan^{-1} \left( -\frac{\frac{\omega_c\omega_2}{Q_c^2\omega_2^2}}{\frac{\omega_c^2}{Q_c^2\omega_2^2}} \right) = -\pi - \tan^{-1} \left( -\frac{\omega_2}{\omega_c} \right)$$
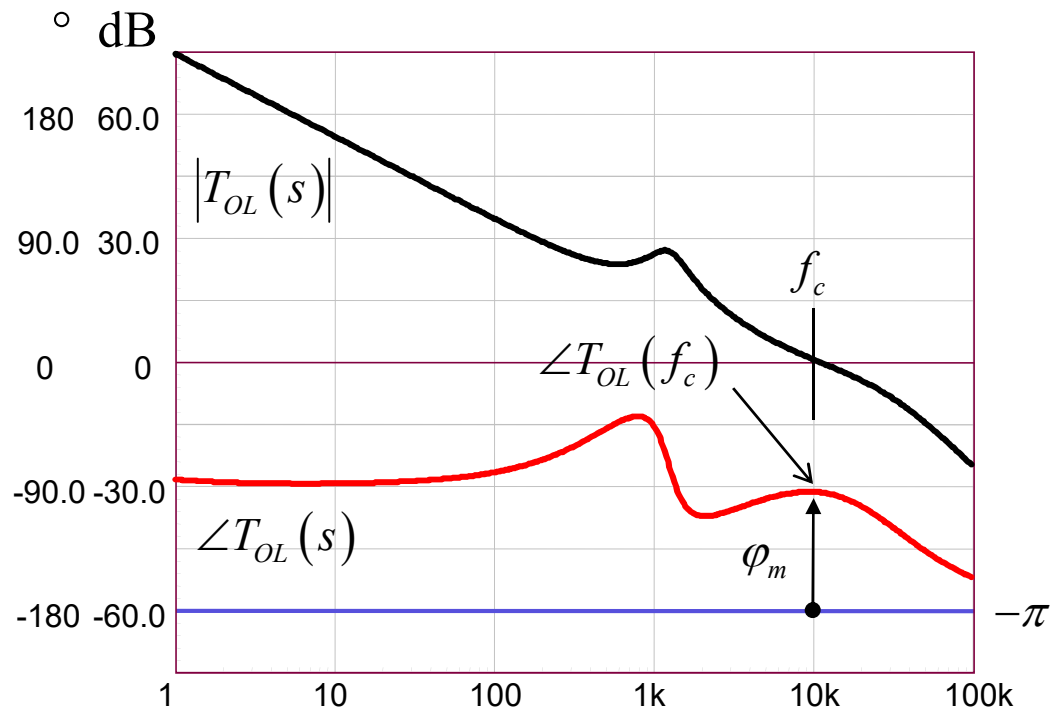
# Output Impedance and Quality Factor

□ If we substitute  $\omega_c$  by its definition, we have:

$$\arg T_{OL}(s) = -\pi - \tan^{-1} \left( -\sqrt{\frac{2}{\sqrt{(1+4Q_c^4)}-1}} \right) = -\pi + \tan^{-1} \left( \sqrt{\frac{2}{\sqrt{(1+4Q_c^4)}-1}} \right)$$



$$\angle T_{OL}(f_c) - \varphi_m = -\pi$$

$$\varphi_m = \angle T_{OL}(f_c) + \pi$$





$$\varphi_m = \tan^{-1} \left( \sqrt{\frac{2}{\sqrt{(1+4Q_c^4)}-1}} \right)$$

# Output Impedance and Quality Factor

- We can now extract the closed-loop quality coefficient:



$$Q_c = \frac{\sqrt[4]{1 + \tan(\varphi_m)^2}}{\tan(\varphi_m)} = \frac{\sqrt{\cos(\varphi_m)}}{\sin(\varphi_m)}$$
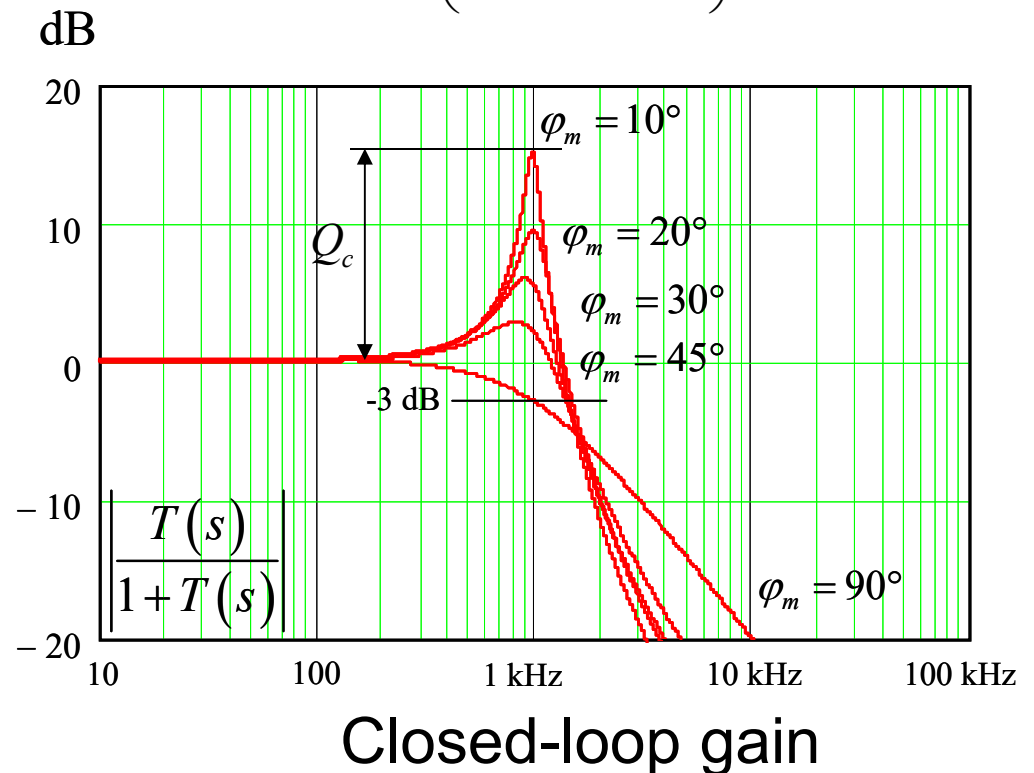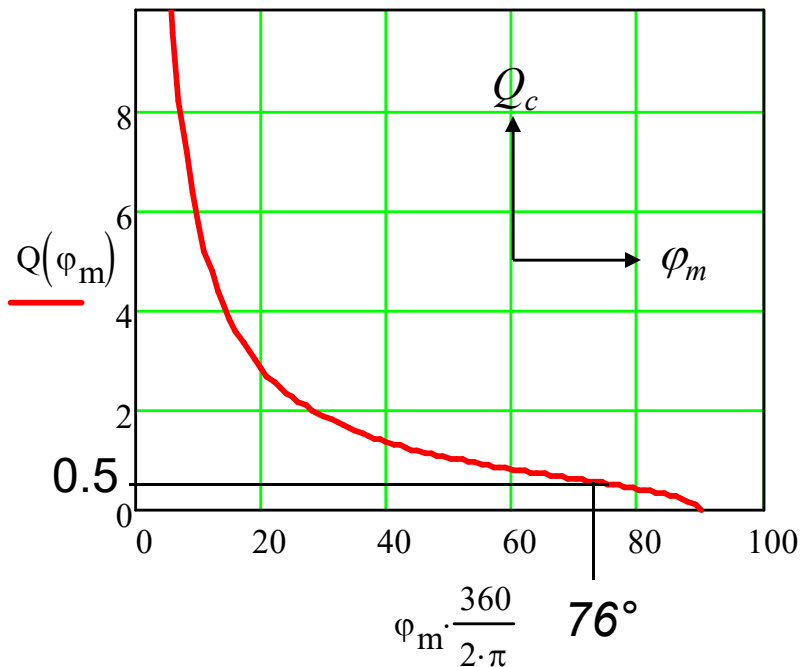
$$\Rightarrow \varphi_m = \cos^{-1} \left( \frac{\sqrt{4Q_c^4 + 1} - 1}{2Q_c^2} \right)$$


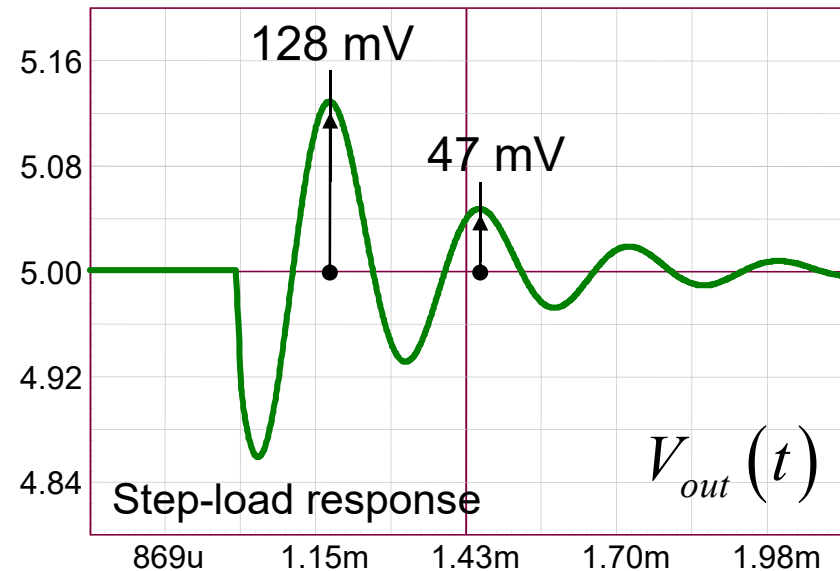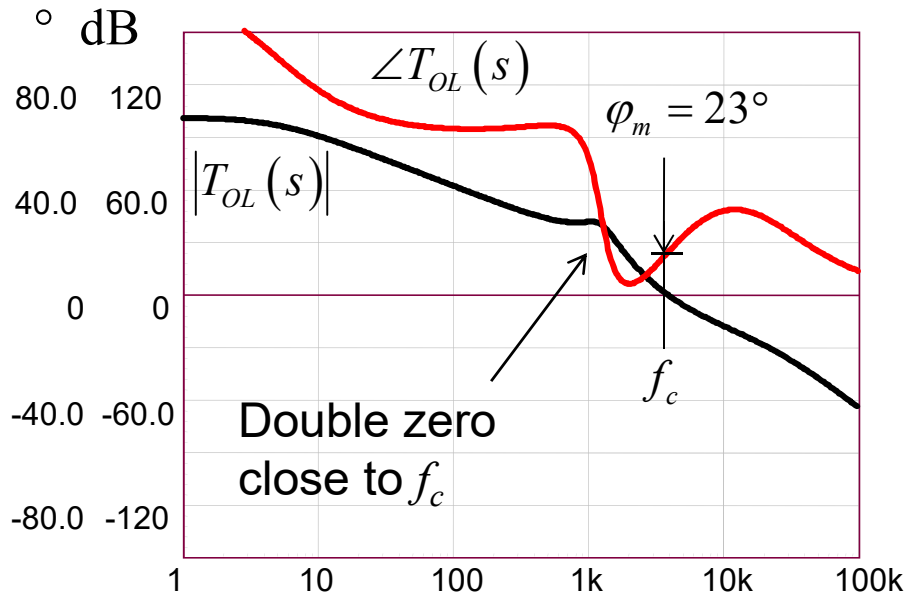
# Output Impedance and Quality Factor

- ❑ The formula considers the vicinity of  $f_c$  only: precision?




$$\Rightarrow Q_c = \sqrt{\left(\frac{\pi}{\ln\left(\frac{47}{128}\right)}\right)^2 + \frac{1}{4}} = 3.1$$

$$\varphi_m = \cos^{-1}\left(\frac{\sqrt{4Q_c^4 + 1} - 1}{2Q_c^2}\right) \approx 18^\circ$$

"Revisiting the Response of Closed Loop of PWM Converters", S. Ben-Yaakov, IEEE Apec 2008
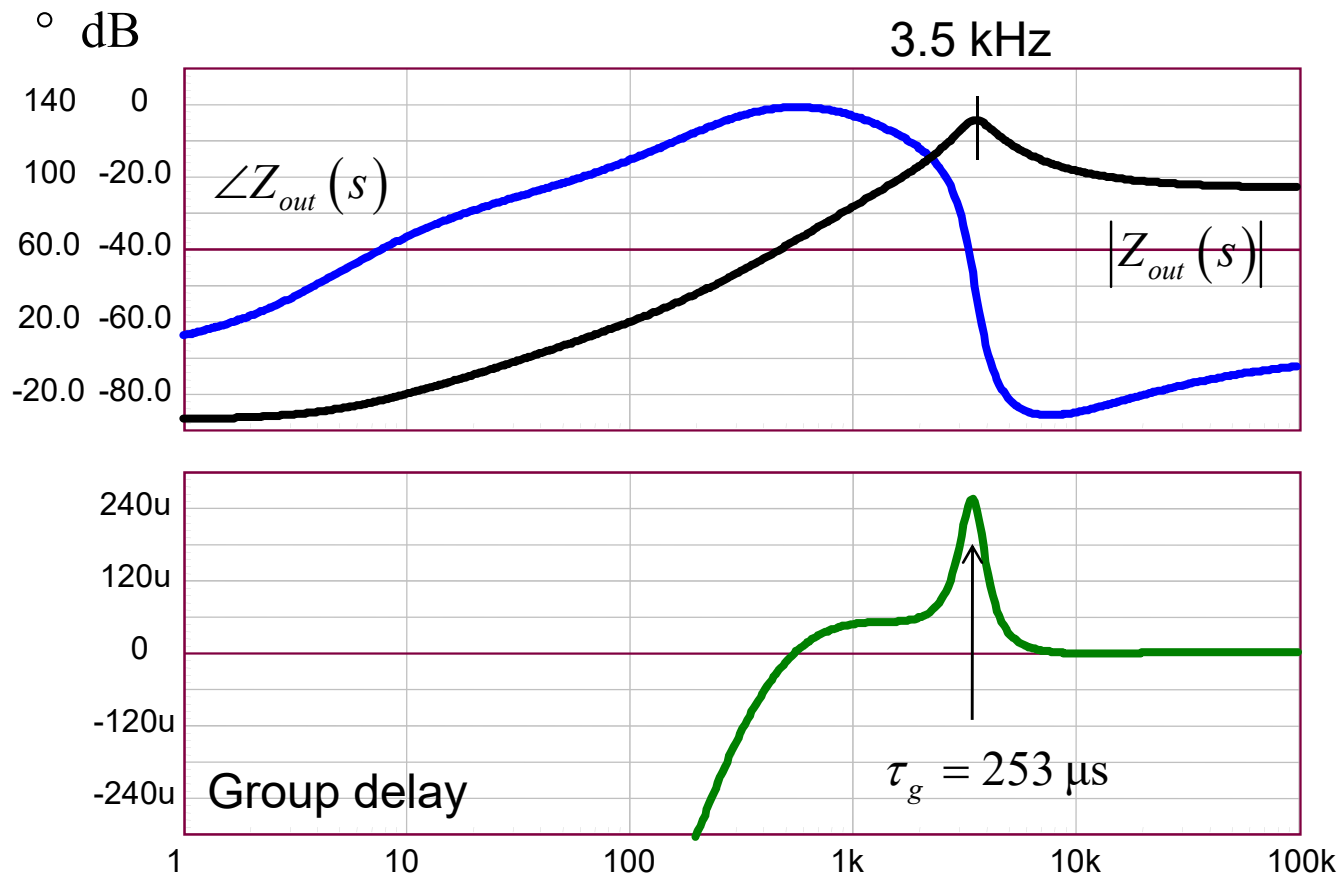
# Output Impedance and Quality Factor


- We can ac sweep the output impedance also and check  $\tau_g$



$$Q = \tau_g \pi f_0 = 3.5k \times 253u \times 3.14159 \approx 2.8 \implies \varphi_m \approx 20.4^\circ$$
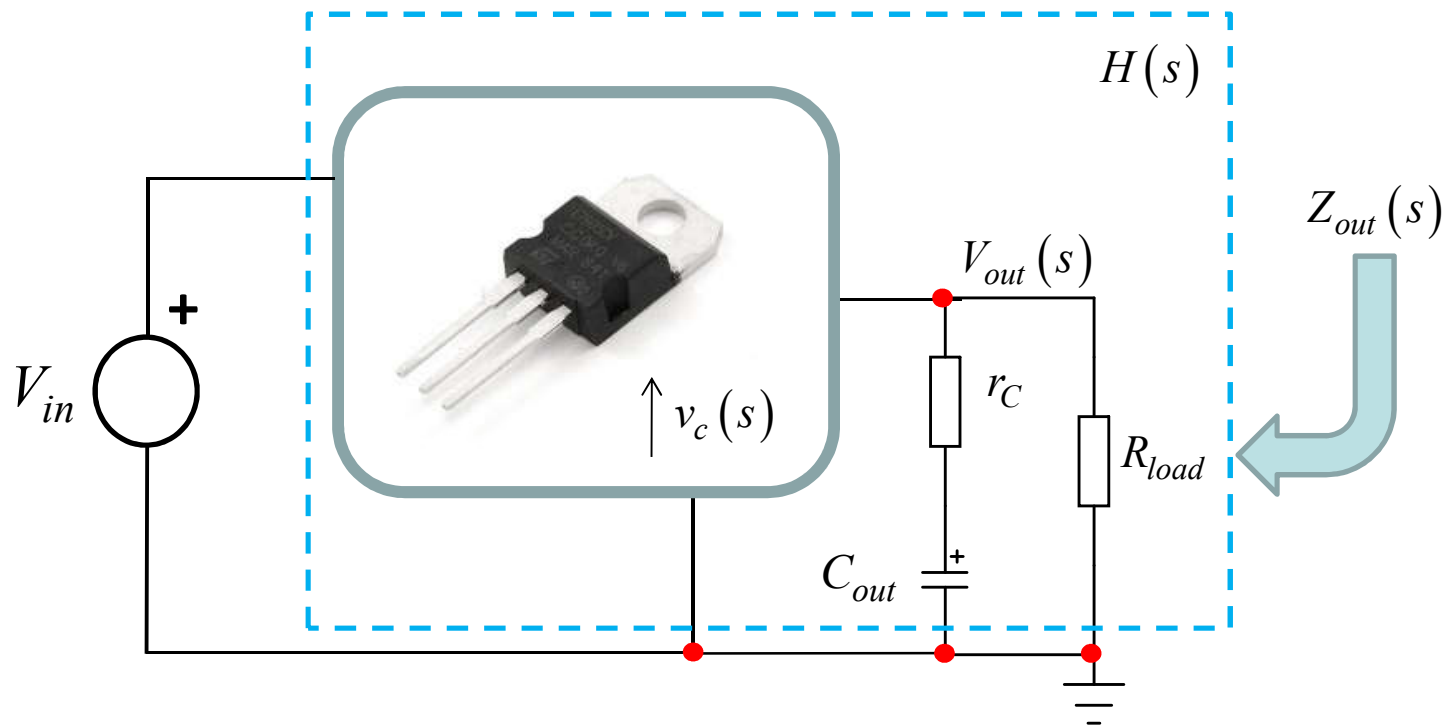
# Output Impedance and Quality Factor

- We can apply the technique to simple linear regulators




- You have no means to perform open-loop analysis
- Plot its output impedance with a network analyzer...

S. Sandler, C. Hymowitz, "New Technique for Non-Invasive Testing of Regulator Stability", PET Magazine, September 2011
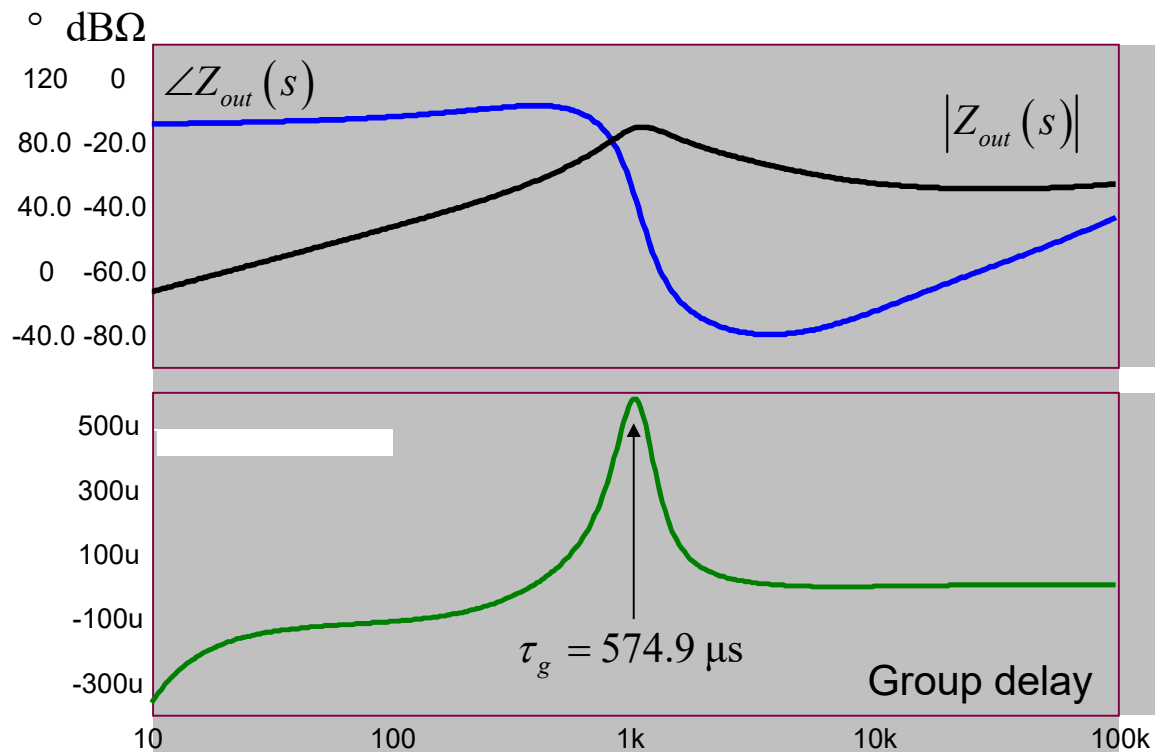
# Output Impedance and Quality Factor

- Plot magnitude and phase of  $Z_{out}$  and compute  $\tau_g$




$$Q = \tau_g \pi f_0 = 1k \times 574.9u \times 3.14159 = 1.8$$

$$\varphi_m = \cos^{-1} \left( \frac{\sqrt{4Q^4 + 1} - 1}{2Q^2} \right) = \cos^{-1} \left( \frac{\sqrt{4 \times 1.8^4 + 1} - 1}{2 \times 1.8^2} \right) = \cos^{-1} (857m) \approx 31^\circ$$
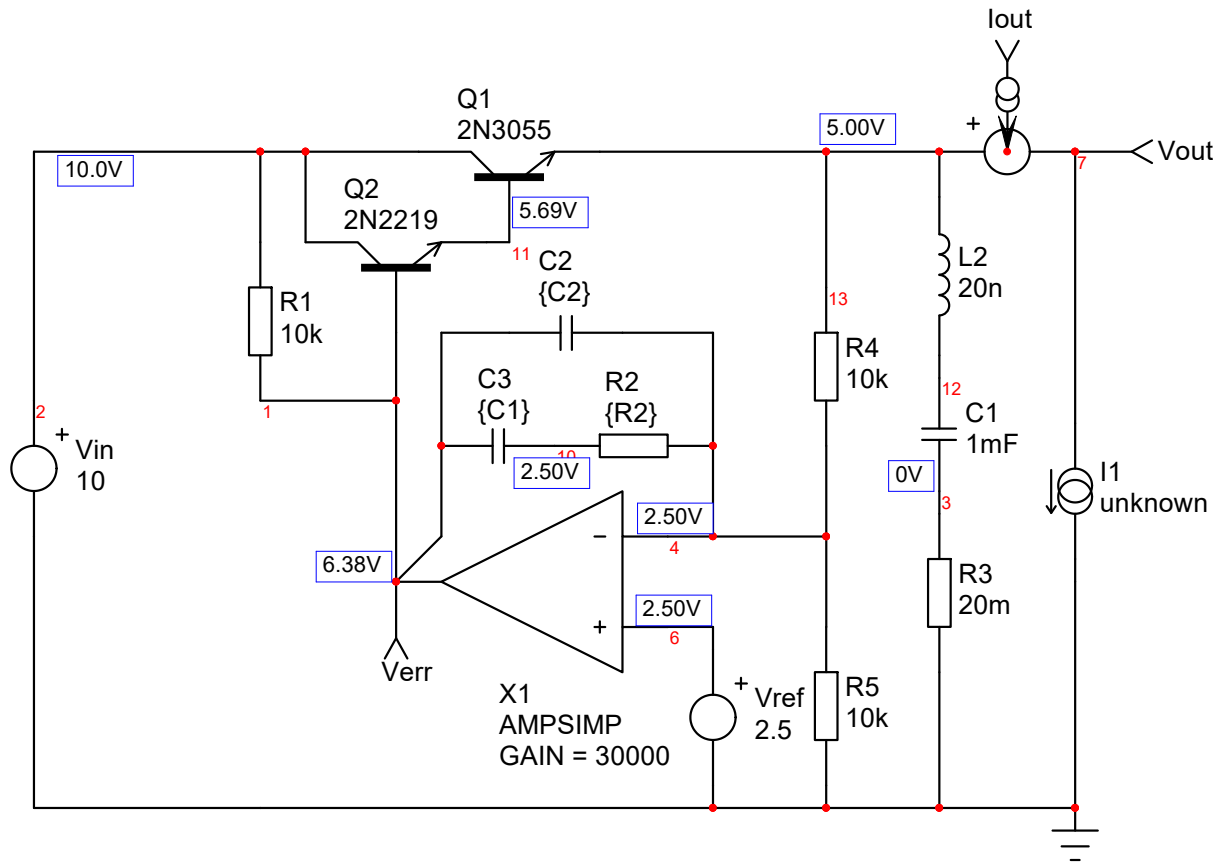
# Output Impedance and Quality Factor

- The LDO circuit is made of the following elements




- We can open its loop and plot the open-loop gain  $T_{OL}(s)$



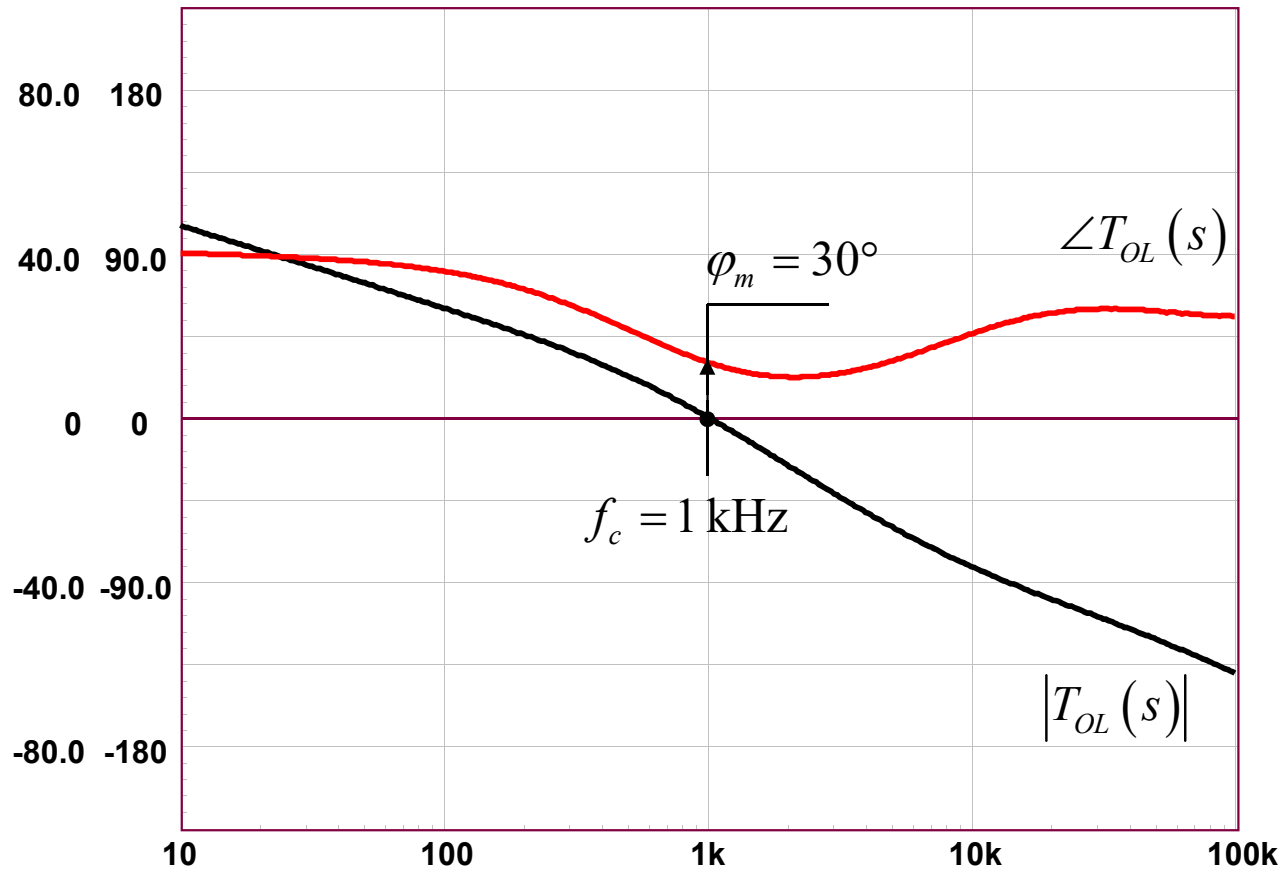
# Output Impedance and Quality Factor

- The open-loop plot confirms the experimental results



# Output Impedance and Quality Factor

- The phase margin is increased to 60°

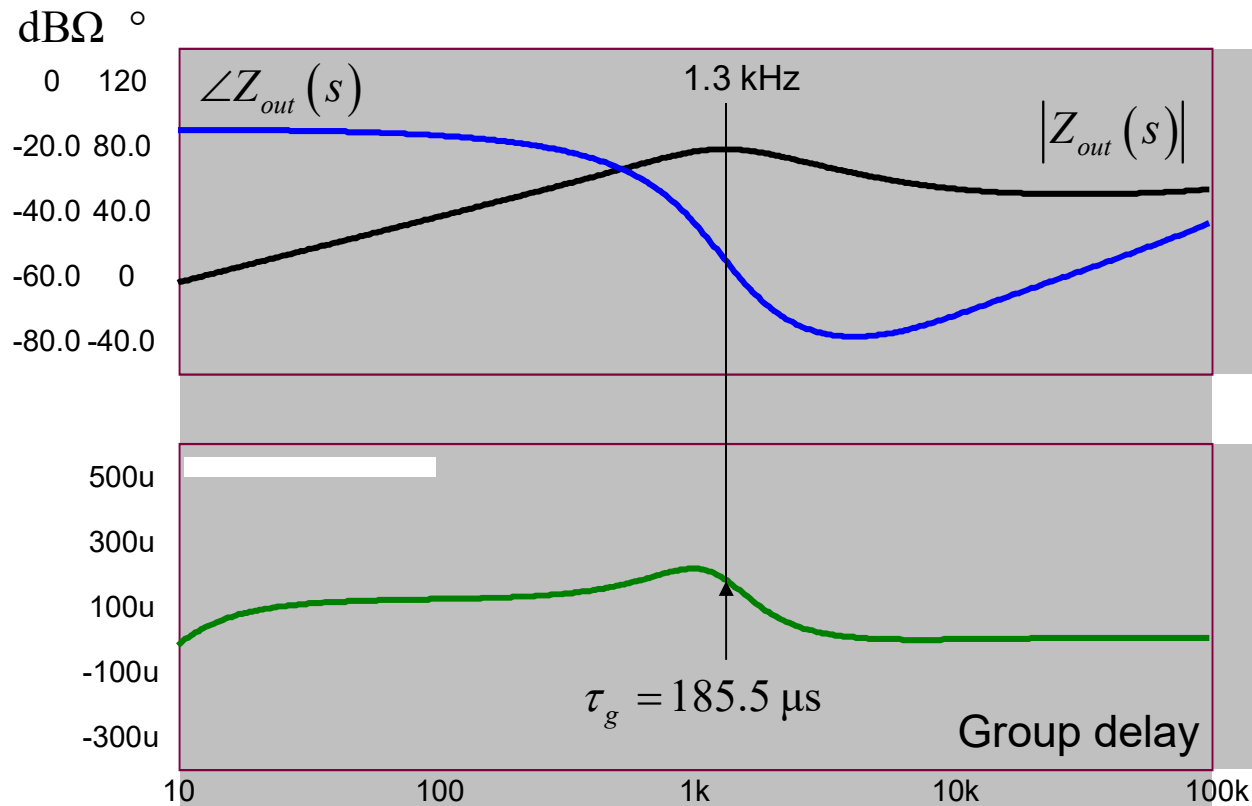

$$Q = \tau_g \pi f_0 = 1.3k \times 185.5u \times 3.14159 \approx 0.76$$

$$\varphi_m = \cos^{-1} \left( \frac{\sqrt{4Q^4 + 1} - 1}{2Q^2} \right) = \cos^{-1} \left( \frac{\sqrt{4 \times 0.76^4 + 1} - 1}{2 \times 0.76^2} \right) = \cos^{-1} (457m) \approx 63^\circ$$


# Course Agenda

- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?**
- Gain Margin is not Enough



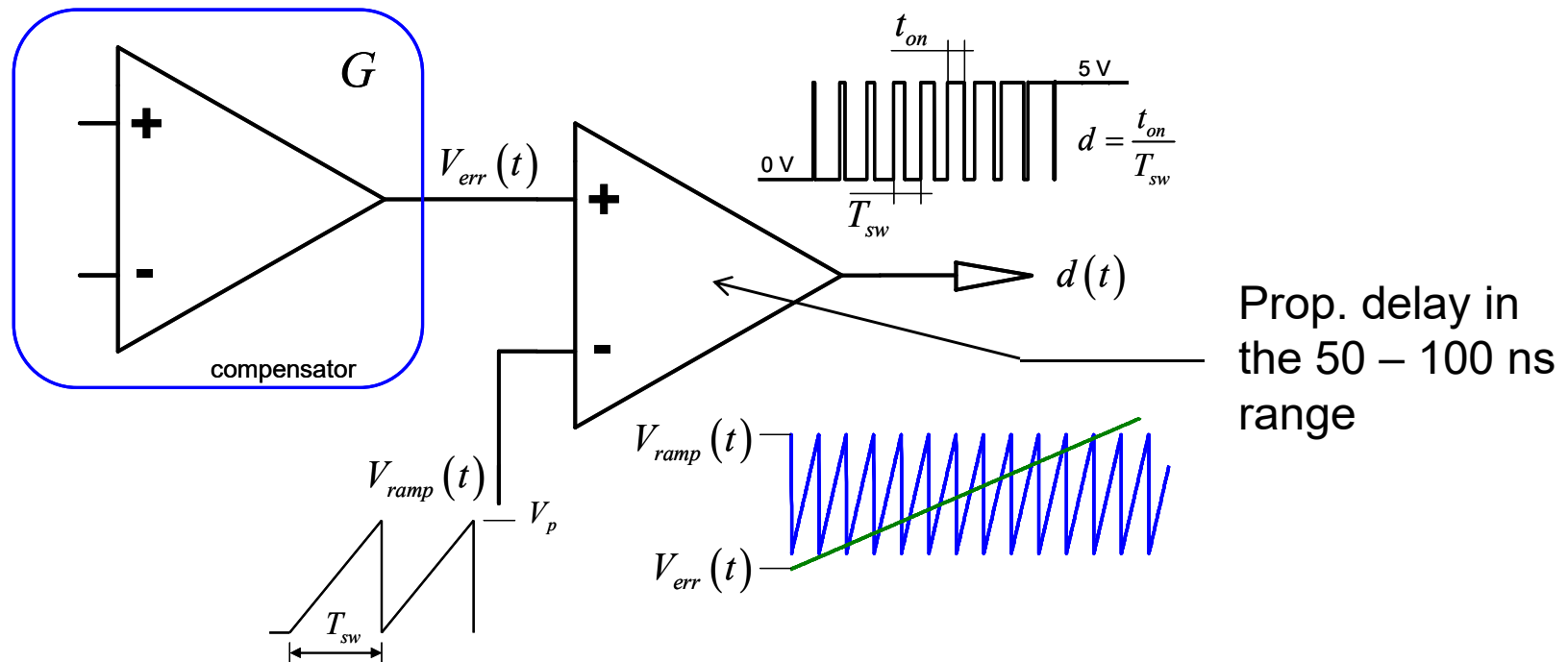
# Considering a Delay in the Loop

- ❑ Before a decision is actually executed, a delay occurs
- ❑ The delay can be digital (computation time) or analogue
- ❑ A typical delay is the duty-ratio conversion in a VM converter



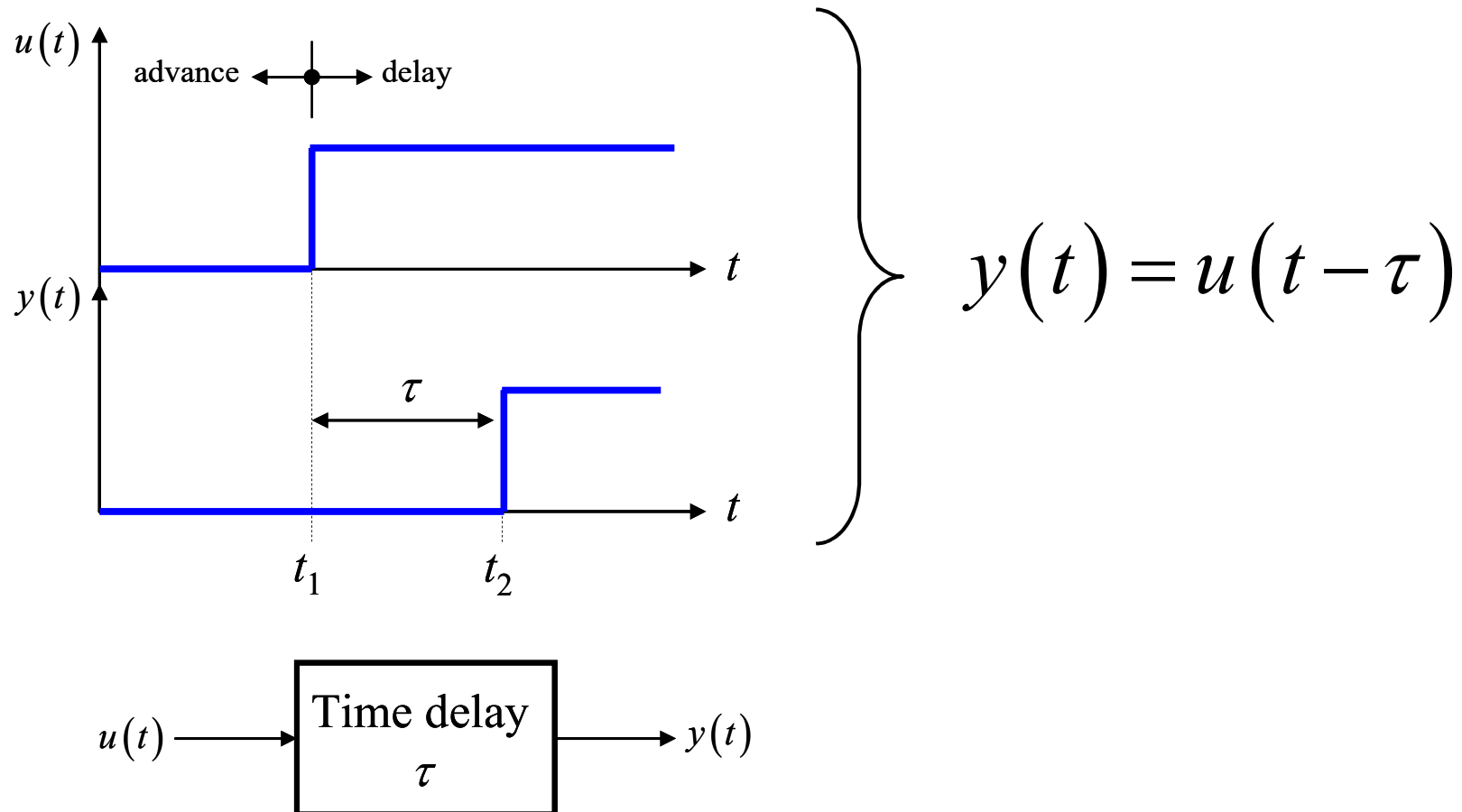
# A Delay is a Time-Domain Shift

- The output signal is the input signal that occurred  $\tau$  s before


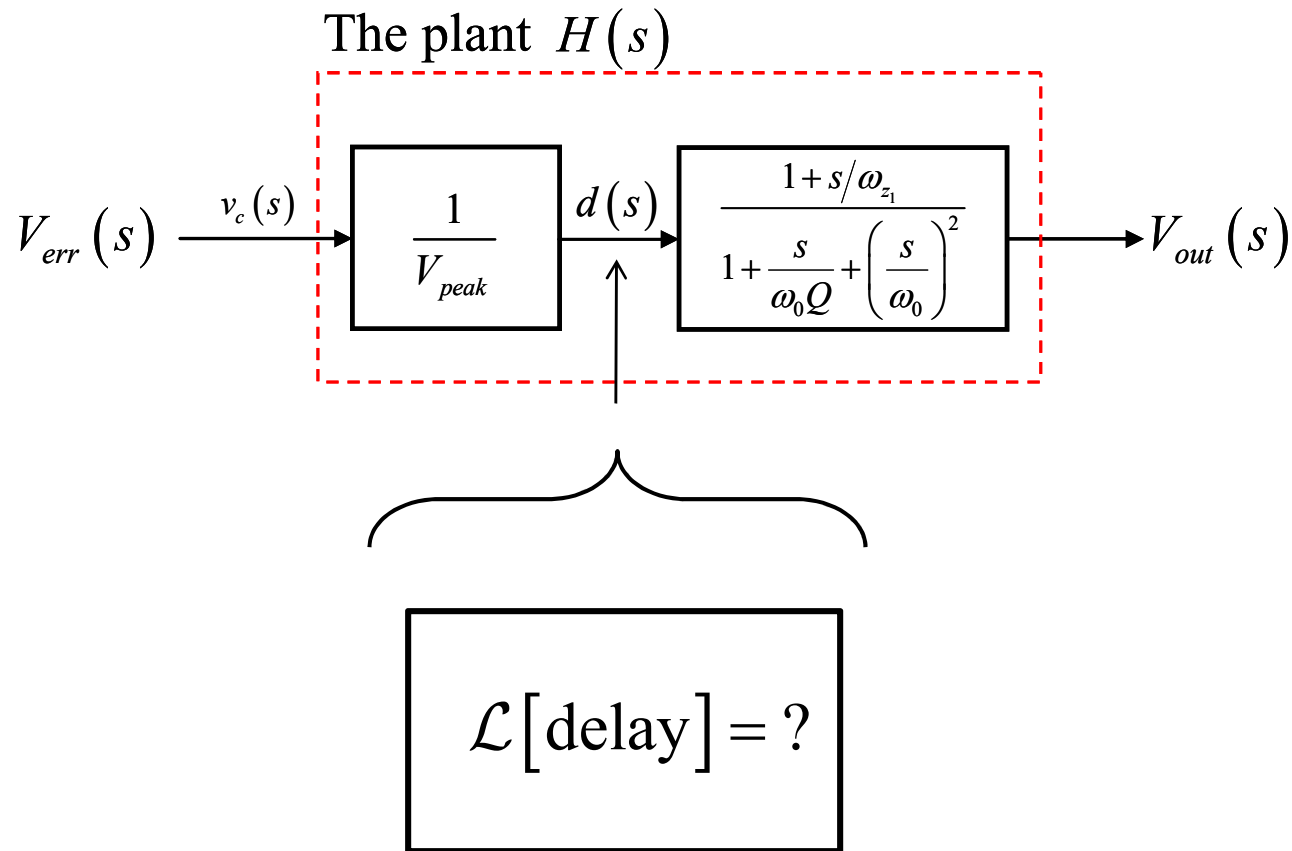
# Deriving the Delay

- To account for the delay, we need its Laplace expression




# Deriving the Delay

- To account for the delay, we need its Laplace expression

$$\mathcal{L}[y(t)] = \mathcal{L}[u(t-\tau)] \quad \longrightarrow \quad ?$$

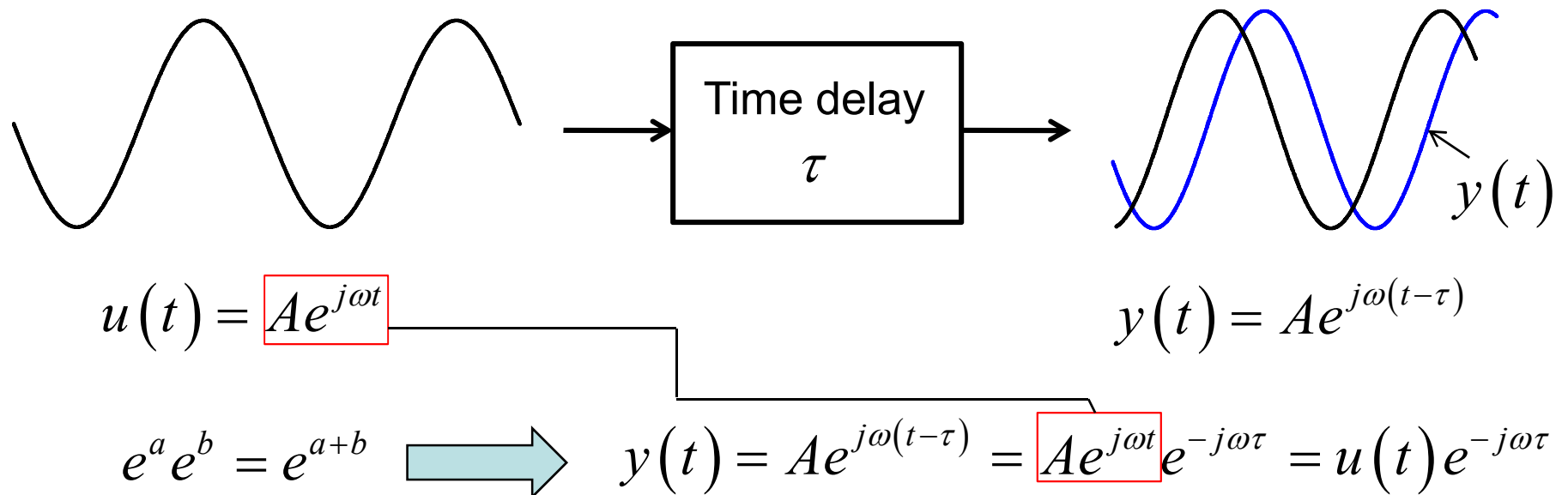- Let's start with a sinewave phasor expression



## Deriving the Delay


- Let's take the Laplace transform of the new expression

$$Y(s) = U(s)e^{-s\tau} \quad \longrightarrow \quad \frac{Y(s)}{U(s)} = \boxed{e^{-s\tau}} \xrightarrow{s=j\omega} \frac{Y(j\omega)}{U(j\omega)} = e^{-j\omega\tau}$$

- Euler phasor formula uses the argument as the exponent

$$\left. \begin{array}{l} e^{-j\omega\tau} \rightarrow e^{j\phi} \end{array} \right\} \begin{array}{l} \arg e^{-j\omega\tau} = -\omega\tau \\ |e^{-j\omega\tau}| = 1 \end{array}$$


- A delay block is a simple delay line!

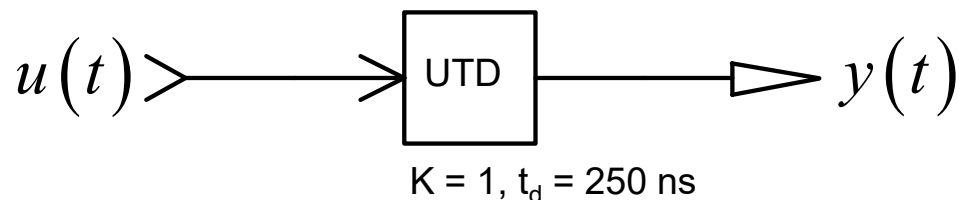


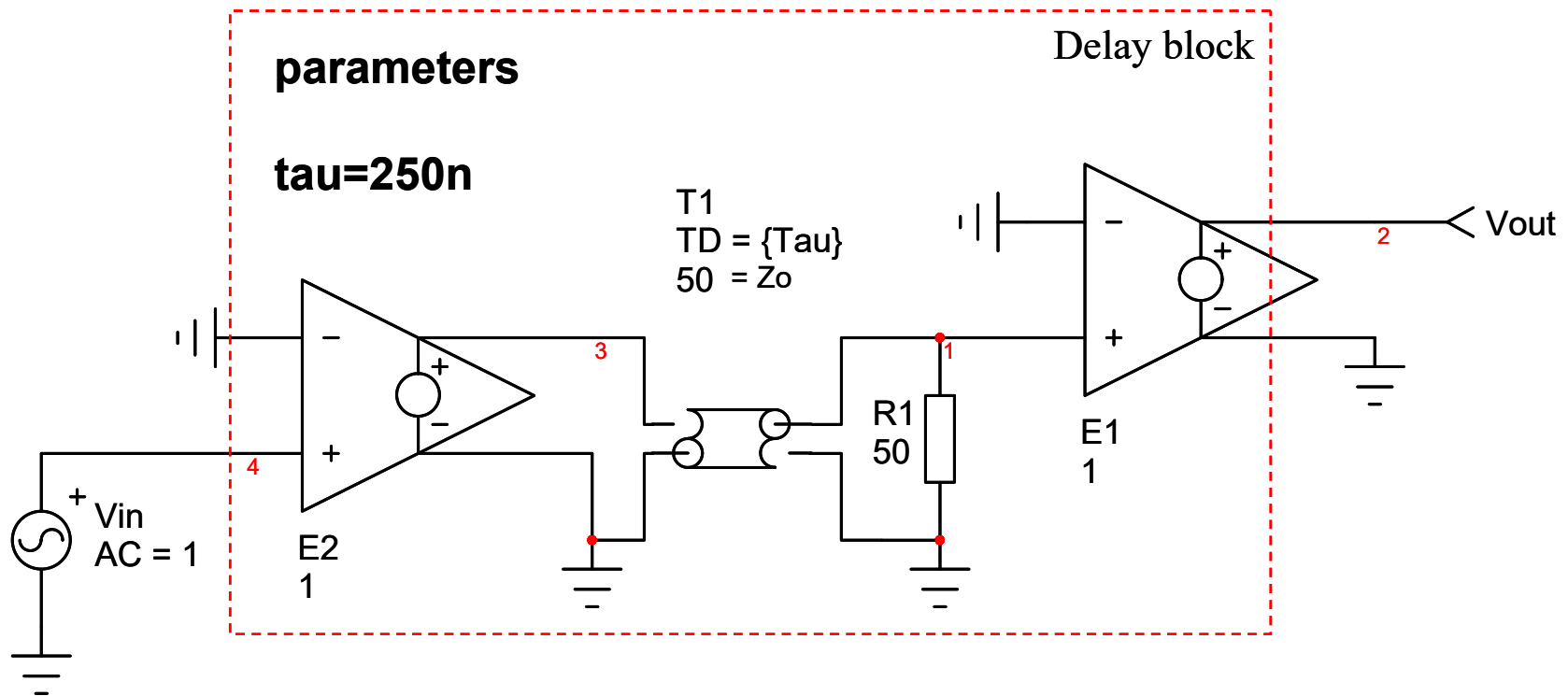
# Building the Delay

- ❑ A delay line can time-shift the input signal




- ❑ Best simulation practice is to buffer the input and the output

D. Adar, S. Ben-Yaakov, "Generic Average Modeling and Simulation of Discrete Controllers", APEC Anaheim, 2001
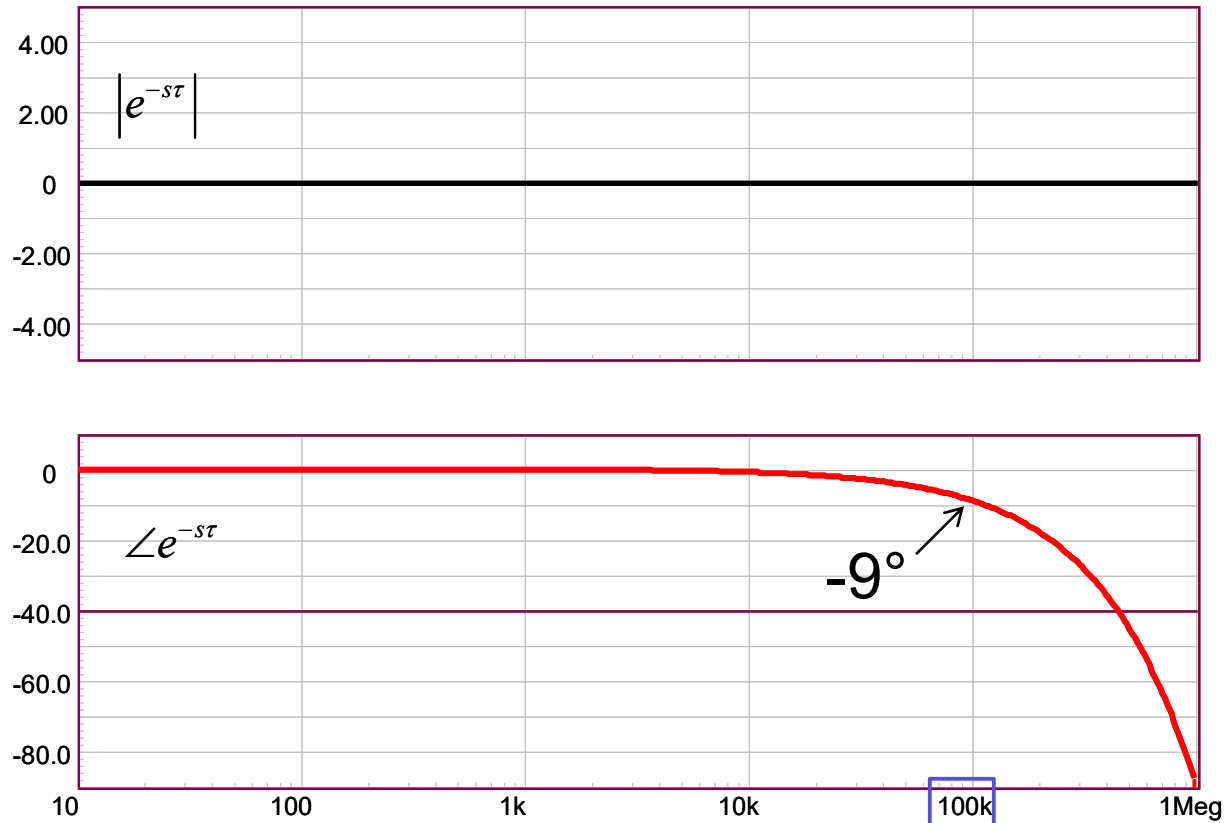
# Building the Delay

- A Bode plot confirms the 0-dB magnitude over frequency




Magnitude is flat

$$\varphi_{100\text{kHz}} = -\omega\tau = -100k \times 6.28 \times 250n \times \frac{180}{\pi} = -9^\circ$$
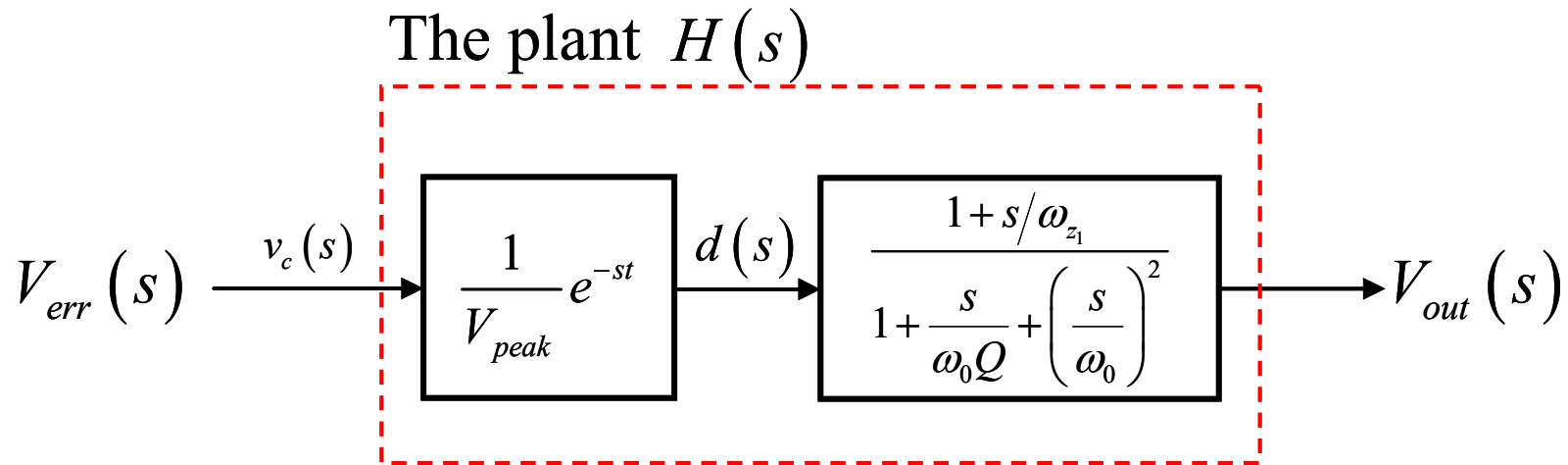
# Adding the Delay in the Laplace Domain

- We can now update our transmission chain with the delay



$$H(s) = \frac{e^{-s\tau}}{V_{peak}} \frac{1 + s/\omega_{z_1}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

# Adding the Delay in the Laplace Domain

- ❑ How do you deal with the term  $e^{-st}$  in the transfer function?
- ❑ You don't: replace it with a poles/zeros combination!
- A pole will bring phase shift as frequency increases

$$\frac{1}{1 + s/\omega_\tau} \longrightarrow \arg = -\tan^{-1}\left(\frac{\omega}{\omega_\tau}\right)$$


- ❑ But you still need to compensate the transmittance decrease
- A zero will do but now, all is neutralized!

$$\left. \frac{1 + s/\omega_\tau}{1 + s/\omega_\tau} \right\} \quad \text{mag} = \frac{\sqrt{1 + \left(\frac{\omega}{\omega_\tau}\right)^2}}{\sqrt{1 + \left(\frac{\omega}{\omega_\tau}\right)^2}} = 1 \quad \arg = \tan^{-1}\left(\frac{\omega}{\omega_\tau}\right) - \tan^{-1}\left(\frac{\omega}{\omega_\tau}\right) = 0$$
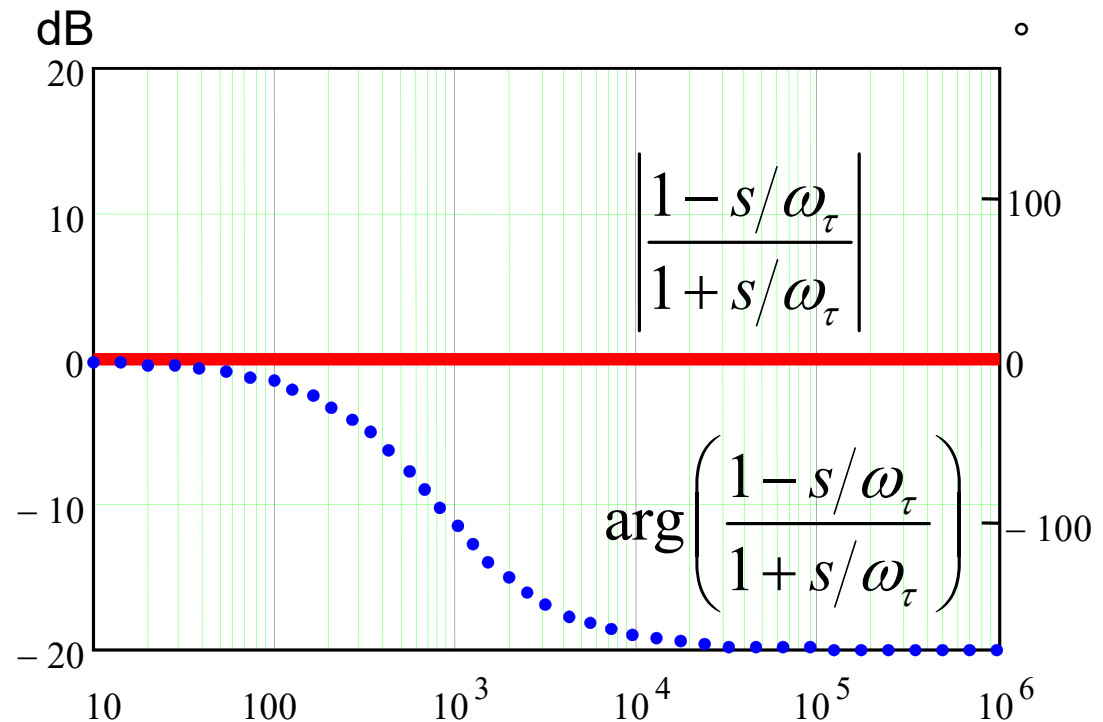
# Calling the RHP Zero for Help

- Replacing the LHP zero by a RHP zero does the job
- ❖ Both pole and zero magnitude neutralize each other
- ❖ The RHPZ phase lags and cumulates with that of the pole

$$e^{-st} \approx \frac{1 - s/\omega_\tau}{1 + s/\omega_\tau}$$



# Mapping the Delay to the Pole/Zero Position

□ Both arguments must be equal:

$$\arg(e^{-s\tau}) = \arg\left(\frac{1-s/\omega_\tau}{1+s/\omega_\tau}\right) \implies -\omega\tau = \arg(1-s/\omega_\tau) - \arg(1+s/\omega_\tau)$$

□ Replacing  $s$  by  $j\omega$ :

$$-\omega\tau = \tan^{-1}\left(-\frac{\omega}{\omega_\tau}\right) - \tan^{-1}\left(\frac{\omega}{\omega_\tau}\right) = -2 \tan^{-1}\left(\frac{\omega}{\omega_\tau}\right)$$

□ Use the arctangent Taylor series equivalent:

$$\tan^{-1} x \approx x - \frac{x^3}{3} + \frac{x^5}{5} + \dots \implies -\omega\tau \approx -2 \left[ \frac{\omega}{\omega_\tau} - \frac{\left(\frac{\omega}{\omega_\tau}\right)^3}{3} + \frac{\left(\frac{\omega}{\omega_\tau}\right)^5}{5} \right] \approx 0$$

# We Have the Padé Approximation


- Solving for  $\omega\tau$  gives us...

$$\omega_\tau = \frac{2}{\tau}$$

- Substituting  $\omega\tau$  in our first expression

$$e^{-s\tau} \approx \frac{1 - \frac{s\tau}{2}}{1 + \frac{s\tau}{2}}$$



Henri Padé  
1863-1953 

- This is the 1<sup>st</sup>-order Padé approximant of an exponential


$$e^x \approx \frac{1 + \frac{x}{2}}{1 - \frac{x}{2}} \quad \xrightarrow{\text{2nd-order}} \quad e^x \approx \frac{1 + \frac{1}{2}x + \frac{1}{12}x^2}{1 - \frac{1}{2}x + \frac{1}{12}x^2}$$

[http://en.wikipedia.org/wiki/Padé\\_approximant](http://en.wikipedia.org/wiki/Padé_approximant)


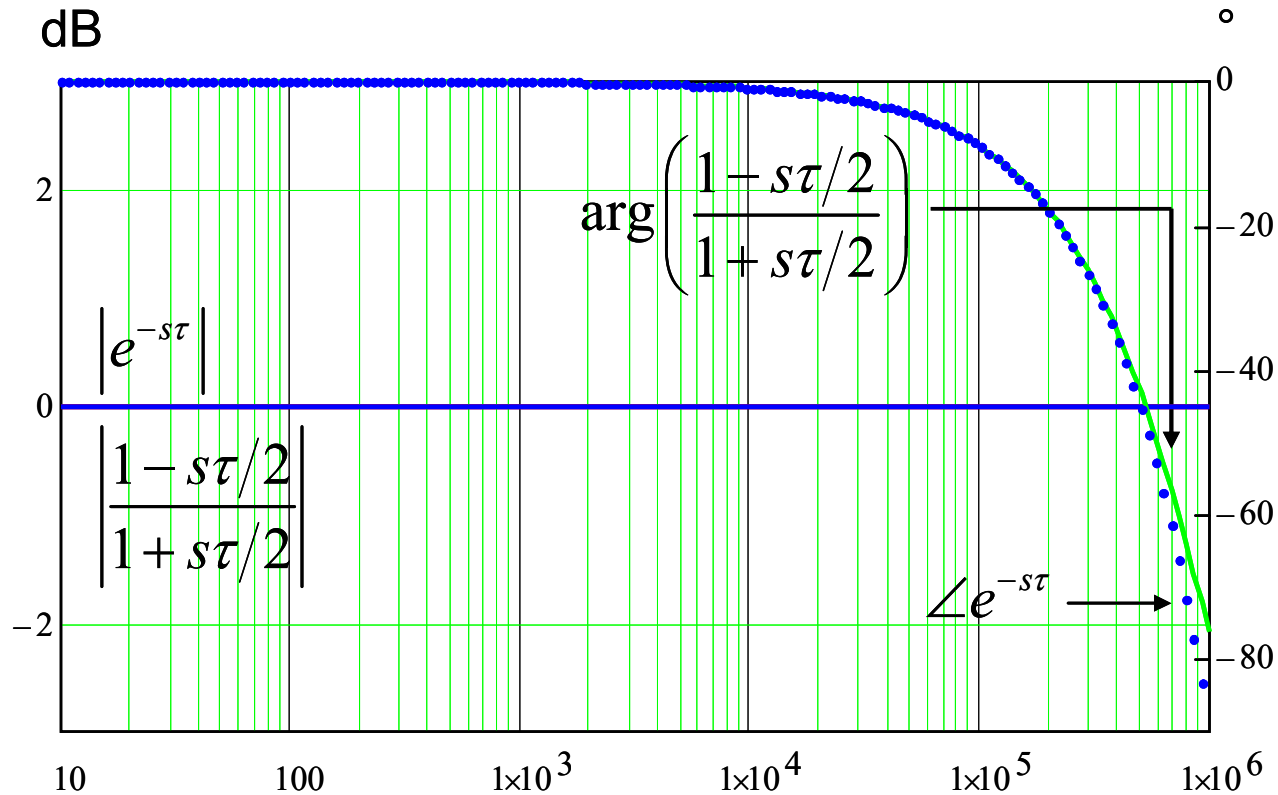
# Padé Approximant Frequency Response

- When frequency increases, a phase deviation occurs




➡ Use higher order approximants to improve precision



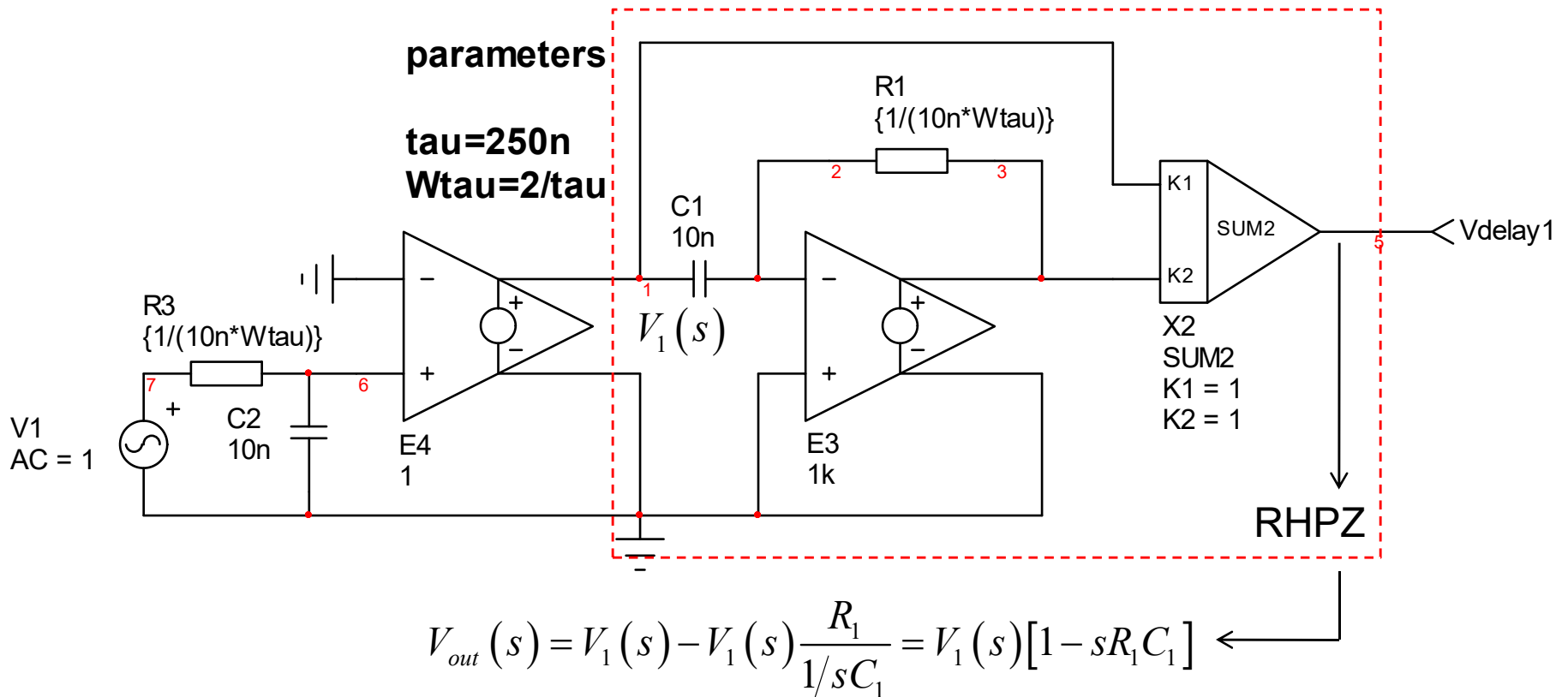
# How to Avoid the Delay Line?

- ❑ A delay line adds computational burden in simulations
- ❑ Is there any simpler circuit that could be used?


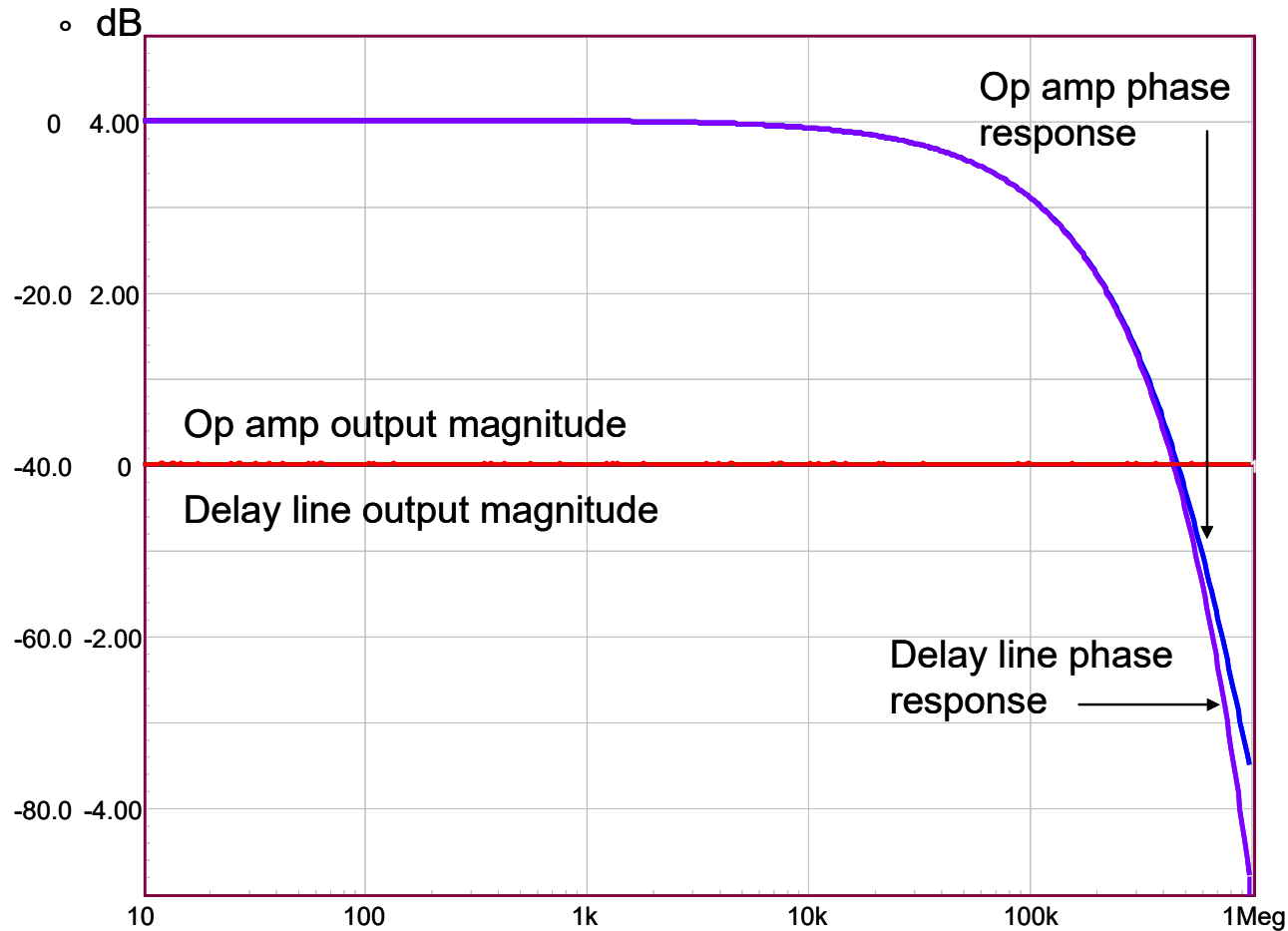
# How to Avoid the Delay Line?

- Good phase response of the analogue circuit



# Delay Margin versus Phase Margin

- The characteristic equation is affected by the delay:

$$\chi(s) = 1 + T(s) = 0 \quad \Longrightarrow \quad \chi(s) = 1 + e^{-s\tau} T(s) = 0$$

Unity return denominator  $T(s)$

- The stability condition for the magnitude does not change:

$$\left| e^{-s\tau_{\max}} T(\omega_c) \right| = 1 \quad \Longrightarrow \quad \left| e^{-s\tau} \right| = 1 \quad \Longrightarrow \quad \left| T(\omega_c) \right| = 1$$

- The stability condition for the argument does change:

$$-\pi = \arg\left(e^{-s\tau_{\max}}\right) + \arg T(\omega_c) = -\omega\tau_{\max} + \arg T(\omega_c)$$

$$\varphi_m = \pi + \arg T(\omega_c)$$

The max acceptable delay in the loop

$$\tau_{\max} = \frac{\varphi_m}{\omega_c}$$

Solving for  $\tau_{\max}$

# Delay Margin versus Phase Margin

□ The delay margin is thus defined by:

$$\Delta\tau = \tau_{\max} - \tau$$

← Current delay

← Maximum acceptable delay


1. A buck converter features a 250-ns internal delay
2. At a 100-kHz crossover, the phase margin is 49.5°
3. The maximum delay, accounting for 250 ns, is:

$$\tau_{\max} = \frac{\varphi_m}{\omega_c} = \frac{49.5}{2\pi \times 100k} \frac{\pi}{180} = 1.375 \mu\text{s}$$

$$\Delta\tau = 1.375 - 0.250 = 1.125 \mu\text{s} \longrightarrow \text{Maximum acceptable extra delay}$$
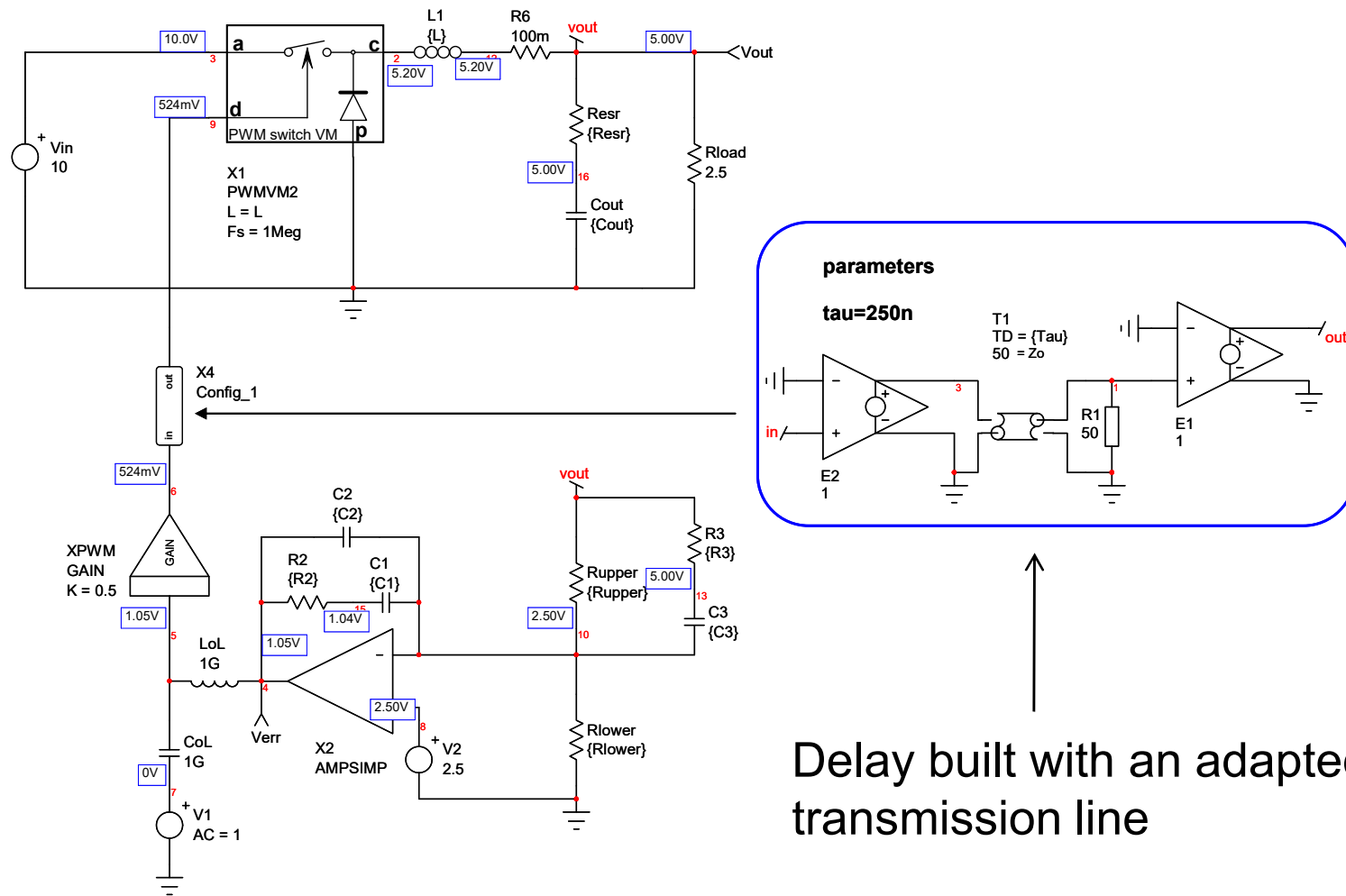
# Checking via Simulation


- The delay is simply added in series with the PWM block



Delay built with an adapted transmission line

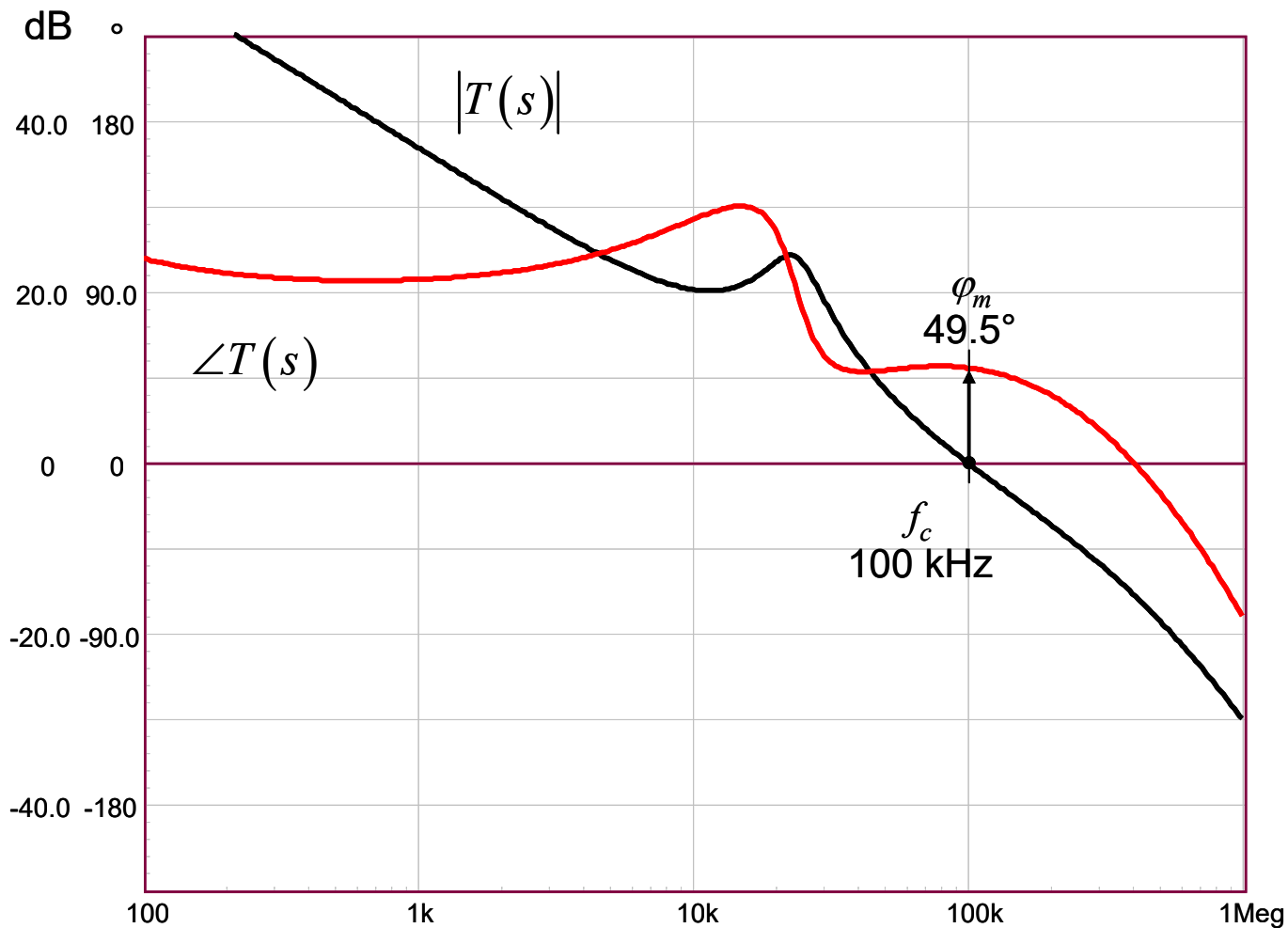
# Checking via Simulation

- With a 250-ns delay, the phase margin is acceptable


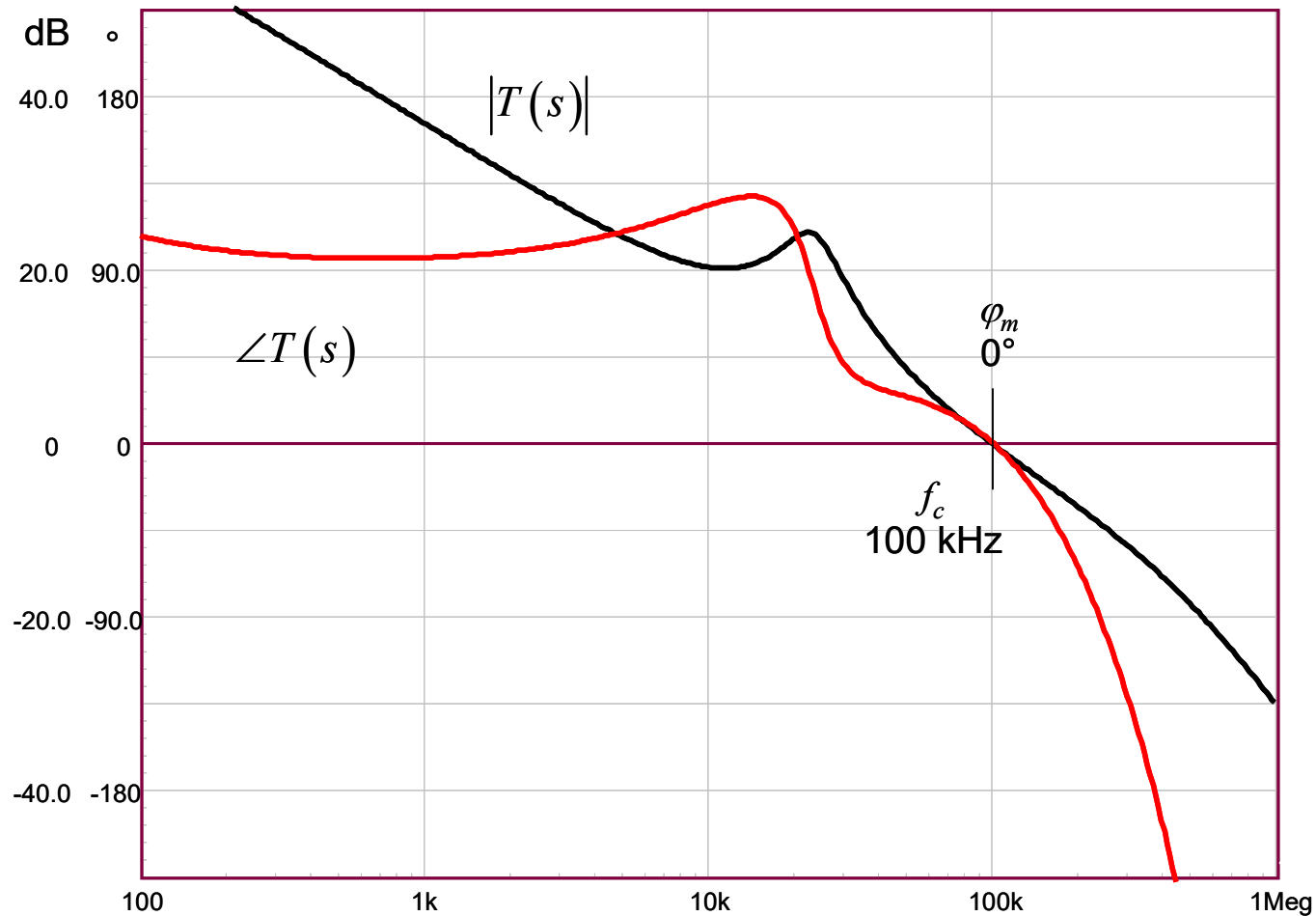
# Checking via Simulation

- If we add 1.125  $\mu\text{s}$  to 250 ns, no phase margin at all!



# Course Agenda


- Introduction to Control Systems
- Shaping the Error Signal
- How to Implement the PID Block?
- The PID at Work with a Buck Converter
- Considering the Output Impedance
- Classical Poles/Zeros Placement
- Shaping the Output Impedance
- Quality Factor and Phase Margin
- What is Delay Margin?
- Gain Margin is not Enough**




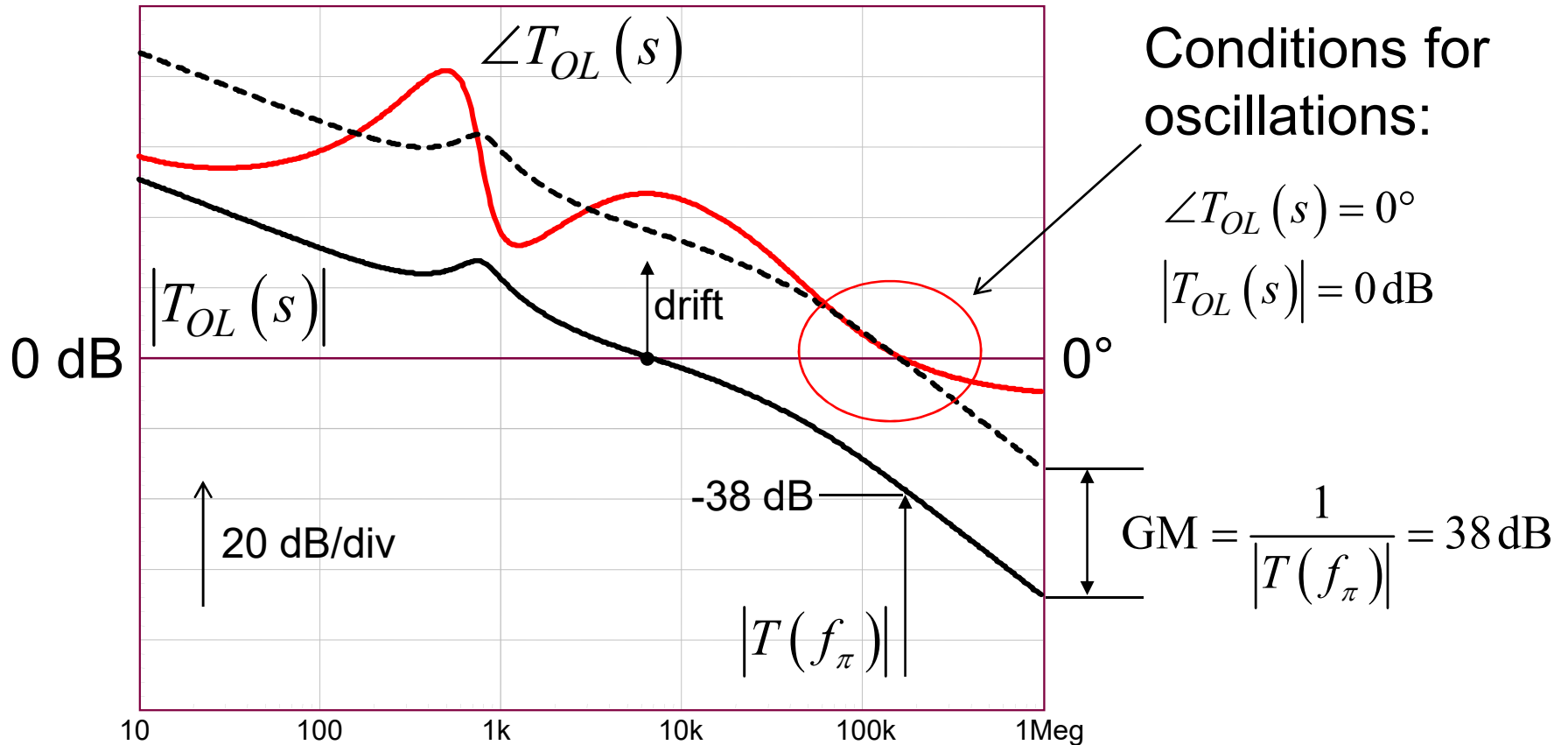
# Gain Margin Defines the Robustness


- GM defines the robustness of a system to gain variations



- If the gain drifts up by 38 dB, we have oscillations
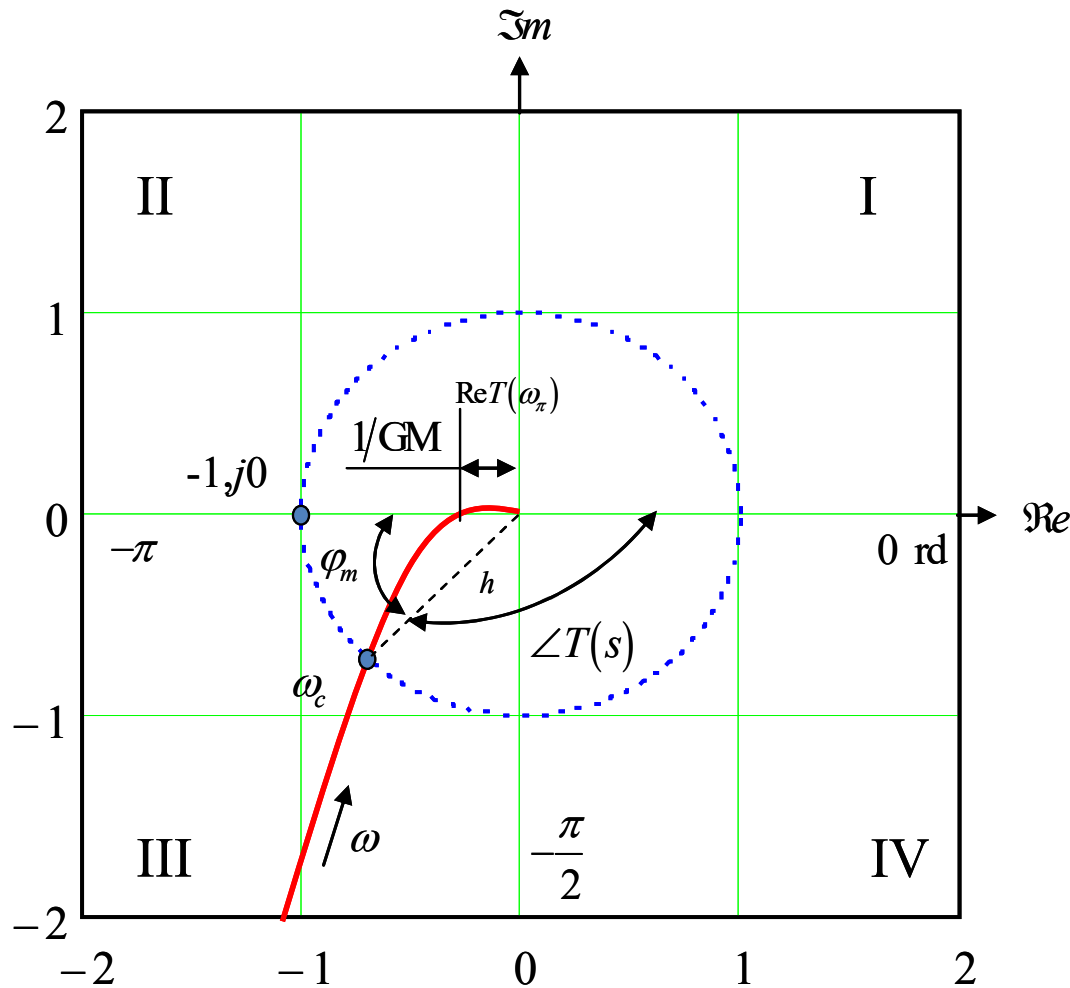
# Gain Margin Defines the Robustness

- In Bode representation but also in Nyquist



$$\angle T(s) = \pi \text{ or } -\pi$$



$$\text{Im } T(s) = 0$$



$$\text{GM} = \frac{1}{\sqrt{\text{Re}T(f_\pi)^2 + \text{Im}T(f_\pi)^2}}$$





$$\frac{1}{\text{GM}} = \text{Re}T(f_\pi)$$


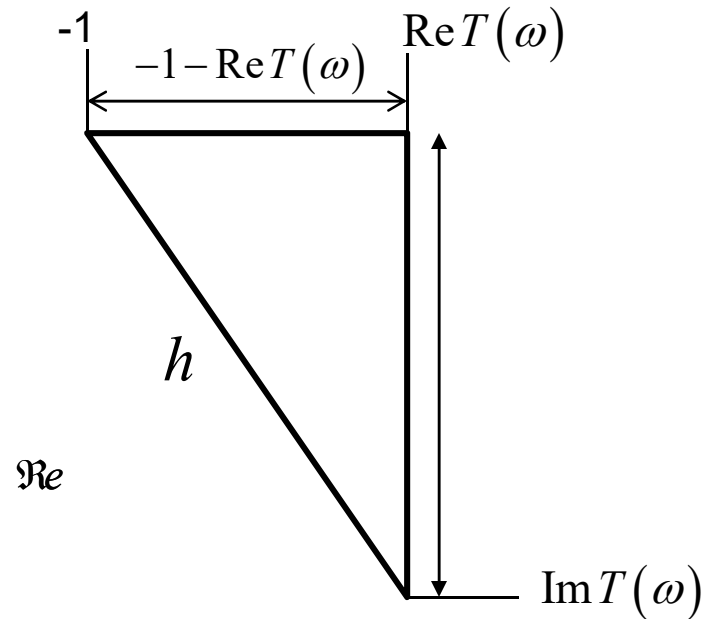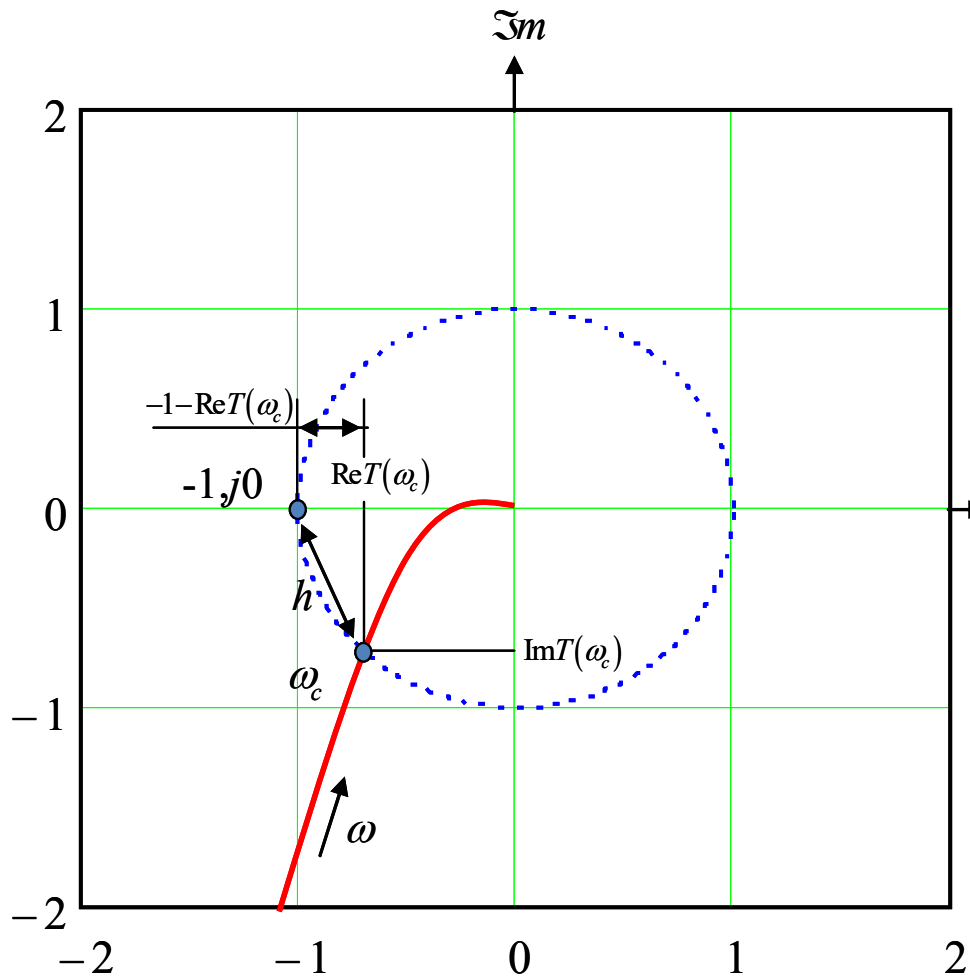
# Gain Margin in Nyquist

□ What really matters is the distance to the "-1" point



$$h = \sqrt{\left[-(1 + \Re T(\omega))\right]^2 + \Im T(\omega)^2}$$




$$h = |1 + T(s)|$$


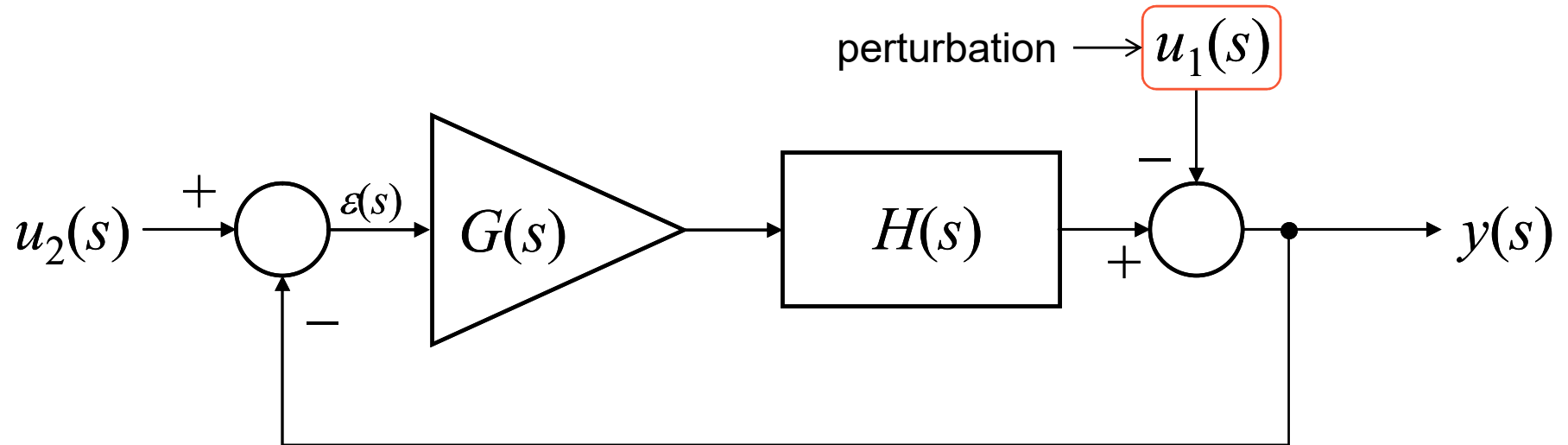
# Rejecting the Perturbation

- A closed-loop system rejects the incoming perturbation  $u_1$





$$y(s) = u_2(s) \frac{T(s)}{1+T(s)} - u_1(s) \frac{1}{1+T(s)}$$

$\uparrow$   
 Sensitivity function  $S$



$\left. \vphantom{\frac{1}{1+T(s)}} \right\} h = |1+T(s)| = \frac{1}{S}$
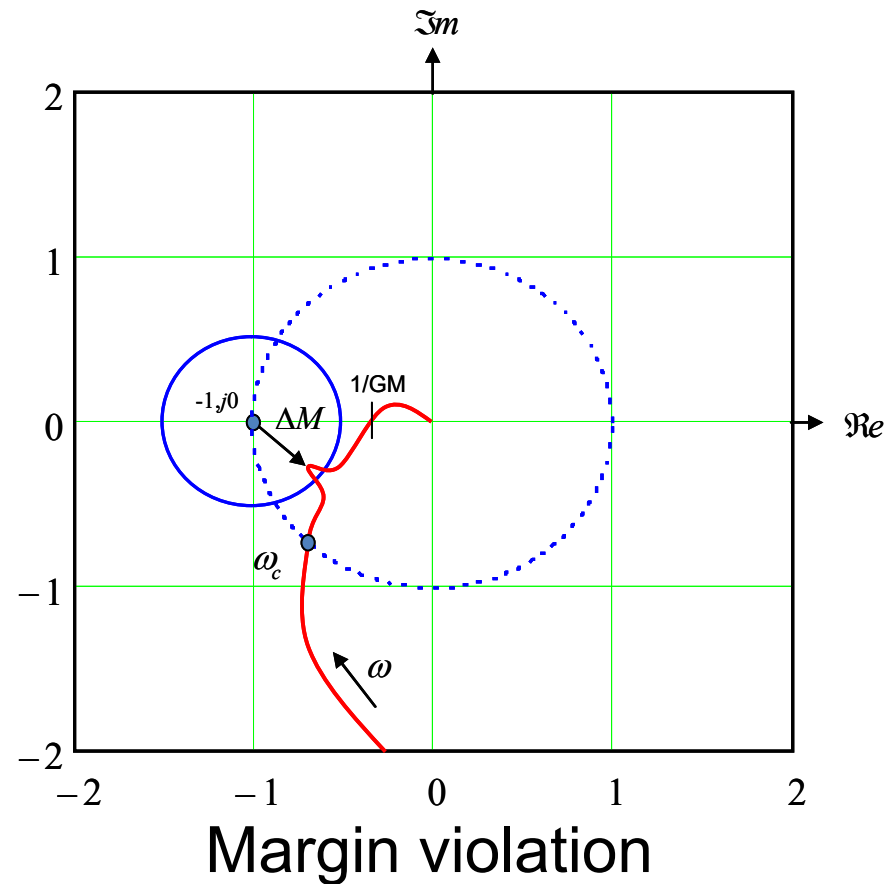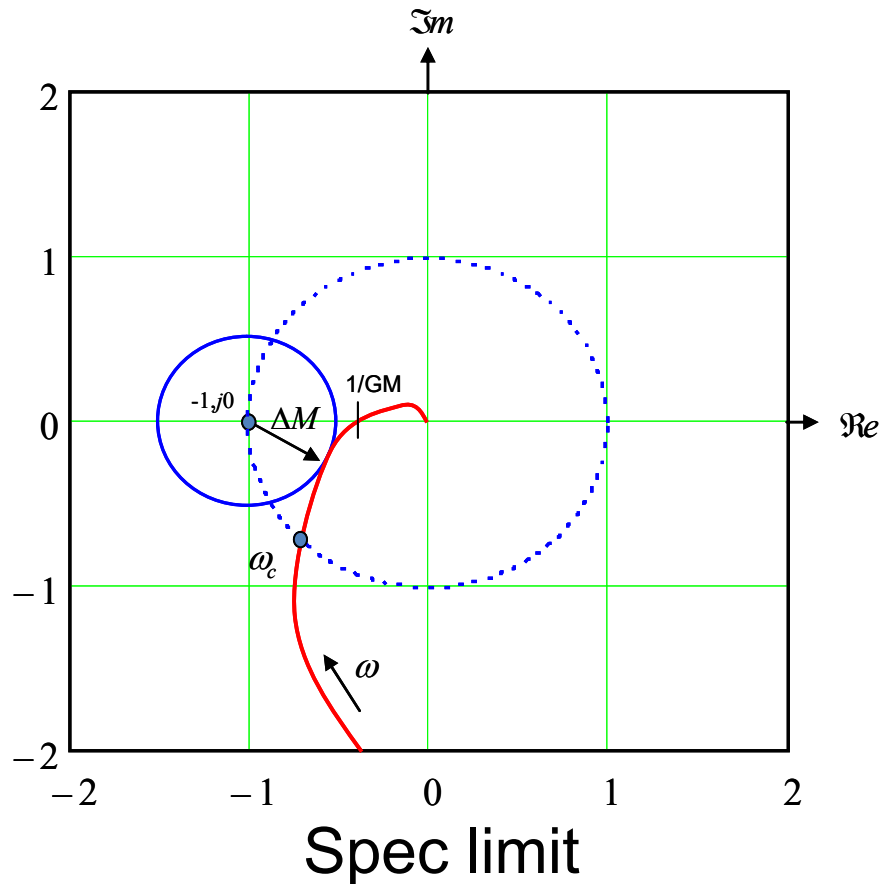
# Watch for a Peak in S

- ❑ The trajectory must keep away from the "-1" point
- ❑ A 0.5-radius circle detects a peak in  $S$ : modulus margin



# Bode can also Show the Modulus Margin

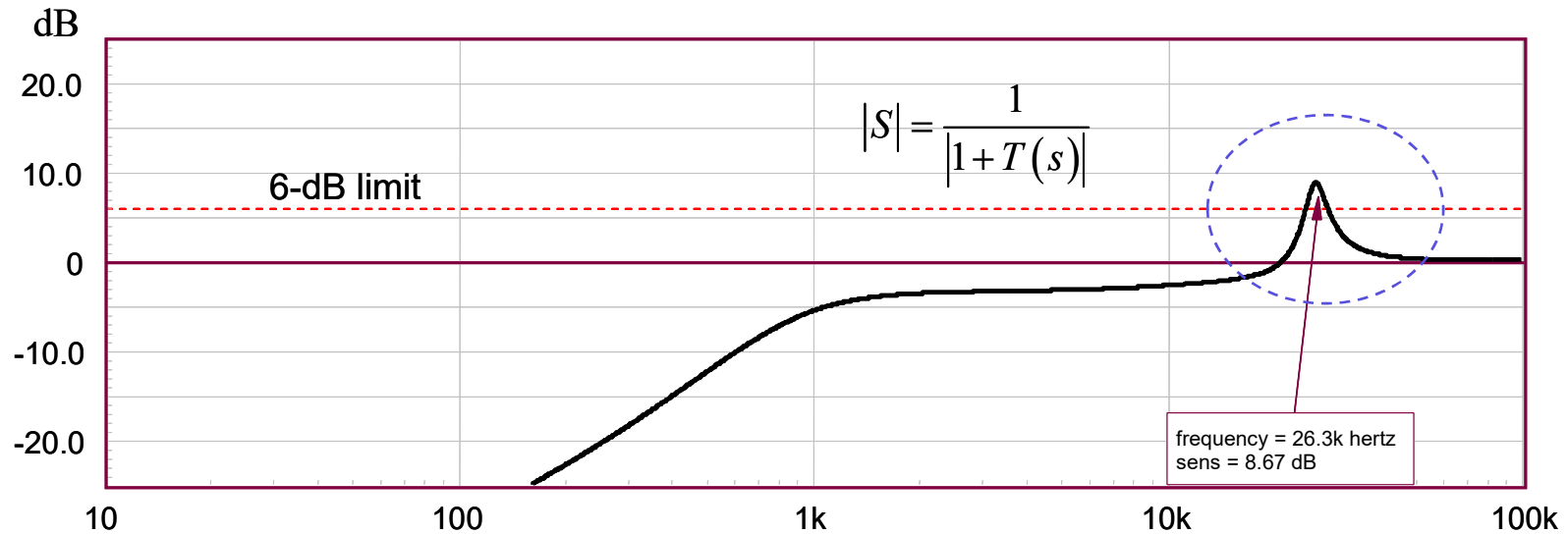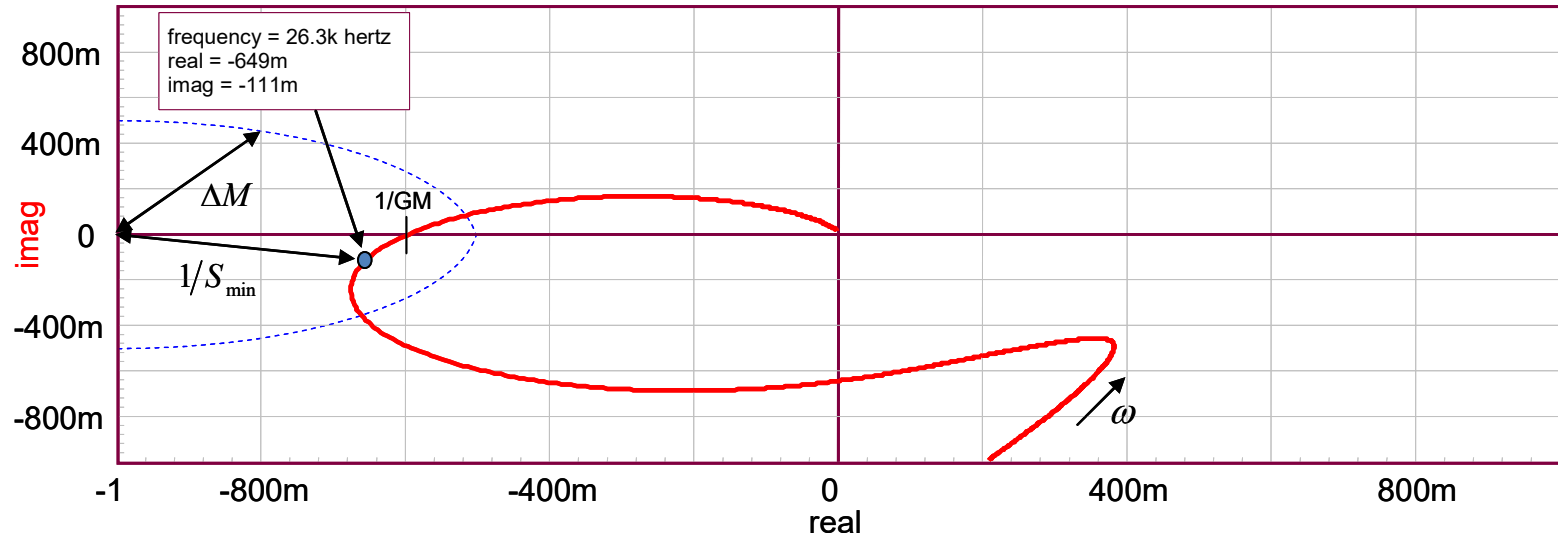

# Conclusion

- ❑ Switching or linear power supplies are regulators
- ❑ Applying a pure mathematical compensation brings problems
- ❑ Engineering judgment found output impedance guilty
- ❑ Lack of sufficient gain at resonance brings oscillations
- ❑ Standard poles/zeros placement method gives good results
- ❑ For high-speed dc-dc converters, resistive shaping rules
- ❑  $Q$  to phase margin approximation requires engineering judgment
- ❑ Less known delay and modulus margins are useful figures!



Merci !  
Thank you!  
Xiè-xie!

